


9

Op-Amps and 555 Timer



Multiple Choice Questions

 - Q.1** In an ideal differential amplifier shown in figure, a large value of R_E



- (a) increases both differential and common mode pairs
(b) increases the common mode gain only
(c) decreases the differential mode gain only
(d) decrease the common mode gain only
- Q.2** A change in the value of emitter resistance R_E in a difference amplifier
- (a) affects A_d
(b) affects A_c
(c) affects both A_d and A_c
(d) does not affect either A_d or A_c
- Q.3** In a differential amplifier, CMRR can be improved by using an increased
- (a) emitter resistance
(b) collector resistance
(c) power supply voltage
(d) source resistance

- Q.4** A differential amplifier has inputs $V_1 = 1050 \mu\text{V}$ and $V_2 = 950 \mu\text{V}$ with CMRR = 1000, what is the error in differential output?

(a) 10% (b) 1%
(c) 0.1% (d) 0.01%

- Q.5** The differential gain of op-amp is 4000 and value of CMRR is 150. Its output voltage, when the two input voltages are $200 \mu\text{V}$ and $160 \mu\text{V}$ respectively, will be

(a) 16 V (b) 164.8 mV
(c) 64 mV (d) 76 mV

[ESE-2014]

- Q.6** Consider the following statements:

1. A differential amplifier is used at the input stage of an operational amplifier.


2. Differential amplifiers have very high CMRR.

Which of these statements are correct?

(a) Both 1 and 2 (b) Neither 1 nor 2
(c) 1 only (d) 2 only


[ESE-2013]

 - Q.7** The op-amp in the figure has an input offset voltage of 5 mV and an open loop voltage gain of 10000, then V_o will be




(a) 0 (b) 5 mV
(c) +15 V or -15 V (d) +50 V or -50 V

Q.8 In the circuit of figure, V_o is

 


- (a) -1 V (b) 2 V
(c) +1 V (d) +15 V

 Q.9 Assuming the op-amp to be ideal. The voltage gain of the amplifier shown below is




- (a) $-\frac{R_2}{R_1}$ (b) $-\frac{R_3}{R_1}$
(c) $-\left(\frac{R_2 \parallel R_3}{R_1}\right)$ (d) $-\left(\frac{R_2 + R_3}{R_1}\right)$

 Q.10 The V_o of the op-amp circuit shown is




- (a) $11 V_i$ (b) $10 V_i$
(c) V_i (d) zero

 Q.11 Find V_o for the circuit shown below:




- (a) 6 V (b) 15 V
(c) 10 V (d) 18 V

 Q.12 The output voltage V_o of the circuit is




- (a) -4 V (b) 6 V
(c) 5 V (d) -5.5 V

 Q.13 In the circuit shown in the figure the current flowing through resistance of 100Ω would be



- (a) 8 mA (b) 10 mA
(c) 20 mA (d) 100 mA

 
Q.14 In the circuit shown below the op-amps are ideal. Then V_{out} in Volts is



- (a) 4 (b) 6
(c) 8 (d) 10

[GATE-2013]

 
Q.15 Given that the op-amps in the figure are ideal, the output voltage V_o is



- (a) $(V_1 - V_2)$ (b) $2(V_1 - V_2)$
(c) $\frac{(V_1 - V_2)}{2}$ (d) $(V_1 + V_2)$

[GATE-2014]

 Q.16 Assume the op-amp to be ideal. The current I through $1\text{ k}\Omega$ resistor is




- (a) -2 mA (b) -4 mA
(c) -6 mA (d) -8 mA

Q.17 The data sheet of an op-amp gives a mid band voltage gain of 200000 with a cut-off frequency of 10 Hz. What is the voltage gain at 1 MHz?

- (a) 2 (b) 3.2
(c) 1 (d) 0

 Q.18 The bandwidth of an amplifier circuit given below is. It is given that 0 dB product of the op-amp is 1 MHz:




- (a) 10^5 Hz (b) 10^7 Hz
(c) 10^4 Hz (d) none

Q.19 An amplifier using an opamp with a slew-rate $SR = 1\text{ V}/\mu\text{sec}$ has a gain of 40 dB. If this amplifier has to faithfully amplify sinusoidal signals from dc to 20 kHz without introducing any slew-rate induced distortion, then the input signal level must not exceed.

- (a) 795 mV (b) 395 mV
(c) 79.5 mV (d) 39.5 mV


[GATE-2002]

 Q.20 For the op-amp circuit given below determine the maximum input signal frequency in rad/sec. that can be used to get an distortionless output by taking $SR = 0.5\text{ V}/\mu\text{sec}$.



- (a) 1.04×10^6 rad/sec
(b) 2.04×10^6 rad/sec
(c) 1.32×10^4 rad/sec
(d) 0.26×10^5 rad/sec

 Q.21 A non-inverting op-amp is shown below (assume ideal op-amp)




The output voltage V_o for an input $V_i = [2 + \sin(100t)]\text{ V}$

- (a) $3/2 \sin(100t)$ (b) $3 \sin(100t)$
(c) $2 \sin(100t)$ (d) $3 \sin(100t) + 1/2$


[ESE-2002]

 Q.22 In the Op-Amp circuit shown, assume that the diode current follows the equation $I = I_s \exp(V/V_T)$. For $V_i = 2\text{ V}$, $V_o = V_{o1}$, and for $V_i = 4\text{ V}$, $V_o = V_{o2}$. The relationship between V_{o1} and V_{o2} is




- (a) $V_{02} = \sqrt{2} V_{01}$
 (b) $V_{02} = e^2 V_{01}$
 (c) $V_{02} = V_{01} \ln 2$
 (d) $V_{01} - V_{02} = V_T \ln 2$ [GATE-2007]

 Q.23 In the inverting op-amp circuit shown below, the resistance R_g is chosen as $R_1 \parallel R_2$ in order to




- (a) increase gain
 (b) reduce offset voltage
 (c) reduce offset current
 (d) increase CMRR [ESE-2002(E)]

 Q.24 Find V_0 for the circuit shown below:



- (a) $-V_{req} \frac{V_z}{V_x}$
 (b) $-V_{req} \frac{V_x}{V_z}$
 (c) $-V_{req} V_z$
 (d) $-V_{req} V_x$

 
Q.25 In the circuit shown below what is the output voltage (V_{out}) if a silicon transistor Q and an ideal op-amp are used?



- (a) -15 V
 (b) -0.7 V
 (c) +0.7 V
 (d) +15 V

[GATE-2013]

 Q.26 An operational amplifier circuit is shown in the figure.







The output of the circuit for a given input v_i is

- (a) $-\left(\frac{R_2}{R_1}\right) v_i$
 (b) $-\left(1 + \frac{R_2}{R_1}\right) v_i$
 (c) $\left(1 + \frac{R_2}{R_1}\right) v_i$
 (d) $+V_{sat}$ or $-V_{sat}$



[GATE-2014]

    Q.27 The transfer characteristic for the precision rectifier circuit shown below is (assume ideal OP-AMP and practical diodes)




[GATE-2010]

  Q.28 The transfer characteristic of the op-amp circuit shown in figure is



[GATE-2014]

 Q.29 In the figure assume the OP-AMPs to be ideal. The output v_0 of the circuit is




- (a) $10 \cos(100t)$
 (b) $10 \int_0^t \cos(100\tau) d\tau$

(c) $10^{-4} \int_0^t \cos(100\tau) d\tau$

(d) $10^{-4} \frac{d}{dt} \cos(100t)$

[GATE-2001]

 
Q.30 For the circuit shown in the following figure, the capacitor C is initially uncharged. At $t = 0$, the switch S is closed. The voltage V_C across the capacitor at $t = 1$ millisecond is (The Op-Amp is supplied with ± 15 V.)



- (a) 0 Volt
 (b) 6.3 Volts
 (c) 9.45 Volts
 (d) 10 Volts

[GATE-2006]

 
Q.31 In the circuit shown in the given figure, V_0 is given by



- (a) $\sin(t - \pi/4)$
 (b) $\sin(t + \pi/4)$
 (c) $\sin t$
 (d) $\cos t$

[ESE-2001]

 
Q.32 The Op-amp circuit shown in the figure is a filter. The type of filter and its cut-off frequency are respectively



- (a) high pass, 1000 rad/sec.
 (b) low pass, 1000 rad/sec.
 (c) high pass, 10000 rad/sec.
 (d) low pass, 10000 rad/sec.


[GATE-2005]

 Q.33 For the circuit shown in figure, the type of filter is



- (a) Low pass (b) Band pass
 (c) Band reject (d) High pass

 
Q.34 The input resistance of the circuit shown in the figure, assuming an ideal op-amp is



- (a) $\frac{R}{3}$ (b) $\frac{2R}{3}$
 (c) R (d) $\frac{4R}{3}$

[GATE-2009]

 
Q.35 Assuming base-emitter voltage of 0.7 V and $\beta = 99$ of transistor Q_1 , the output voltage V_o in the ideal opamp circuit shown below is



- (a) -1 V (b) -1/3.3 V
 (c) 0 V (d) 2 V

[GATE-2011]

 Q.36 An active filter is shown in the adjoining figure. The dc gain and the 3 dB cut-off frequency of the filter respectively, are nearly





$$R_1 = 15.9 \text{ k}\Omega, \quad R_2 = 159 \text{ k}\Omega, \\ C_1 = 1.0 \text{ nF}$$


- (a) 40 dB, 3.14 kHz (b) 40 dB, 1.00 kHz
 (c) 20 dB, 6.28 kHz (d) 20 dB, 1.00 kHz

[GATE-2010]

  Q.37 Given the ideal op-amp shown in figure indicate correct transfer characteristics assuming ideal diode with zero cut-in voltage



 
Q.38 The saturation voltage of the ideal op-amp shown below is $\pm 10 \text{ V}$. The output voltage V_o of the following circuit in the steady-state is



- (a) square wave of period 0.55 ms
 (b) triangular wave of period 0.55 ms
 (c) square wave of period 0.25 ms
 (d) triangular wave of period 0.25 ms

[GATE-2015]

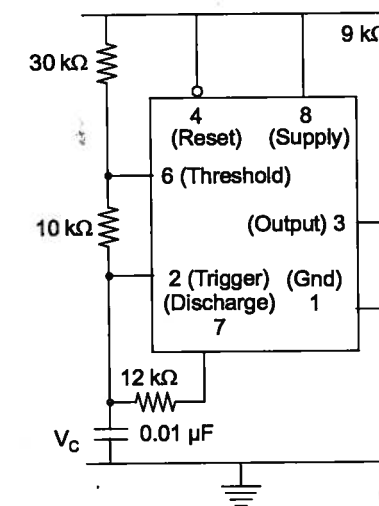Q.39 An astable multi-vibrator circuit using IC 555 timer is shown below. Assume that the circuit is oscillating steadily.




The voltage V_C across the capacitor varies between

- (a) 3 V to 5 V (b) 3 V to 6 V
 (c) 3.6 V to 6 V (d) 3.6 V to 5 V

[GATE-2008]

 Q.40 Circuit shown in the figure represents




- (a) astable multivibrator
 (b) a mono stable multi vibrator
 (c) voltage controlled oscillator
 (d) ramp generator


Numerical Data Type Questions

Q.41 Consider an inverting amplifier circuit having gain of -100 is designed using an op-amp and two resistors $R_1 = 10 \text{ k}\Omega$ and $R_2 = 1 \text{ M}\Omega$. If the op-amp is specified to have input bias current of 100 nA and input offset current of 10 nA then the output dc offset voltage will be = ____ V. Assume bias current at inverting terminal is greater than bias current at non-inverting terminal.

 Q.42 The following circuit has $R = 10 \text{ k}\Omega$, $C = 10 \text{ μF}$. The input voltage is sinusoidal having frequency of 50 Hz and rms value of 10 V. Under ideal condition the phase of i_s with respect to V_s is ____.



 Q.43 Consider the ideal op-amp circuit shown below.




If it is given that

$$\frac{R_2}{R_1} = 10, \frac{R_4}{R_3} = 11$$


then the common mode rejection ratio (CMRR) is ____ dB.

 Q.44 For the circuit shown below the input resistance is ____ k Ω .



Q.45 An op-amp has an open-loop gain of 10^5 and an open-loop upper cut-off frequency of 10 Hz. If this op-amp is connected as an amplifier with a closed-loop gain of 100, then the new upper cut-off frequency is ____ kHz.

 Q.46 An oscillator circuit using ideal op-amp and diodes is shown in the figure.




The time duration for +ve part of the cycle is Δt_1 and for -ve part is Δt_2 . The value of $e^{\frac{\Delta t_1 - \Delta t_2}{RC}}$ will be ____.





[GATE-2014]




T1. For the circuit shown below

 

    the transfer characteristic can be represented as




 T2. Consider an op-amp circuit shown in figure, with an open loop gain of $A_{ol} = 10^5$ and open loop input impedance $R_{oi} = 10 \text{ k}\Omega$. If the output resistance of op-amp is zero, then closed loop input impedance (R_{if}) at the inverting terminal of op-amp is



 - (a) $R_{if} = 10 \text{ k}\Omega$ (b) $R_{if} = 1 \text{ k}\Omega$
(c) $R_{if} = 40 \text{ k}\Omega$ (d) $R_{if} = 0.1 \Omega$


T3. Consider the amplifier circuit shown below, where A_v is the voltage gain of amplifier.



What is the value of input resistance, $R_{in} = \frac{V_{in}}{i_{in}}$?

 - (a) $\frac{A_v R_f}{1 - A_v}$ (b) $(1 - A_v) R_f$
(c) $\frac{R_f}{1 - A_v}$ (d) $\frac{(1 - A_v)}{A_v} R_f$


T4. Consider the circuit shown in figure below. Assume op-amp is ideal.



What is the value of current i_o ?

- (a) $-\frac{V_{in}}{10 \text{ k}\Omega}$ (b) $-\frac{V_{in}}{R_f}$
(c) $-\frac{V_{in}}{R_L}$ (d) None of the above

T5. In the figure shown below.

 

If $R_A = R_B$ then

- (a) Duty cycle of the output wave is greater than 50%.
(b) Duty cycle of the output wave is 50%.
(c) R_A and R_B do not influence the duty cycle of the output.
(d) Duty cycle is 50% irrespective of R_A and R_B values.