

# CURRENT ELECTRICITY

## 1. State and explain Ohm's law

This law states that, *the current flowing through a conductor is directly proportional to the potential difference between the ends of the conductor. Provided temperature and other physical conditions of the conductor remaining constant*

$$I \propto V$$

$$I = \frac{1}{R} V$$

$$V = IR$$

## 2. Define (a) Drift velocity

## (b) Mobility of electrons

**Drift velocity:** The average velocity with which free electrons get drifted towards the positive end of conductor under the influence of an external electric field is called drift velocity.

**Mobility:** It is defined as the ratio of magnitude of drift velocity per unit electric field.

$$\mu = \frac{|v_d|}{E}$$

## 3. Derive an expression for Drift velocity in terms of electric field and relaxation time.

The average velocity of the electrons due to *random motion in the conductor* will be zero.

This velocity is given by  $u_{av} = 0$

When a potential difference  $V$  is applied between the ends of the conductor, it produces an electric field  $E$ .

It exerts force on the electron in the opposite direction, therefore electron accelerates in the opposite direction.

$$a = \frac{-F}{m} = \frac{-eE}{m}$$



And The average time between successive collisions is denoted by  $\tau$  and is given by

$$t_{av} = \tau = \frac{t_1 + t_2 + t_3 + \dots + t_N}{N}$$

Consider,  $v = u + at$

$$V_d = 0 + \frac{-eE}{m} \cdot \tau$$

$$\therefore v_d = -\frac{eE}{m} \tau \rightarrow \text{This is the expression for drift velocity.}$$


#### 4. Write the Limitations of Ohm's law

The limitations of Ohm's law are

- 1) The variation between Current and Potential difference is non linear.
- 2) The relation between Current and Potential difference is non unique.
- 3) Ohm's law is not applicable for semiconductors.
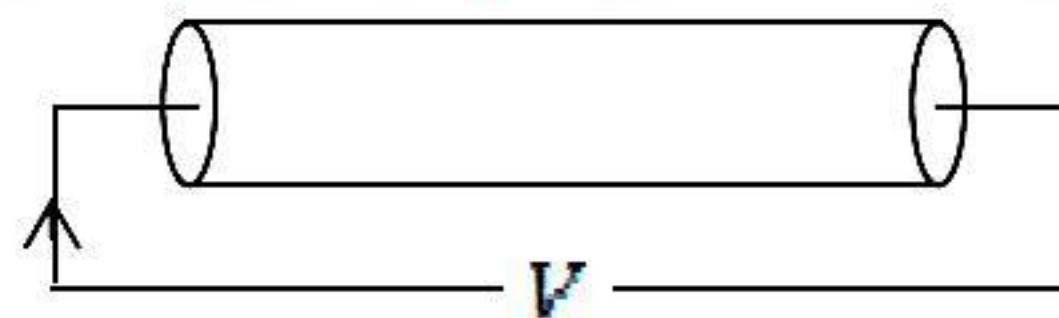
#### 5. Derive the vector form of ohm's law $\vec{J} = \sigma \vec{E}$

Or Derive an expression for equivalent form of Ohm's law.



Let  $I$  be the current in the conductor due to the potential difference  $V$  across the conductor, then according to ohm's law

$$V = IR \dots\dots\dots(i)$$

The electric field  $E$  produced in the conductor is given by

$$E = \frac{V}{L}$$

$$\therefore V = EL \dots\dots\dots(ii)$$

From (i) and (ii) we get

$$EL = IR$$

$$EL = I \times \rho \frac{L}{A} \quad \left( R = \rho \frac{L}{A} \right)$$


$$EL = \rho J L \quad \left( \frac{I}{A} = J \right)$$

$$E = \rho J$$

$$J = \frac{E}{\rho} \quad \left( \frac{1}{\rho} = \sigma \right)$$

$$\vec{J} = \sigma \vec{E} \rightarrow \text{This is the vector form of ohm's law.}$$
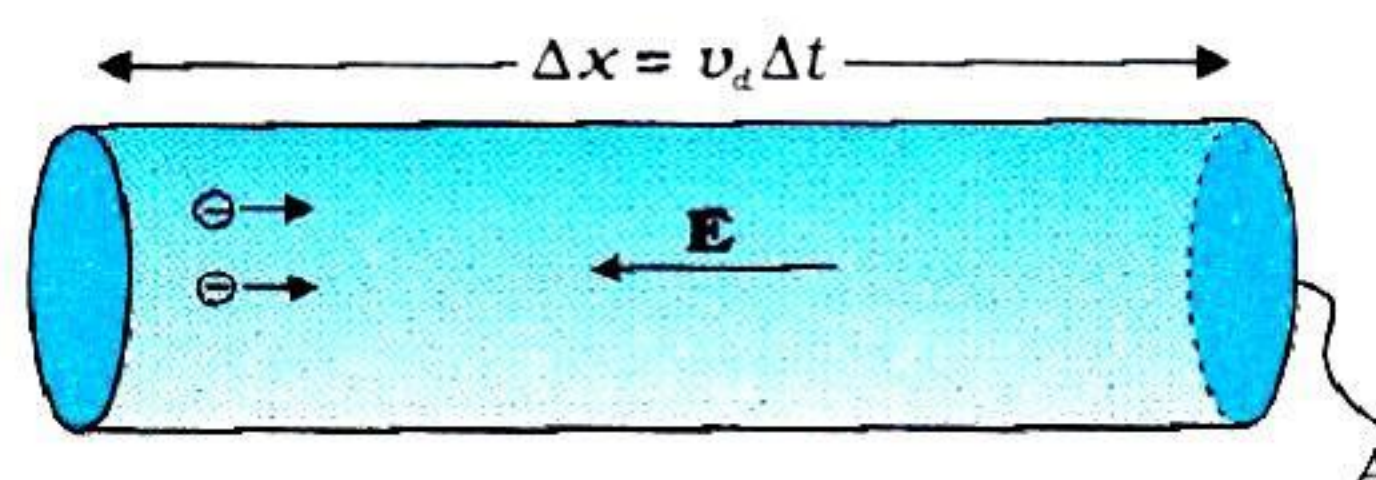
#### 6. Obtain an Expression for conductivity $(\sigma = \frac{ne^2\tau}{m})$ of a conductor.



The expression for current in the conductor is given by

$$I = nAev_d \quad \text{but } v_d = \frac{e\tau}{m} E$$

$$I = nAe \frac{e\tau}{m} E \quad \text{by defn., } \frac{I}{A} = J$$



$$\frac{I}{A} = \frac{ne^2\tau}{m} E$$

$$|J| = \frac{ne^2\tau}{m} |E| \quad \text{As } J \text{ is parallel to } E$$

$$J = \frac{ne^2\tau}{m} E \quad \text{but } J = \sigma E$$


$$\sigma E = \frac{ne^2\tau}{m} E$$

$$\sigma = \frac{ne^2\tau}{m} \rightarrow \text{This is the expression for conductivity}$$

**7. Draw the graph for temperature dependence of Resistivity of**  
**(a) metals and (b) semiconductors (c) Nichrome**


**1) In Metals:** Resistivity is directly proportional to temperature

**i.e.**  $\rho \propto T$

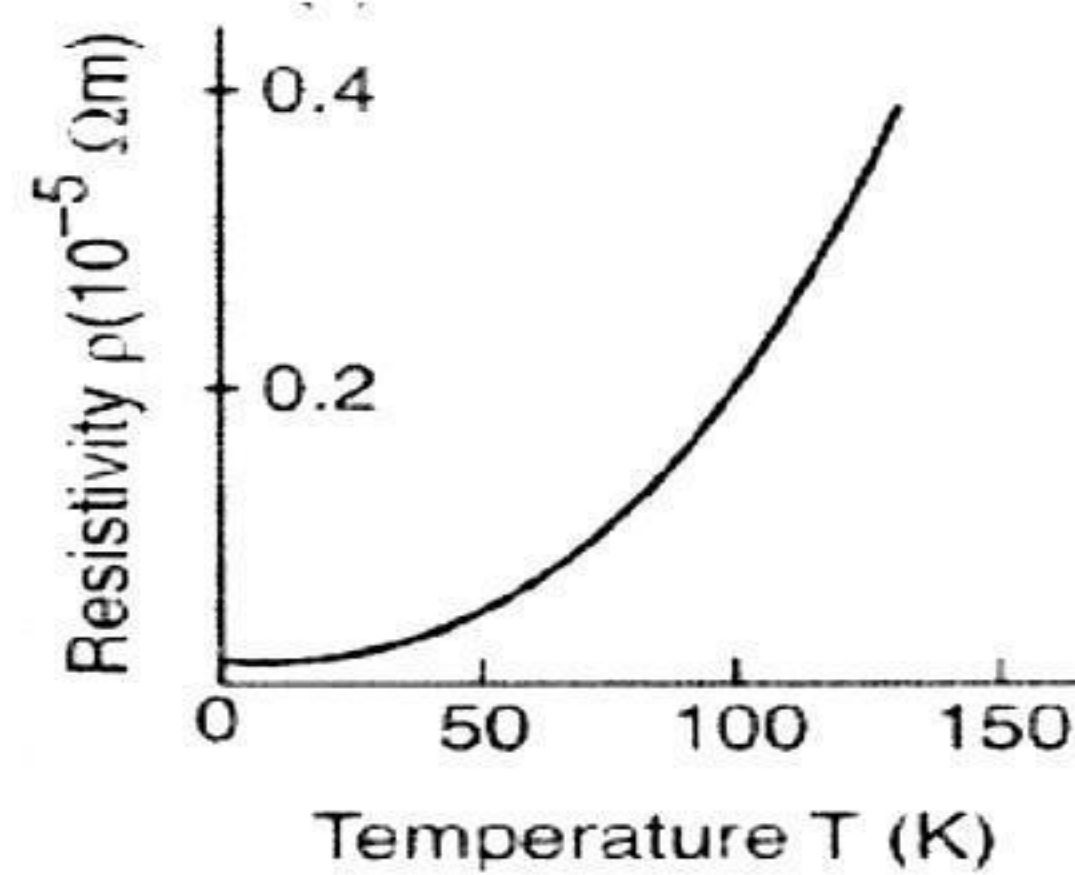


**2) In semiconductors :** Resistivity is inversely proportional to temperature

**i.e.**  $\rho \propto \frac{1}{T}$

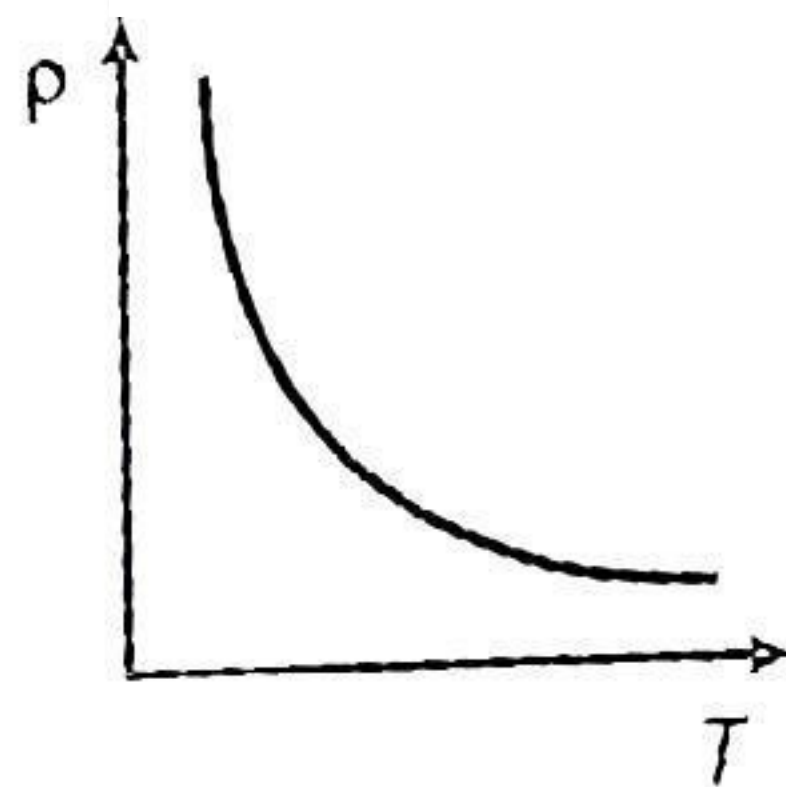

**3) Nichrome :**

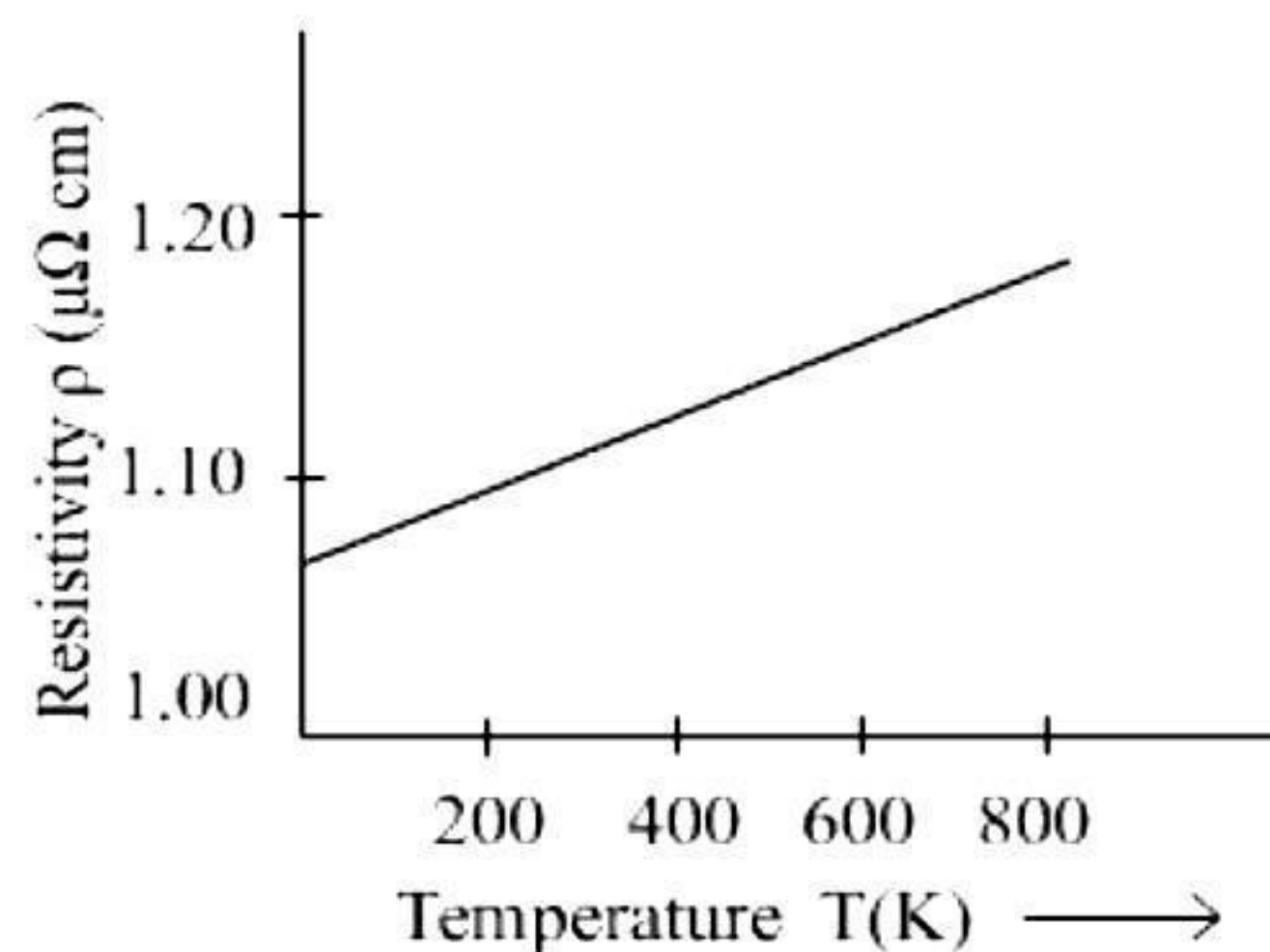



## 8. Obtain an expression for effective emf and internal resistance of Cells connected in series:

The terminal potential of cell  $E_1$  is  $V_1 = E_1 - I r_1$

The terminal potential of cell  $E_2$  is  $V_2 = E_2 - I r_2$

The terminal potential of the combination

$$V_{\text{eff}} = V_1 + V_2 = E_1 - I r_1 + E_2 - I r_2 \\ = E_1 + E_2 - I (r_1 + r_2)$$


$$V_{\text{eff}} = E_1 + E_2 - I [r_1 + r_2] \quad \text{----- (1)}$$

For the combination we have


$$V_{\text{eff}} = E_{\text{eff}} - I r_{\text{eff}} \quad \text{----- (2)}$$

Comparing equations (1) and (2), we get.
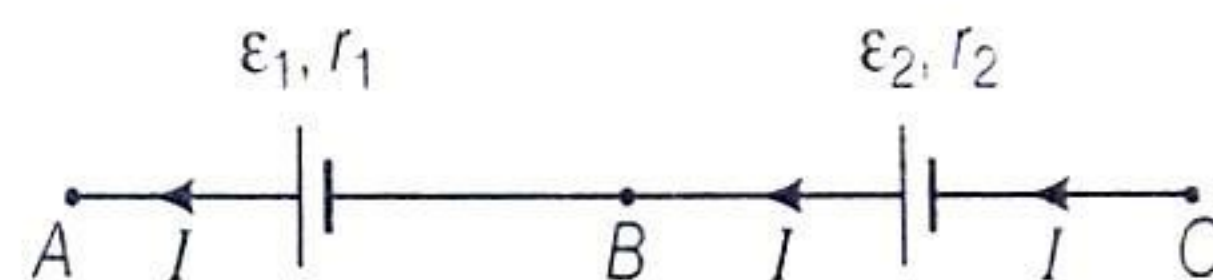
$$E_{\text{eff}} = E_1 + E_2 \text{ and } r_{\text{eff}} = r_1 + r_2$$




(a)

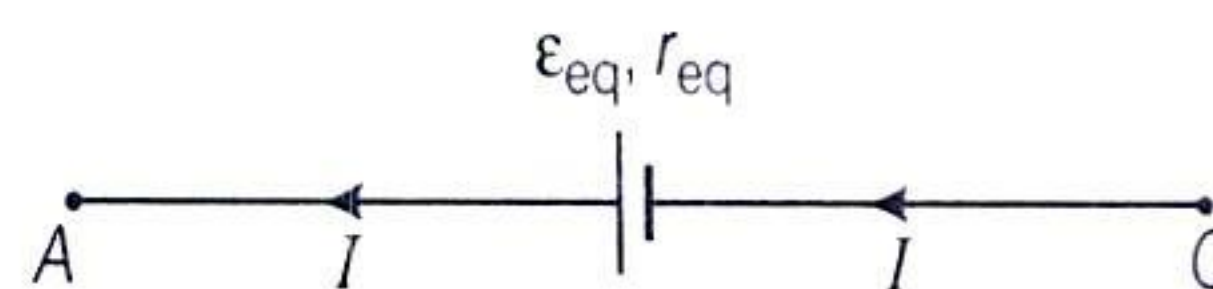


(b)
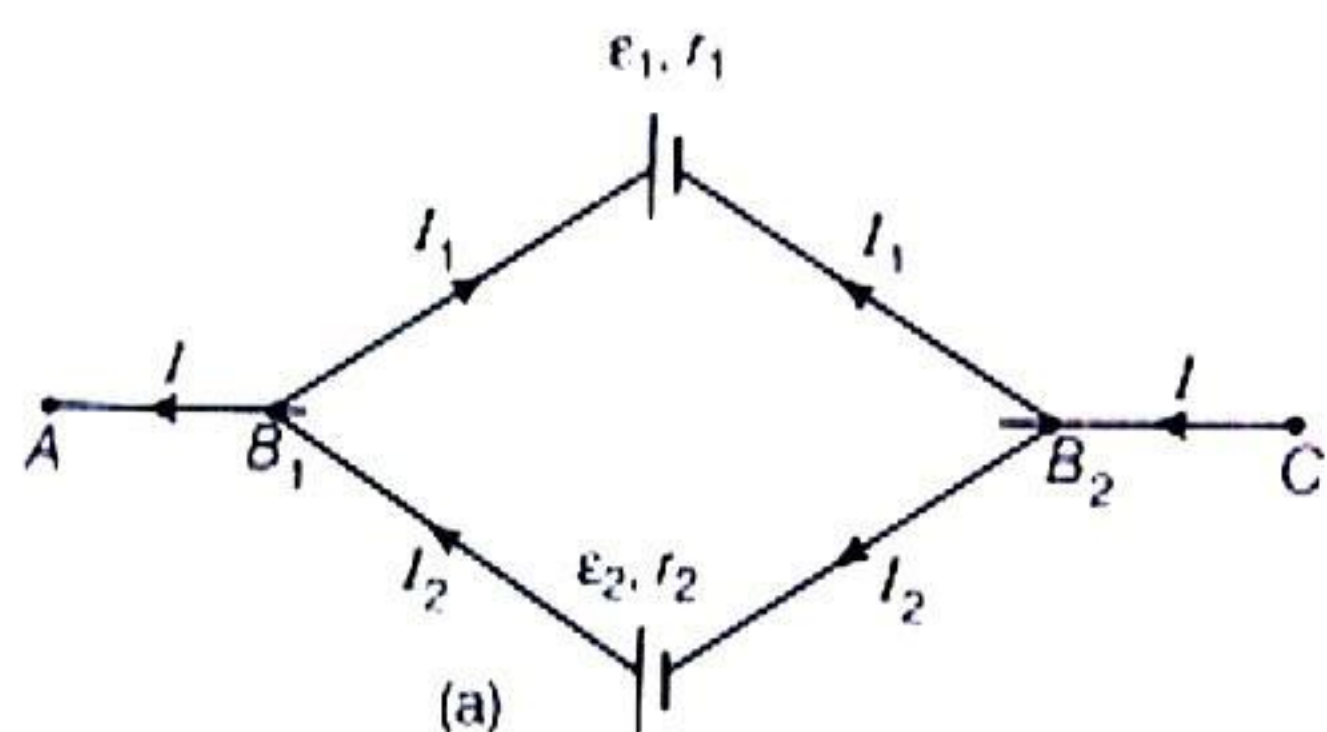
## 9. Obtain an expression for effective emf and internal resistance Cell in parallel.



(a)

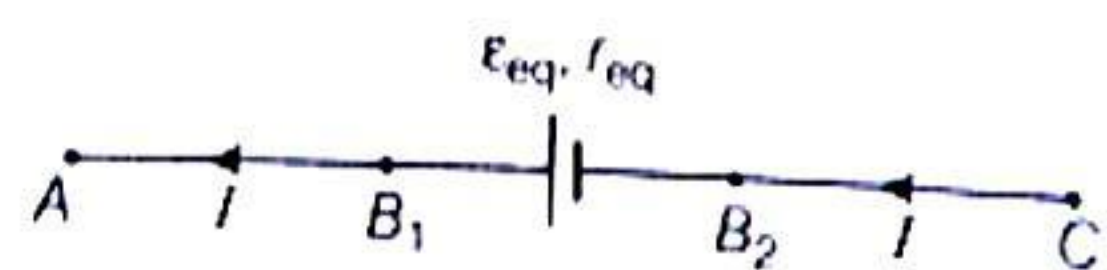

(b)

Potential difference across cell  $E_1$  is  $V_1 = E_1 - I_1 r_1$

Potential difference across cell  $E_2$  is  $V_2 = E_2 - I_2 r_2$

$$I_1 = \frac{E_1 - V_1}{r_1} = \frac{E_1 - V}{r_1} \quad (\because V_1 = V_2 = V)$$

$$\text{Similarly } I_2 = \frac{E_2 - V}{r_2}$$

Main current in the circuit is given by

$$I = I_1 + I_2$$

$$I = \frac{E_1}{r_1} - \frac{V}{r_1} + \frac{E_2}{r_2} - \frac{V}{r_2}$$

$$I = \frac{E_1}{r_1} + \frac{E_2}{r_2} - V \left( \frac{1}{r_1} + \frac{1}{r_2} \right)$$

$$I = \frac{E_1 r_2 + E_2 r_1}{r_1 r_2} - V \left( \frac{r_1 + r_2}{r_1 r_2} \right)$$

$$V \left( \frac{r_1 + r_2}{r_1 r_2} \right) = \frac{E_1 r_2 + E_2 r_1}{r_1 r_2} - I$$

$$V = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} - I \left[ \frac{r_1 r_2}{r_1 + r_2} \right] \quad \text{----- (1)}$$

For the combination we have

$$V = E_{\text{eff}} - I r_{\text{eff}} \quad \text{----- (2)}$$

Comparing equations (1) and (2) we get

$$E_{\text{eff}} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} \text{ and } r_{\text{eff}} = \frac{r_1 r_2}{r_1 + r_2}$$



## 10. State Kirchhoff's laws (or rules).

**Junction rule:** In any electrical network, the algebraic sum of the currents at a junction is zero. **i.e.**  $\sum \mathbf{I} = \mathbf{0}$ .

Significance of Kirchhoff's I law is **law of conservation of charge**.

**Loop rule:** In any closed loop, the algebraic sum of the e.m.f is equal to the algebraic sum of product of currents and resistances in that mesh.

$$\sum \mathbf{E} = \sum \mathbf{IR}.$$

Significance of Kirchhoff's II law is '**law of conservation of energy**'.

## 11. Applications of Potentiometer:

- 1) It is used to verify the emf of the two different cells
- 2) It is used to find the internal resistance of the given cell.