
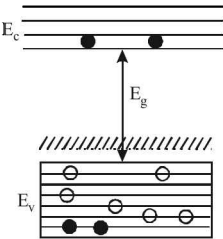







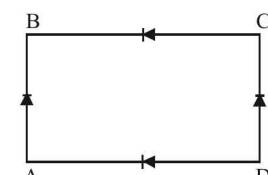


## Conceptual MCQs




- In order to prepare a p-type semiconductor, pure silicon can be doped with
  - Phosphorus
  - Aluminium
  - Antimony
  - Germanium
- In the energy band diagram of a material shown below, the open circles and filled circles denote holes and electrons respectively. The material is
  - an insulator
  - a metal
  - an n-type semiconductor
  - a p-type semiconductor
- In a full wave rectifier circuit operating from 50 Hz mains frequency, the fundamental frequency in the ripple would be
  - 25 Hz
  - 50 Hz
  - 70.7 Hz
  - 100 Hz
- In the middle of the depletion layer of a reverse-biased p-n junction, the
  - electric field is zero
  - potential is maximum
  - electric field is maximum
  - potential is zero
- p-n junction is said to be forward biased, when
  - the positive pole of the battery is joined to the p-semiconductor and negative pole to the n-semiconductor
  - the positive pole of the battery is joined to the n-semiconductor and p-semiconductor
  - the positive pole of the battery is connected to n-semiconductor and p-semiconductor
  - a mechanical force is applied in the forward direction
- The difference in the variation of resistance with temperature in a metal and a semiconductor arises essentially due to the difference in the
  - crystal structure
  - variation of the number of charge carriers with temperature
  - type of bonding
  - variation of scattering mechanism with temperature
- Application of a forward bias to a p-n junction
  - widens the depletion zone.
  - increases the potential difference across the depletion zone
  - increases the number of donors on the n side.
  - increases the electric field in the depletion zone.
- At absolute zero, Si acts as
  - non-metal
  - metal
  - insulator
  - None of these
- In a common base amplifier the phase difference between the input signal voltage and the output voltage is
  - 0
  - $\frac{\pi}{4}$
  - $\frac{\pi}{2}$
  - $\pi$
- A transistor has three impurity regions. All the three regions have different doping levels. In order of increasing doping level, the regions are
  - emitter, base and collector
  - collector, base and emitter
  - base, emitter and collector
  - base, collector and emitter
- For a transistor,  $I_C = 25$  mA and  $I_B = 1$  mA. The value of current gain  $\alpha$  is
  - $\frac{25}{26}$
  - $\frac{26}{25}$
  - $\frac{24}{25}$
  - $\frac{25}{24}$
- In figure, the input is across the terminals A and C and the output is across B and D. Then the output is
  - zero
  - same as the input
  - half wave rectified
  - full wave rectified
- The charge carriers in a p-type semiconductor are
  - electrons only
  - holes only
  - holes in larger number and electrons in smaller numbers
  - holes and electrons in equal numbers
- A common emitter amplifier has a voltage gain of 50, an input impedance of  $100\Omega$  and an output impedance of  $200\Omega$ . The power gain of the amplifier is
  - 1000
  - 1250
  - 100
  - 500
- NAND gate is a combination of
  - AND gate and NOT gate
  - AND gate and OR gate
  - NOT gate and OR gate
  - NOT gate and NOR gate




## Application Based MCQs

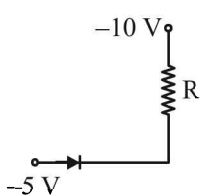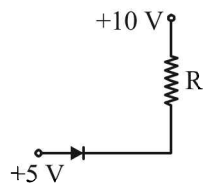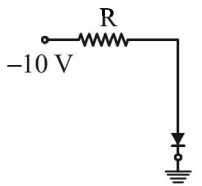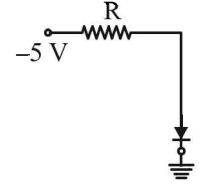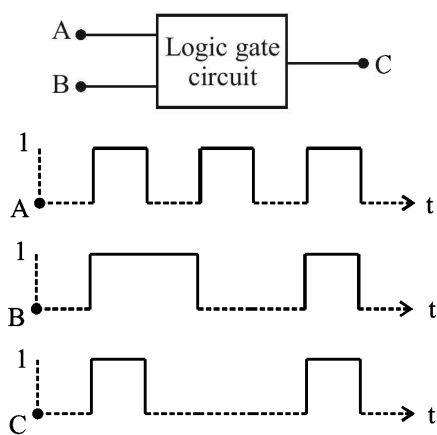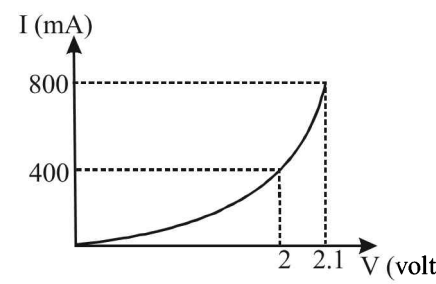16. If the ratio of the concentration of electrons to that of holes in a semiconductor is  $\frac{7}{5}$  and the ratio of currents is  $\frac{7}{4}$ , then what is the ratio of their drift velocities?
- (a)  $\frac{5}{8}$  (b)  $\frac{4}{5}$  (c)  $\frac{5}{4}$  (d)  $\frac{4}{7}$
17. A potential barrier of 0.50 V exists across a p-n junction. If the depletion region is  $5.0 \times 10^{-7}$  m wide, the intensity of the electric field in this region is
- (a)  $1.0 \times 10^6$  V/m (b)  $1.0 \times 10^5$  V/m  
(c)  $2.0 \times 10^5$  V/m (d)  $2.0 \times 10^6$  V/m
18. Which of the junction diodes shown below are forward biased?
- (a)  (b) 
- (c)  (d) 
19. A transistor is operated in common-emitter configuration at  $V_c = 2$  V such that a change in the base current from 100  $\mu$ A to 200  $\mu$ A produces a change in the collector current from 5 mA to 10 mA. The current gain is
- (a) 100 (b) 150 (c) 50 (d) 75
20. The device that can act as a complete electronic circuit is
- (a) junction diode (b) integrated circuit  
(c) junction transistor (d) zener diode
21. Transfer characteristics [output voltage ( $V_0$ ) vs input voltage ( $V_i$ )] for a base biased transistor in CE configuration is as shown in the figure. For using transistor as a switch, it is used
- (a) in region (III) (b) both in region (I) and (III)  
(c) in region (II) (d) in region (I)
22. The electrical conductivity of a semiconductor increases when electromagnetic radiation of wavelength shorter than 2480 nm is incident on it. The band gap in (eV) for the semiconductor is
- (a) 2.5 eV (b) 1.1 eV (c) 0.7 eV (d) 0.5 eV
23. In an experiment with nPn transistor amplifier in common emitter configuration, the current gain of the transistor is 100. If the collector current changes by 1 mA, what will be the change in emitter current?
- (a) 1.1 mA (b) 1.01 mA (c) 0.01 mA (d) 10 mA
24. The following figure shows a logic gate circuit with two inputs A and B and the output C. The voltage waveforms of A, B and C are as shown below
- 
- The logic gate is
- (a) NAND gate (b) NOR gate  
(c) OR gate (d) AND gate
25. A zener diode of voltage  $V_Z (= 6\text{ V})$  is used to maintain a constant voltage across a load resistance  $R_L (= 1000 \Omega)$  by using a series resistance  $R_s (= 100 \Omega)$ . If the e.m.f. of source is  $E (= 9 \text{ V})$ , what is the power being dissipated in Zener diode?
- (a) 0.144 watt (b) 0.324 watt  
(c) 0.244 watt (d) 0.544 watt
26. The I-V characteristic of a P-N junction diode is shown below. The approximate dynamic resistance of the p-n junction when a forward bias of 2 volt is applied is
- 
- (a)  $1 \Omega$  (b)  $0.25 \Omega$  (c)  $0.5 \Omega$  (d)  $5 \Omega$

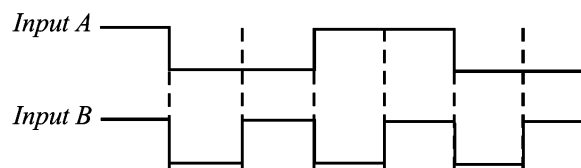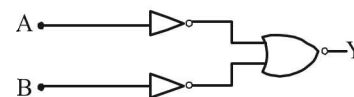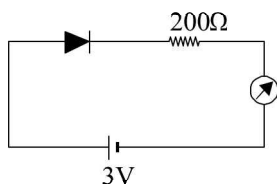
27. The current gain in the common emitter mode of a transistor is 10. The input impedance is  $20\text{ k}\Omega$  and output impedance is  $100\text{ k}\Omega$ . The power gain is  
(a) 300 (b) 500 (c) 200 (d) 100
28. A silicon diode has a threshold voltage of  $0.7\text{ V}$ . If an input voltage given by  $2\sin(\pi t)$  is supplied to a half wave rectifier circuit using this diode, the rectified output has a peak value of  
(a)  $2\text{ V}$  (b)  $1.4\text{ V}$  (c)  $1.3\text{ V}$  (d)  $0.7\text{ V}$
29. A working transistor with its three legs marked  $P$ ,  $Q$  and  $R$  is tested using a multimeter. No conduction is found between  $P$  and  $Q$ . By connecting the common (negative) terminal of the multimeter to  $R$  and the other (positive) terminal to  $P$  or  $Q$ , some resistance is seen on the multimeter. Which of the following is true for the transistor?  
(a) It is an npn transistor with  $R$  as base  
(b) It is a pnp transistor with  $R$  as collector  
(c) It is a pnp transistor with  $R$  as emitter  
(d) None of these
30. When germanium is doped 1 part in a million with indium, its conductivity increases by a factor of about  
(a) 10 (b)  $10^3$  (c)  $10^5$  (d)  $10^6$
31. The depletion layer in the p-n junction region is caused by  
(a) drift of holes  
(b) diffusion of charge carriers  
(c) migration of impurity ions  
(d) drift of electrons
32. A change of  $8.0\text{ mA}$  in the emitter current bring a change of  $7.9\text{ mA}$  in the collector current. The values of  $\alpha$  and  $\beta$  are  
(a) 0.99, 90 (b) 0.96, 79 (c) 0.97, 99 (d) 0.99, 79
33. The current gain  $\alpha$  of transistor in common base mode is 0.995. Its current gain  $\beta$  in the common emitter mode is  
(a) 199 (b) 90.5 (c) 100 (d) 1.005
34. When a p-n junction diode is reverse biased the flow of current across the junction is mainly due to  
(a) diffusion of charges  
(b) drift of charges  
(c) depends on the nature of material  
(d) both drift and diffusion of charges.
35. The reading of the ammeter for a silicon diode in the given circuit is :  
(a) 0 (b)  $15\text{ mA}$  (c)  $11.5\text{ mA}$  (d)  $13.5\text{ mA}$
36. The logic circuit shown below has the input waveforms 'A' and 'B' as shown. Pick out the correct output waveform.



Output is

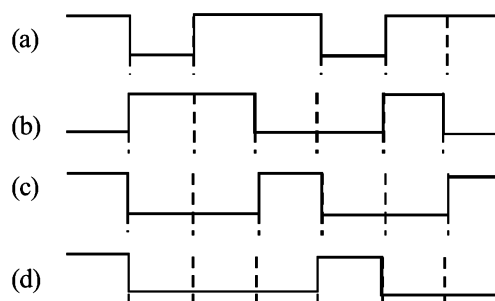


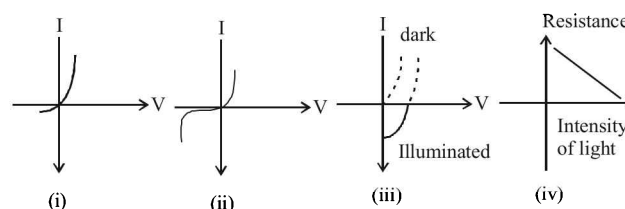37. In a transistor the base is  
(a) an insulator  
(b) a conductor of low resistance  
(c) a conductor of high resistance  
(d) an extrinsic semiconductor
38. Identify the semiconductor devices whose characteristics are given below, in the order (i), (ii), (iii), (iv) :




- (a) Solar cell, Light dependent resistance, Zener diode, simple diode  
(b) Zener diode, Solar cell, simple diode, Light dependent resistance  
(c) Simple diode, Zener diode, Solar cell, Light dependent resistance  
(d) Zener diode, Simple diode, Light dependent resistance, Solar cell
39. Pure Si at  $500\text{ K}$  has equal number of electron ( $n_e$ ) and hole ( $n_h$ ) concentrations of  $1.5 \times 10^{16}\text{ m}^{-3}$ . Doping by indium increases  $n_h$  to  $4.5 \times 10^{22}\text{ m}^{-3}$ . The doped semiconductor is of  
(a) n-type with electron concentration  $n_e = 5 \times 10^{22}\text{ m}^{-3}$   
(b) p-type with electron concentration  $n_e = 2.5 \times 10^{10}\text{ m}^{-3}$   
(c) n-type with electron concentration  $n_e = 2.5 \times 10^{23}\text{ m}^{-3}$   
(d) p-type having electron concentration  $n_e = 5 \times 10^9\text{ m}^{-3}$

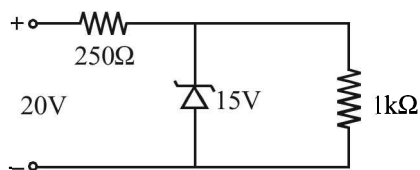40. A zener diode, having breakdown voltage equal to 15V, is used in a voltage regulator circuit shown in figure. The current through the diode is




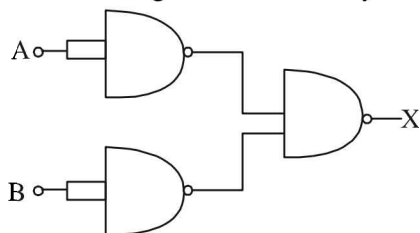- (a) 10mA (b) 15mA (c) 20mA (d) 5mA
41. Transistor working as an amplifier operates in its active region of characteristics only when
- (a) the emitter junction is forward biased and the collector junction is reverse biased
- (b) the emitter junction is reverse biased
- (c) the collector junction is forward biased
- (d) the emitter junction is reverse biased and the collector junction is forward biased
42. The input resistance of a silicon transistor is  $100\ \Omega$ . Base current is changed by  $40\ \mu\text{A}$  which results in a change in collector current by 2 mA. This transistor is used as a common emitter amplifier with a load resistance of  $4\ \text{k}\Omega$ . The voltage gain of the amplifier is
- (a) 2000 (b) 3000 (c) 4000 (d) 1000
43. If a small amount of antimony is added to germanium crystal
- (a) it becomes a p-type semiconductor
- (b) the antimony becomes an acceptor atom
- (c) there will be more free electrons than holes in the semiconductor
- (d) its resistance is increased
44. In a CE transistor amplifier, the audio signal voltage across the collector resistance of  $2\ \text{k}\Omega$  is 2V. If the base resistance is  $1\ \text{k}\Omega$  and the current amplification of the transistor is 100, the input signal voltage is
- (a) 0.1V (b) 1.0V (c) 1mV (d) 10 mV
45. The combination of gates shown below yields







- (a) OR gate (b) NOT gate
- (c) XOR gate (d) NAND gate
46. Which one of the following statement is false ?
- (a) Pure Si doped with trivalent impurities gives a p-type semiconductor
- (b) Majority carriers in a n-type semiconductor are holes
- (c) Minority carriers in a p-type semiconductor are electrons
- (d) The resistance of intrinsic semiconductor decreases with increase of temperature

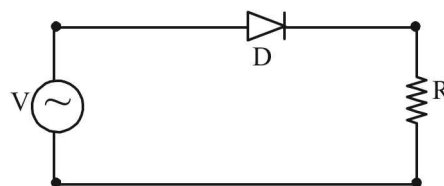
47. A p-n junction (D) shown in the figure can act as a rectifier. An alternating current source (V) is connected in the circuit.



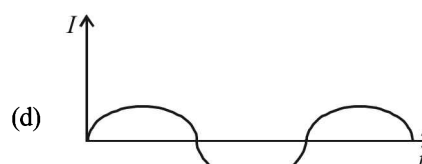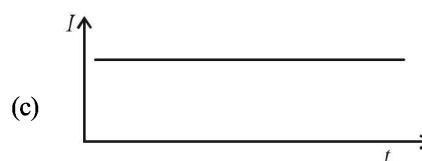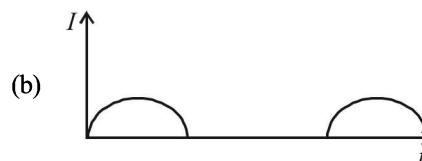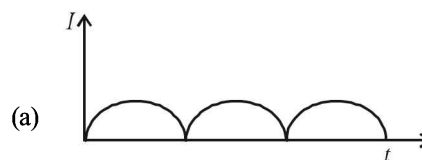The current ( $I$ ) in the resistor ( $R$ ) can be shown by :




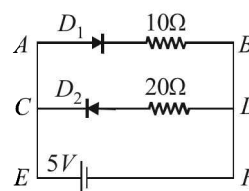48. Two ideal diodes are connected to a battery as shown in the circuit. The current supplied by the battery is



- (a) 0.75 A (b) zero (c) 0.25 A (d) 0.5 A
49. The barrier potential of a p-n junction depends on:
- (A) type of semi conductor material
- (B) amount of doping
- (C) temperature
- Which one of the following is correct ?
- (a) (A) and (B) only (b) (B) only
- (c) (B) and (C) only (d) (A), (B) and (C)

50. The I-V characteristic of an LED is

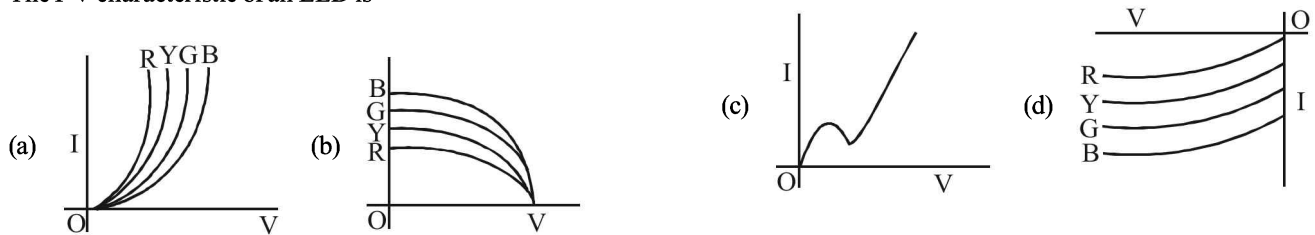

## Skill Based MCQs


51. The concentration of hole - electron pairs in pure silicon at  $T = 300 \text{ K}$  is  $7 \times 10^{15}$  per cubic meter. Antimony is doped into silicon in a proportion of 1 atom in  $10^7$  Si atoms. Assuming that half of the impurity atoms contribute electron in the conduction band, calculate the factor by which the number of charge carriers increases due to doping. The number of silicon atoms per cubic meter is  $5 \times 10^{28}$

- (a)  $2.8 \times 10^5$  (b)  $3.1 \times 10^2$   
(c)  $4.2 \times 10^5$  (d)  $1.8 \times 10^5$

52. A sinusoidal voltage of amplitude 25 volt and frequency 50Hz is applied to a half wave rectifier using P-n junction diode. No filter is used and the load resistor is  $1000\Omega$ . The forward resistance  $R_f$  of ideal diode is  $10\Omega$ . The percentage rectifier efficiency is


- (a) 40% (b) 20% (c) 30% (d) 15%

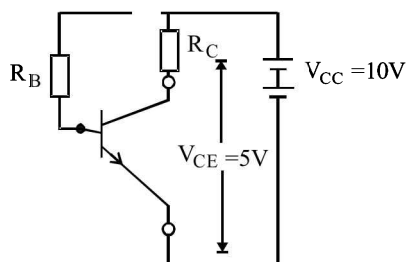53. A transistor connected in common emitter configuration has input resistance  $R_B = 2 \text{ k}\Omega$  and load resistance of  $5 \text{ k}\Omega$ . If  $\beta = 60$  and an input signal  $12 \text{ mV}$  is applied, calculate the voltage gain, the power gain and the value of output voltage




- (a)  $A_v = 150$ ,  $V_{out} = 1.8 \text{ V}$ , and power gain = 9000  
(b)  $A_v = 20$ ,  $V_{out} = 1 \text{ V}$ , and power gain = 2000  
(c)  $A_v = 150$ ,  $V_{out} = 1.5 \text{ V}$ , and power gain = 8500  
(d)  $A_v = 20$ ,  $V_{out} = 1.5 \text{ V}$ , and power gain = 2000

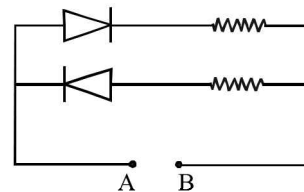54. A  $2 \text{ V}$  battery is connected across the points A and B as shown in the figure given below. Assuming that the resistance of each diode is zero in forward bias, and infinity in reverse bias, the current supplied by the battery when its positive terminal is connected to A, is



- (a)  $0.2 \text{ A}$  (b)  $0.4 \text{ A}$  (c) zero (d)  $0.1 \text{ A}$

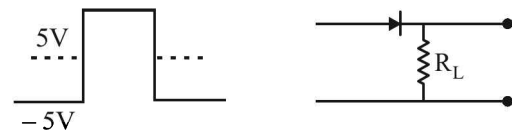55. In a p-n junction diode, a square input signal of  $10 \text{ V}$  is applied as shown in fig.




The output signal across  $R_L$  will be

- (a) (b)   
(c) (d)

56. Within depletion region of p-n junction diode

- (a) p-side is positive and n-side is negative  
(b) p-side is negative and n-side is positive  
(c) both sides are positive or both negative  
(d) both sides are neutral

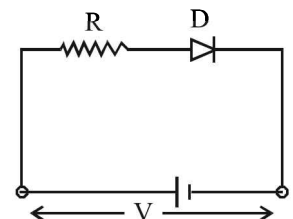57. A d.c. battery of  $V$  volt is connected to a series combination of a resistor  $R$  and an ideal diode  $D$  as shown in the figure below. The potential difference across  $R$  will be




- (a)  $2V$  when diode is forward biased  
(b) Zero when diode is forward biased  
(c)  $V$  when diode is reverse biased  
(d)  $V$  when diode is forward biased

58. The input signal given to a CE amplifier having a voltage gain of 150 is  $V_i = 2 \cos \left( 15t + \frac{\pi}{3} \right)$ . The corresponding output signal will be :

(a)  $75 \cos \left( 15t + \frac{2\pi}{3} \right)$  (b)  $2 \cos \left( 15t + \frac{5\pi}{6} \right)$   
 (c)  $300 \cos \left( 15t + \frac{4\pi}{3} \right)$  (d)  $300 \cos \left( 15t + \frac{\pi}{3} \right)$

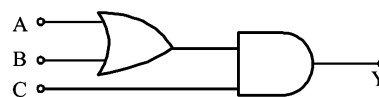59. To get output 1 for the following circuit, the correct choice for the input is



- (a)  $A=0, B=1, C=0$  (b)  $A=1, B=0, C=0$   
 (c)  $A=1, B=1, C=0$  (d)  $A=1, B=0, C=1$
60. A npn transistor is connected in common emitter configuration in a given amplifier. A load resistance of  $800 \Omega$  is connected in the collector circuit and the voltage drop across it is  $0.8 \text{ V}$ . If the current amplification factor is  $0.96$  and the input resistance of the circuit is  $192 \Omega$ , the voltage gain and the power gain of the amplifier will respectively be
- (a) 4, 3.84 (b) 3.69, 3.84 (c) 4, 4 (d) 4, 3.69

## ANSWER KEY

## Conceptual MCQs

1	(b)	3	(d)	5	(a)	7	(c)	9	(a)	11	(a)	13	(c)	15	(a)				
2	(d)	4	(c)	6	(b)	8	(c)	10	(d)	12	(d)	14	(b)						

## Application Based MCQs

16	(c)	20	(b)	24	(d)	28	(c)	32	(d)	36	(d)	40	(d)	44	(d)	48	(d)		
17	(a)	21	(b)	25	(a)	29	(d)	33	(a)	37	(d)	41	(a)	45	(a)	49	(d)		
18	(a)	22	(d)	26	(b)	30	(d)	34	(b)	38	(c)	42	(a)	46	(b)	50	(a)		
19	(c)	23	(b)	27	(b)	31	(b)	35	(c)	39	(d)	43	(c)	47	(b)				

## Skill Based MCQs

51	(d)	52	(a)	53	(a)	54	(a)	55	(b)	56	(b)	57	(b)	58	(c)	59	(d)	60	(a)
----	-----	----	-----	----	-----	----	-----	----	-----	----	-----	----	-----	----	-----	----	-----	----	-----