

Lecture - 13

Four cases of complete mismatch on a line ($|\Gamma| = 1$):

Case - (1):

$$Z_L = jR_0 = \text{Inductive load}$$

$$Z_0 = R_0 = \text{lossless line}$$

$$|\Gamma| = 1$$

$$V_f \rightarrow \sin$$

$$V_r \rightarrow \cos$$

$$\Gamma = \frac{jR_0 - R_0}{jR_0 + R_0} = \frac{j-1}{j+1}$$

$$= \frac{\sqrt{2} \angle 135^\circ}{\sqrt{2} \angle 45^\circ}$$

$$= 1 \angle 90^\circ = j$$

Case-(II):-

$$Z_L = -jR_0 = \text{capacitive load}$$

$$Z_0 = R_0 = \text{lossless line}$$

$$\Gamma = \frac{-jR_0 - R_0}{-jR_0 + R_0} = \frac{-j-1}{-j+1}$$

$$= \frac{\sqrt{2} \angle 45^\circ}{\sqrt{2} \angle 135^\circ} = -j$$

Note:-

Real Power dissipation in any resistive load is always zero.

Case-(III):-

$$Z_L = 0 \Rightarrow \text{S.C load}$$

$$Z_0 = R_0 = \text{lossless line}$$

$$\Gamma = \frac{0 - Z_0}{0 + Z_0} = -1 = 1 \angle 180^\circ$$

$$V_f + V_r = 0$$

$$V_f \rightarrow \sin$$

$$V_r = -\sin$$

Voltage at S.C is always zero

Case-(IV):-

$$Z_L = \infty \Rightarrow \text{O.C load}$$

$$Z_0 = R_0 = \text{lossless line}$$

$$\Gamma = \frac{1 - Z_0/Z_L}{1 + Z_0/Z_L} = 1 \angle 0$$

$$V_f + V_r = V_{\max}$$


Voltage at O.C is always maximum

$$|\Gamma| = 1$$

$$V_f \rightarrow \sin$$

$$V_r = \sin$$

Standing Wave and SWR:-

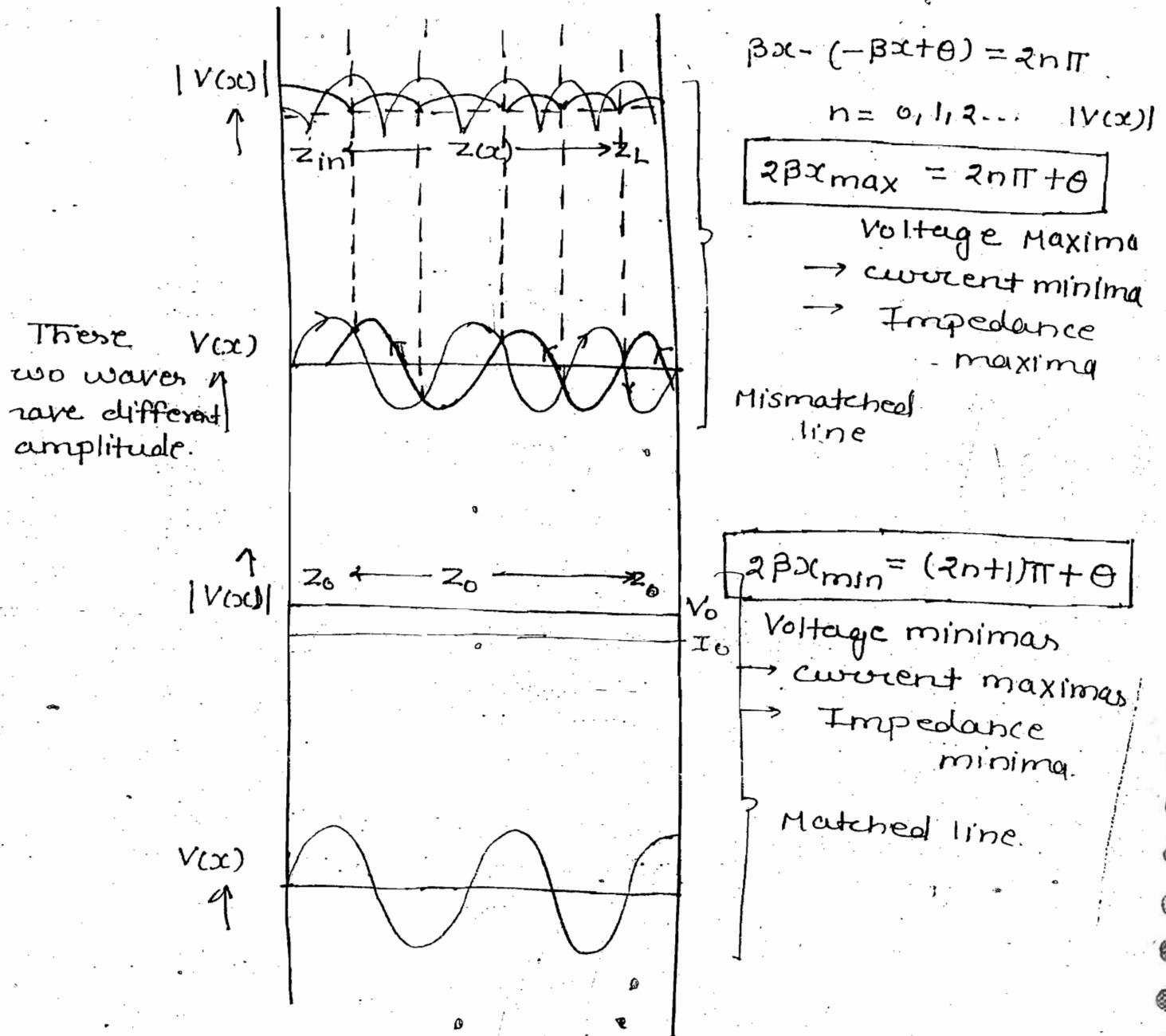

$$V(x) = V_0 e^{j\beta x} + V_0 |\Gamma| e^{j\theta} e^{-j\beta x}$$

$$= V_0 e^{j\beta x} + V_0 |\Gamma| e^{j(-\beta x + \theta)}$$

The magnitude plot of a single harmonic matched line as a constant value straight line graph. The magnitude plot of two harmonics mismatched line as shown below:-

$$|V(x)| = V_{max} = V_0 + V_0 |\Gamma| \text{ when they are inphase}$$

$$\beta x - (-\beta x + \theta) = 2n\pi$$

$$|V(x)|$$

$n = 0, 1, 2$

$$2\beta x_{\max} = 2n\pi + \theta$$

Voltage Maxima Positions

$$|V(x)| = V_{\min} = V_0 - V_0 |\Gamma| \text{ when they are out of phase}$$

$$2\beta x_{\min} = (2n+1)\pi + \theta$$

→ Voltage Minima

→ The magnitude plot of two harmonics travelling in opposite direction having periodic interference results in addition and cancellation leading to standing wave formation

Note 1:-

The current also has identical standing wave pattern with the voltage maxima coincide with current minima

Note 2:-

As the impedance is different at different point on line voltage and current distribution is also extremely spread on the line such that

$$Z_{\max} = \frac{V_{\max}}{I_{\min}}$$

$$Z_{\min} = \frac{V_{\min}}{I_{\max}}$$

Note 3:-

$$\left. \begin{array}{l} \beta x = \frac{2\pi}{\lambda} x \rightarrow \text{Periodic} - 2\pi \\ x \rightarrow \text{Periodic} - \lambda \end{array} \right\} \text{ Harmonic}$$

$$\left. \begin{array}{l} 2\beta x = \frac{2\pi}{\lambda/2} x \rightarrow \text{Periodic} - 2\pi \\ x \rightarrow \text{Periodic} - \lambda/2 \end{array} \right\} \text{ Standing wave}$$

Maxima to Maxima distance on standing wave is $\lambda/2$

Standing Wave Ratio (SWR):-

It can be VSWR or CSWR

$$= \frac{V_{\max}}{V_{\min}} \text{ or } \frac{I_{\max}}{I_{\min}}$$


$$\boxed{\text{SWR} = \frac{V_0 + V_0 |\Gamma|}{V_0 - V_0 |\Gamma|} = \frac{1 + |\Gamma|}{1 - |\Gamma|}}$$

$$0 \leq |\Gamma| \leq 1$$

$$\boxed{1 \leq \text{SWR} < \infty}$$

Matched
line

Complete Mismatch

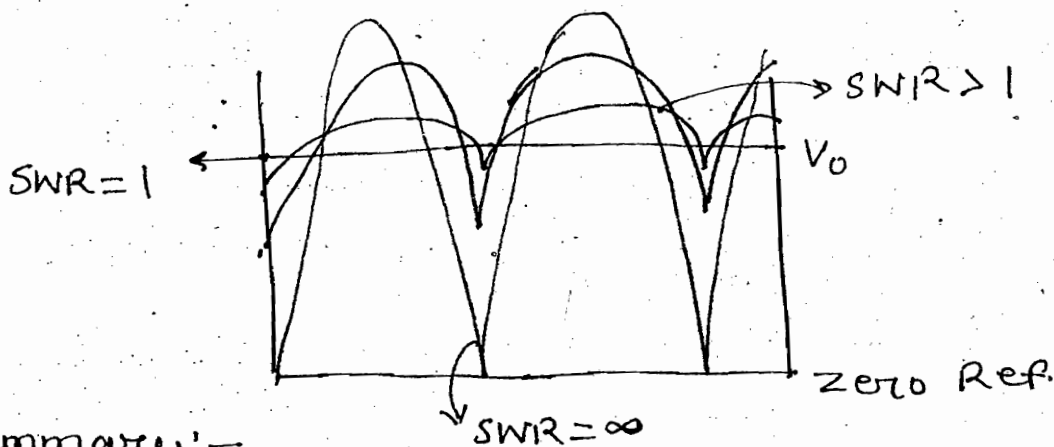

Summary:-

$$\left. \begin{array}{l} Z_0 \downarrow \uparrow \\ V_0 \uparrow \downarrow \\ I_0 \uparrow \downarrow \end{array} \right\} \text{SWR}$$

$$\begin{aligned} Z_{\max} &= \frac{V_{\max}}{I_{\min}} \\ &= \frac{V_0 + V_0 |\Gamma|}{I_0 - I_0 |\Gamma|} \end{aligned}$$

SWR is a measure of mismatch on the line

$$Z_{\max} = Z_0 \cdot \text{SWR}$$

$$Z_{\min} = Z_0 / \text{SWR}$$

$$ESWR = 5 = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$|\Gamma| = \frac{5-1}{5+1} = \frac{2}{3}$$

$$\Gamma = \frac{n_2 - n_1}{n_2 + n_1} = \frac{2}{3} \angle \theta = \pm \frac{2}{3}$$

$$n_2 + n_1 \rightarrow 120\pi \text{ (real)}$$

$$\frac{120\pi}{\sqrt{\epsilon_r}} \text{ (real)}$$

$$\text{As } n_2 < n_1$$


$$\Gamma = -\frac{2}{3} = \frac{n_2 - 120\pi}{n_2 + 120\pi} \Rightarrow n_2 = 24\pi$$

$$VSWR = 4$$

$$|\Gamma| = \frac{4-1}{4+1} = \frac{3}{5}$$

$$\Gamma = \frac{Z_L - 50}{Z_L + 50} = \frac{3}{5} \angle \theta = \pm \frac{3}{5}$$

$$\text{real} \rightarrow \text{real}$$

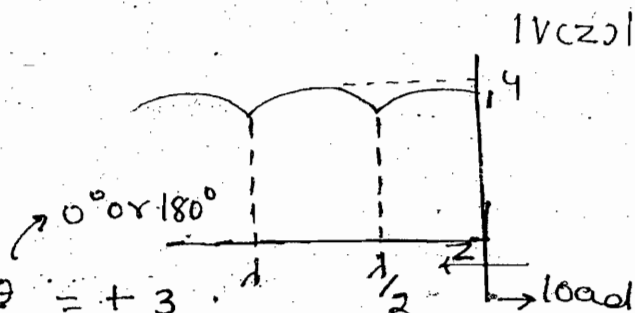

V_{min} is exactly at the load, Z_{min} is at the load

$$Z_L < Z_0$$

$\Rightarrow \Gamma$ is negative

$$\Gamma = -\frac{3}{5} = \frac{Z_L - 50}{Z_L + 50} \Rightarrow Z_L = 12.5\Omega$$

1st voltage maxima occurs at $\lambda/4$

$$2 \cdot \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = 2n\pi + \theta$$

$$\Rightarrow \theta = \pi$$

1 Note:-

2 $\rightarrow$ If Z_L, Z_0 are real
3 $Z_L > Z_0$

4 Γ is real & positive

5 Γ 's phase is 0

6 $2\beta x_{\max} = 2n\pi + 0 \Rightarrow x_{\max} = 0$

7 First voltage maxima exactly occurs

8 eg:- OC line where $\Gamma = +1$

9 $\rightarrow$ If Z_L, Z_0 are real

10 $Z_L < Z_0$

11 Γ is real and negative

12 First voltage minima exactly occurs

13 eg:- SC line where $\Gamma = -1$

14 $\rightarrow$

15
$$VSWR = \frac{1 + \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|}{1 - \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|}$$

16 If Z_L, Z_0 are real & $Z_L > Z_0$

17
$$VSWR = \frac{1 + \frac{Z_L - Z_0}{Z_L + Z_0}}{1 - \frac{Z_L - Z_0}{Z_L + Z_0}}$$

18
$$VSWR = \frac{Z_L}{Z_0}$$

19 If Z_L, Z_0 are real

20 $Z_L < Z_0$

21 $VSWR = ?$

24.

$$\Gamma(\lambda/8) = ?$$

$$\Gamma \text{ at load} = 0.6 \angle 60^\circ$$

$$\Gamma(x) = \frac{Z(x) - Z_0}{Z(x) + Z_0} = \frac{Z_L - Z_0}{Z_L + Z_0} e^{-j2\beta x}$$

$$\Gamma(\lambda/8) = \Gamma(0) e^{-j2\beta \cdot \frac{\lambda}{8}}$$

$$= 0.6 e^{j60} e^{-j2 \cdot \frac{2\pi}{\lambda} \cdot \frac{\lambda}{8}}$$

$$= 0.6 e^{j60} e^{-j90}$$

$$= 0.6 \angle -30^\circ$$


18+
← 17
7cm
h=0

25.

30V D.C Battery


D.C Transients

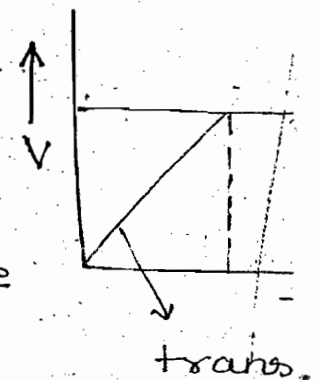During the transient state even DC has time variations and all AC fundamentals are applicable



$$V_f + V_r = \text{Adding}$$
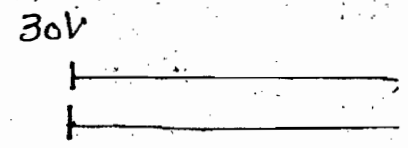
$$\Gamma = \frac{10}{30} = \frac{Z_L - 50}{Z_L + 50}$$



$$\Rightarrow Z_L = 100 \Omega$$

$$V_f =$$

$$V_r$$

$$I_L = \frac{30}{Z_L}$$

(Steady state)

$$= \frac{30}{100}$$

$$= 0.3 \text{ Amp.}$$

n=0


2.2

26.

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$= \frac{\sqrt{17} + 1}{\sqrt{17} - 1}$$

$$= 1.63$$

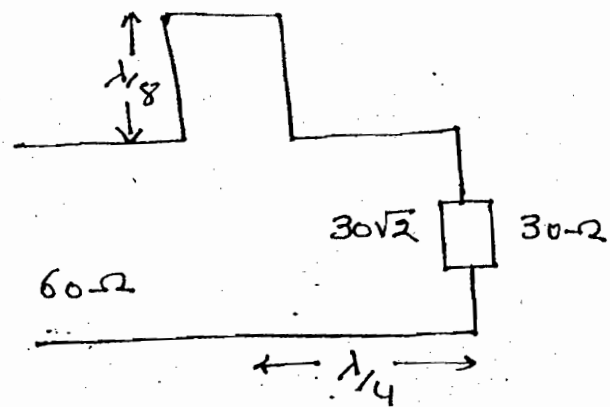

$$Z_{L1} = Z_{in2} + Z_{in3}$$

$$= 60 + j30 \Omega$$

$$Z_{in2} = j30 \Omega$$

$$Z_{in3} = \frac{(30\sqrt{2})^2}{30} = 60 \Omega$$

$$\Gamma = \frac{Z_{L1} - jZ_0}{Z_{L1} + jZ_0} = \frac{60 + j30 - 60}{60 + j80} = \frac{j}{j+4}$$

$$|\Gamma| = \frac{1}{\sqrt{17}}$$

27.

$$V_f = 25 \sin(\omega t - 75^\circ)$$

$$\Gamma = 0.6 \angle -30^\circ$$

$$V_r = ?$$

$$\frac{|V_r|}{|V_f|} = 0.6 \quad |V_r| = 15$$

$$V_r \text{ phase} = V_f \text{ phase} + \Gamma \text{ phase}$$

$$= -75^\circ - 30^\circ = -105^\circ$$

$$V_r = 15 \sin(-\omega t - 105^\circ)$$


28. V_f & V_r are inphase
and add up at centre

I_f & I_r cancel
at the centre

$$|I_f| = |I_r|$$

$$\Rightarrow I_{\min} = 0$$
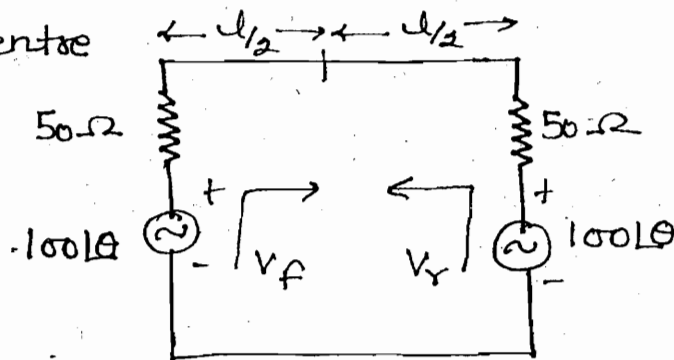
$$Z_{\max} = \frac{V_{\max}}{I_{\min}} = \infty$$



29. $VSWR = \frac{Z_L}{Z_0} = \frac{75}{50} = 1.5$

Smith Chart (Circle Diagrams):

→ It is used to calculate Γ and VSWR for a known Z_L & Z_0 .

$$\begin{aligned} \Gamma &= \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \end{aligned}$$

→ It is used normalised or relative ratio of Z_L/Z_0 for its calculation

→ It is a rectangular graph or polar plot of Γ_r vs Γ_i having two families of circles

→ constant R circles

where $R = \text{Real} [Z_L/Z_0]$

→ constant X circles.

$X = \text{Imag} [Z_L/Z_0]$

$$\Gamma_Y + j \Gamma_I = \frac{R + jX - 1}{R + jX + 1} = \frac{(R-1) + jX}{(R+1) + jX}$$

$$\left(\Gamma_Y - \frac{R}{R+1} \right)^2 + \Gamma_I^2 = \left(\frac{1}{R+1} \right)^2$$


Constant R circles
Equation.

$$(\Gamma_Y - 1)^2 + \left(\Gamma_I - \frac{1}{X} \right)^2 = \left(\frac{1}{X} \right)^2$$

constant X circles
Equation.

Properties of constant R circles:-

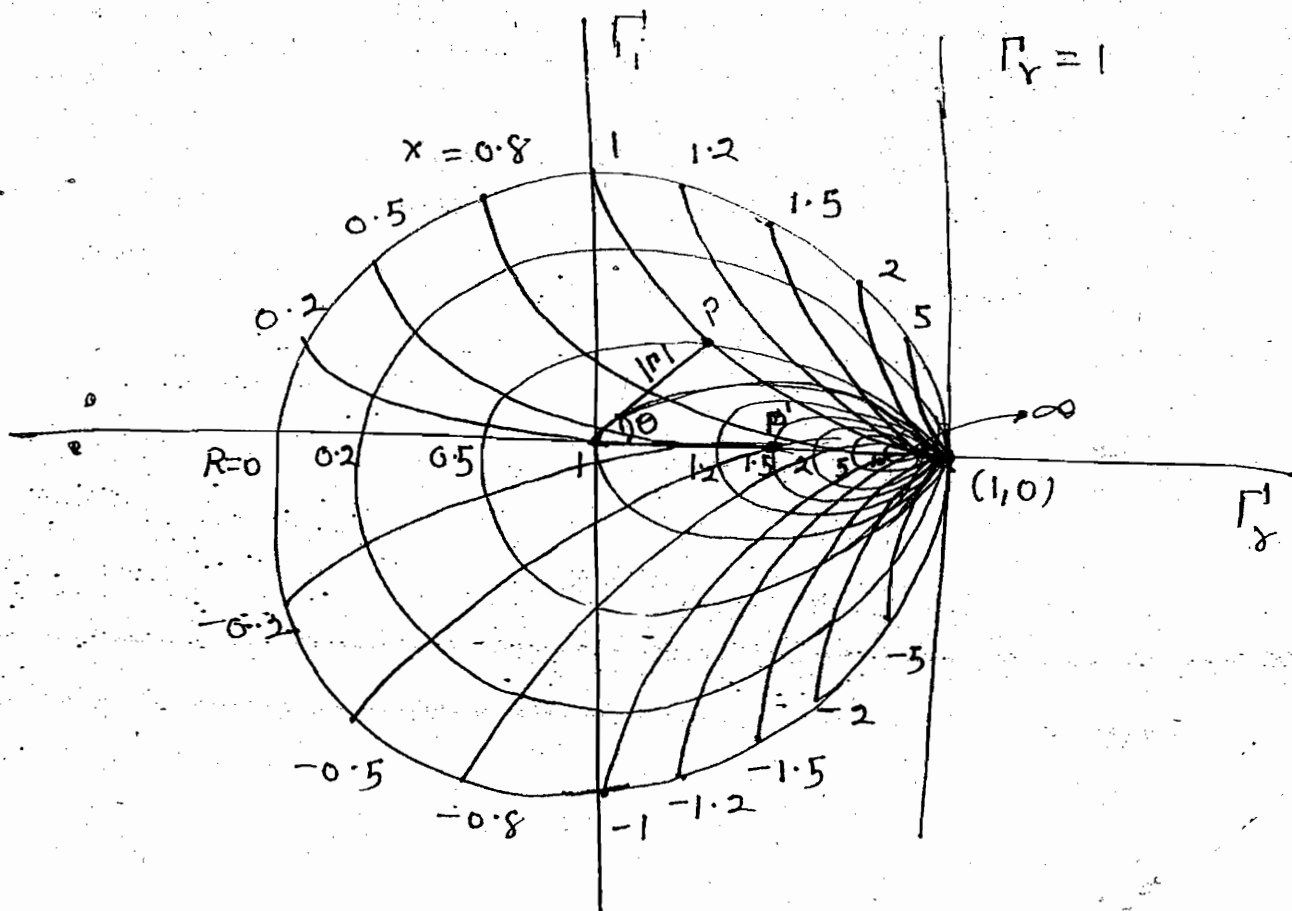- (a) Centres - $\left(\frac{R}{R+1}, 0 \right)$
- (b) Radius - $\left(\frac{1}{R+1} \right)$
- (c) They all pass through $(1, 0)$
- (d) Range $(0, \infty)$



1. The $R=0$ circle is the biggest possible R circle and it is periphery or boundary of Smith Chart.
2. All circles $R=0$ to 1 extend into the four quadrants the circles with $R>1$ confined in the Ist and IV quadrants
3. All the R -circles are concurrent with their centres on a straight line and have a common tangent $\Gamma_r = 1$ axis

Properties of constant X-circles:-

- a) Centres - $(1, \frac{1}{X})$ (b) Radius - $(\frac{1}{X})$
 - c) They all pass through $(1, 0)$
 - d) Range $(-\infty, \infty)$
1. $X=0$ circle is the biggest possible X circle and it is Γ_r axis
 2. All circles with $X=0$ to 1 extend into the first two quadrant but circles with $X>1$ confined in the 1st quadrant
 3. All the X -circles are concurrent and have a common tangent with Γ_r axis

Note:-



1. The centres of R circles lie on the common tangent of X -circle and vice-versa. Hence R and X constitute a pair of orthogonal families of circles.
2. A horizontal movement on the $X=0$ circle as R value increasing and a clockwise movement on the $R=0$ circle as X increasing inductively (trly)

Calculation of Γ :-

For a known Z_L and Z_0 calculate

$\frac{Z_L}{Z_0} = R + jX$ and locate the corresponding point of intersection of R and X circle

- Join the point P to origin the OP length = $|\Gamma|$
- OP segments inclination with Γ_r axis is Γ 's phase
- End

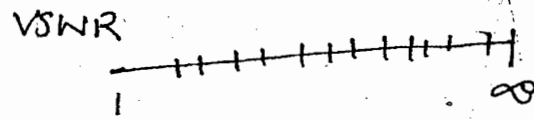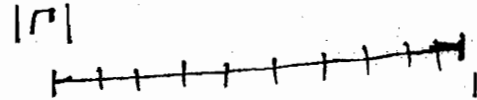

Calculation of VSWR :-

- For a known $|\Gamma|$ identify a point P' on the the $|\Gamma|$ real axis such that OP' length = $|\Gamma|$. The R circle value at P' is VSWR

$$\left. \begin{array}{l} R + jX \\ X = 0 \\ \Gamma_r \text{ axis} \end{array} \right| = \frac{Z_L}{Z_0} = \text{VSWR}$$

Identify following points on the Smith's Chart :-

(I) $Z_L = jR_0$, $Z_0 = R_0$

$$\frac{Z_L}{Z_0} = 0 + j1$$

$\downarrow$ $\downarrow$
R=0 X=1

$$\Gamma = j$$

(II) $Z_L = -jR_0$

$$Z_0 = R_0$$

bottom

(III)

$$Z_L = 0$$

$$Z_0 = R_0$$

$$\frac{Z_L}{Z_0} = 0 + j0$$

↓ ↓
R X

$$\Gamma = -1$$

Extremely left

(IV)

$$Z_L = \infty$$

$$Z_0 = R_0$$

Extremely right

(V)

$$Z_L = R_0$$

$$Z_0 = R_0$$

→ centre $\Gamma = 0$