

Speed Test-17

1. (b) $V = IR = (neAv_d)\rho \frac{\ell}{A}$

$$\therefore \rho = \frac{V}{V_d n e}$$

Here V = potential difference

ℓ = length of wire

n = no. of electrons per unit volume of conductor.

e = no. of electrons

Placing the value of above parameters we get resistivity

$$\rho = \frac{5}{8 \times 10^{28} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-4} \times 0.1}$$

$$= 1.6 \times 10^{-5} \Omega \text{m}$$

2. (d) From the curve it is clear that slopes at points A, B, C, D have following order $A > B > C > D$.

And also resistance at any point equals to slope of the $V-i$ curve.

So order of resistance at three points will be

$$R_A > R_B > R_C > R_D$$


3. (d) From the principle of potentiometer, $V \propto l$

$$\Rightarrow \frac{V}{E} = \frac{l}{L}; \text{ where}$$

V = emf of battery, E = emf of standard cell.

L = length of potentiometer wire

$$V = \frac{El}{L} = \frac{30E}{100}$$

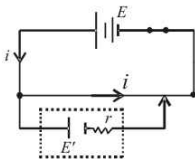

NOTE In this arrangement, the internal resistance of the battery E does not play any role as current is not passing through the battery.

4. (d) $R = \frac{\rho l}{\pi r^2}$. But $m = \pi r^2 l d \therefore \pi r^2 = \frac{m}{ld}$

$$\therefore R = \frac{\rho l^2 d}{m}, R_1 = \frac{\rho l_1^2 d}{m_1}, R_2 = \frac{\rho l_2^2 d}{m_2}$$

$$R_3 = \frac{\rho l_3^2 d}{m_3}$$

$$R_1 : R_2 : R_3 = \frac{l_1^2}{m_1} : \frac{l_2^2}{m_2} : \frac{l_3^2}{m_3}$$

$$R_1 : R_2 : R_3 = \frac{25}{1} : \frac{9}{3} : \frac{1}{5} = 125 : 15 : 1$$

5. (c) In series, $R_s = nR$

$$\text{In parallel, } \frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} + \dots n \text{ terms}$$

$$\therefore R_s/R_p = n^2/1 = n^2$$

6. (a) Efficiency is given by $\eta = \frac{\text{output}}{\text{input}}$

$$= \frac{5 \times 15 \times 14}{10 \times 8 \times 15} = 0.875 \text{ or } 87.5\%$$

7. (b) According to the condition of balancing

$$\frac{55}{20} = \frac{R}{80} \Rightarrow R = 220 \Omega$$

8. (a) $J = eE \Rightarrow J\rho = E$

J is current density, E is electric field

so $B = \rho = \text{resistivity}$.

9. (d) Kirchhoff's first law is based on conservation of charge and Kirchhoff's second law is based on conservation of energy.

10. (c) $R = \frac{\rho \ell}{A}$

When wire is cut into 4 pieces and connected in parallel.

$$R_{\text{eff}} = \frac{R}{16} \Rightarrow P_C = 16P$$


$$P_A : P_B : P_C : P_D = \frac{V^2}{R} : \frac{V^2}{R/4} : \frac{V^2}{R/16} : \frac{V^2}{R/2}$$

11. (b) $S = \frac{I_g R}{n I_g - I_g} \Rightarrow S = \frac{I_g}{(n-1)I_g} R$

12. (d) Resistance of a conductor, $R = \frac{m}{ne^2 \tau} \frac{l}{A}$

As the temperature increases, the relaxation time τ decreases because the number of collisions of electrons per second increases due to increase in thermal energy of electrons.

13. (b)

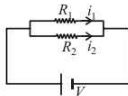

$$R_1 = \frac{\rho \ell_1}{\pi r_1^2}; R_2 = \frac{\rho \ell_2}{\pi r_2^2}$$

$$i_1 R_1 = i_2 R_2 \text{ (same potential difference)}$$

$$\therefore \frac{i_1}{i_2} = \frac{R_2}{R_1} = \frac{\ell_2}{\ell_1} \times \frac{r_1^2}{r_2^2} = \frac{3}{4} \times \frac{4}{9} = \frac{1}{3}$$


14. (c) $\frac{R_1}{R_2} = \frac{\ell_1}{\ell_2}$ where $\ell_2 = 100 - \ell_1$

In the first case $\frac{X}{Y} = \frac{20}{80}$

In the second case

$$\frac{4X}{Y} = \frac{\ell}{100 - \ell} \Rightarrow \ell = 50$$

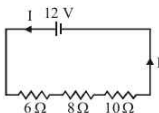15. (c) Before connecting E, the circuit diagram is



Then, $R_{eq} = 6 \Omega + 8 \Omega + 10 \Omega = 24 \Omega$

Current in the 8Ω resistance, $I = \frac{12V}{24\Omega} = \frac{1}{2} A$

After connecting E, the current through 8Ω is

$$I = \frac{1}{2} A$$

$$\therefore E = \frac{1}{2} A \times 8 \Omega = 4V$$

16. (d) By junction rule at point B
 $-I + 1A + 2A = 0$
 So, $I = 3A$
 By Loop rule,
 $-3 \times 2 - 1 \times 1 - E + 12 = 0$
 $E = 5V$


17. (d) Resistance of bulb $R_b = \frac{(1.5)^2}{4.5} = 0.5 \Omega$

Current drawn from battery $= \frac{E}{2.67 + 0.33} = \frac{E}{3}$

Share of bulb $= \frac{2}{3} \times \frac{E}{3} = \frac{2E}{9}$

$$\therefore \left(\frac{2E}{9}\right)^2 \times 0.5 = 4.5 \text{ or } E = 13.5V$$

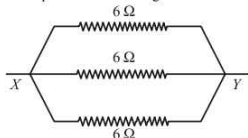18. (d) The equivalent circuit is given below :



The equivalent resistance is given by

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{6} + \frac{1}{6} = \frac{3}{6} = \frac{1}{2}$$

$$\Rightarrow R_{eq} = 2 \Omega$$

19. (a) Since average drift velocity $= \frac{1}{2} \frac{eE}{m} \times (\tau)$
 Now $I = NeA \times (\text{avg. drift velocity})$

$$= \frac{Ne^2 AE}{2m\ell} \times \tau = \frac{Ne^2 A V}{2m\ell} \times \tau$$


$$R = \frac{V}{I} = \frac{2m\ell}{Ne^2 A \tau}, \text{ where } N \text{ is electron density.}$$

20. (c) The current through the resistance R

$$I = \left(\frac{\varepsilon}{R + r} \right)$$


The potential difference across R
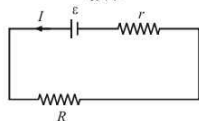
$$V = IR = \left(\frac{\varepsilon}{R + r} \right) R$$



$$V = \left(\frac{\varepsilon}{1 + \frac{r}{R}} \right)$$

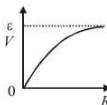when $R = 0$, $V = 0$,
 $R = \infty$, $V = \varepsilon$



Thus V increases as R increases upto certain limit, but it does not increase further.

21. (c) Resistance of bulb is constant

$$P = \frac{V^2}{R} \Rightarrow \frac{\Delta p}{p} = \frac{2\Delta V}{V} + \frac{\Delta R}{R}$$

$$\frac{\Delta p}{p} = 2 \times 2.5 + 0 = 5\%$$

22. (a) Potential gradient = Potential fall per unit length. In this case resistance of unit length.

$$R = \frac{\rho l}{A} = \frac{10^{-7} \times 1}{10^{-6}} = 10^{-1} \Omega$$

Potential fall across R is

$$V = I.R = 0.1 \times 10^{-1} = 0.01 \text{ volt/m.}$$

$$= 10^{-2} \text{ volt / m}$$

23. (d) $R_1 + R_2 = \text{Constant}$, R_1 will increase, R_2 will decrease.
 $R_1 \alpha \Delta T - R_2 \beta \Delta T = 0 \Rightarrow R_1 \alpha \Delta T = R_2 \beta \Delta T$

$$\therefore \frac{R_1}{R_2} = \frac{\beta}{\alpha}$$

24. (d) Given : Number of cells, $n = 5$, emf of each cell = E

Internal resistance of each cell = r

In series, current through resistance R

$$I = \frac{nE}{nr + R} = \frac{5E}{5r + R}$$

In parallel, current through resistance R

$$I' = \frac{E}{\frac{r}{n} + R} = \frac{nE}{r + nR} = \frac{5E}{r + 5R}$$

According to question, $I = I'$

$$\therefore \frac{5E}{5r + 5R} = \frac{5E}{r + 5R} \Rightarrow 5r + R = r + 5R$$

$$\text{or } R = r \quad \therefore \frac{R}{r} = 1$$

25. (d) The total volume remains the same before and after stretching.

Therefore $A \times \ell = A' \times \ell'$

Here $\ell' = 2\ell$

$$\therefore A' = \frac{A \times \ell}{\ell'} = \frac{A \times \ell}{2\ell} = \frac{A}{2}$$

Percentage change in resistance

$$\begin{aligned} &= \frac{R_f - R_i}{R_i} \times 100 = \frac{\rho \left(\frac{\ell'}{A'} \times \frac{\ell}{A} \right)}{\frac{\rho \ell}{A}} \times 100 \\ &= \left[\left(\frac{\ell'}{A'} \times \frac{A}{\ell} \right) - 1 \right] \times 100 = \left[\left(\frac{2\ell}{\frac{A}{2}} \times \frac{A}{\ell} \right) - 1 \right] \times 100 \\ &= 300\% \end{aligned}$$

26. (a) Pot. gradient = 0.2 mV/cm

$$= \frac{0.2 \times 10^{-3}}{10^{-2}} = 2 \times 10^{-2} \text{ V/m}$$


Emf of cell = $2 \times 10^{-2} \times 1 \text{ m} = 2 \times 10^{-2} \text{ V} = 0.02 \text{ V}$

As per the condition of potentiometer

$0.02 (R + 490) = 2 (R)$ or $1.98 R = 9.8$

$$\Rightarrow R = \frac{9.8}{1.98} = 4.9 \Omega$$

27. (d)

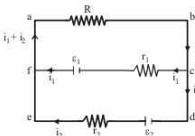

Applying Kirchhoff's rule in loop **abefa**

$$E_1 - (i_1 + i_2)R - i_1 r_1 = 0.$$

28. (c) Total power consumed by electrical appliances in the building, $P_{\text{total}} = 2500 \text{ W}$


$$\text{Watt} = \text{Volt} \times \text{ampere}$$

$$\Rightarrow 2500 = V \times I \Rightarrow 2500 = 220 I$$

$$\Rightarrow I = \frac{2500}{220} = 11.36 \approx 12 \text{ A}$$

(Minimum capacity of main fuse)

29. (a)

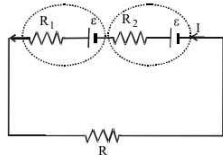

$$I = \frac{2E}{R + R_1 + R_2}$$

Potential difference across second cell

$$= V = E - iR_2 = 0$$

$$E - \frac{2E}{R + R_1 + R_2} \cdot R_2 = 0$$

$$R + R_1 + R_2 - 2R_2 = 0$$

$$R + R_1 - R_2 = 0$$

$$\therefore R = R_2 - R_1$$

30. (c)



Resistance of the series combination,

$$S = R_1 + R_2$$

Resistance of the parallel combination,

$$P = \frac{R_1 R_2}{R_1 + R_2}$$

$$S = nP \Rightarrow R_1 + R_2 = \frac{n(R_1 R_2)}{(R_1 + R_2)}$$

$$\Rightarrow (R_1 + R_2)^2 = n R_1 R_2$$

Minimum value of n is 4 for that

$$(R_1 + R_2)^2 = 4 R_1 R_2 \Rightarrow (R_1 - R_2)^2 = 0$$

31. (c) To convert a galvanometer into a voltmeter we connect a high resistance in series with the galvanometer.

The same procedure needs to be done if ammeter is to be used as a voltmeter.

32. (c)

Given, emf of cell $E = 200 \text{ V}$

Internal resistance of cells = 1Ω

D. C. main supply voltage $V = 220 \text{ V}$

External resistance $R = ?$

$$r = \left(\frac{E - V}{V} \right) R$$

$$1 = \left(\frac{20}{220} \right) \times R$$

$$\therefore R = 11 \Omega.$$

33. (a) In steady state, flow of current through capacitor will be zero.

Current through the circuit,

$$i = \frac{E}{r + r_2}$$

Potential difference through capacitor

$$V_c = \frac{Q}{C} = E - ir = E - \left(\frac{E}{r + r_2} \right) r$$

$$\therefore Q = CE \frac{r_2}{r + r_2}$$

34. (c) $i = neAV_d$ and $V_d \propto \sqrt{E}$ (Given)

or, $i \propto \sqrt{E}$

$$i^2 \propto E$$

$$i^2 \propto V$$

Hence graph (c) correctly depicts the V - I graph for a wire made of such type of material.

35. (b) Current, $I = (2.9 \times 10^{18} + 1.2 \times 10^{18}) \times 1.6 \times 10^{-19}$
 $= 0.66 \text{ A}$ towards right.

36. (a) Copper rod and iron rod are joined in series.

$$\therefore R = R_{Cu} + R_{Fe} = (\rho_1 + \rho_2) \frac{\ell}{A}$$

$$\left(\because R = \rho \frac{\ell}{A} \right)$$

From ohm's law $V = RI$

$$= (1.7 \times 10^{-6} \times 10^{-2} + 10^{-5} \times 10^{-2}) \div 0.01 \times 10^{-4} \text{ volt}$$

$$= 0.117 \text{ volt } (\because I = 1 \text{ A})$$

37. (d) $I = \frac{E}{R + r}$, Internal resistance (r) is

$$\text{zero, } I = \frac{E}{R} = \text{constant.}$$

38. (b) $R_t = R_0 (1 + \alpha t)$

Initially, $R_0 (1 + 30\alpha) = 10 \Omega$

Finally, $R_0 (1 + \alpha t) = 11 \Omega$

$$\therefore \frac{11}{10} = \frac{1 + \alpha t}{1 + 30\alpha}$$

$$\text{or, } 10 + (10 \times 0.002 \times t) = 11 + 330 \times 0.002$$

$$\text{or, } 0.02t = 1 + 0.66 = 1.66 \quad \text{or } t = \frac{1.66}{0.02} = 83^\circ \text{C.}$$

39. (b) As $P = I^2 R$, so $P_1 = (1.01 I)^2 R = 1.02 I^2 R = 1.02 P$.
 It means % increase in power

$$= \left(\frac{P_1}{P} - 1 \right) \times 100 = 2\%.$$

40. (b) Let I_1 be the current through 5Ω resistance, I_2 through $(6 + 9) \Omega$ resistance. Then as per question,

$$I_1^2 \times 5 = 20 \text{ or, } I_1 = 2 \text{ A.}$$

Potential difference across C and D = $2 \times 5 = 10 \text{ V}$

$$\text{Current } I_2 = \frac{10}{6 + 9} = \frac{2}{3} \text{ A.}$$

Heat produced per second in 2Ω

$$= I_2^2 R \left(\frac{8}{3} \right)^2 \times 2 = 14.2 \text{ cal/s.}$$

41. (b) $\frac{P}{Q} = \frac{R}{S}$ where $S = \frac{S_1 S_2}{S_1 + S_2}$

42. (c) $R = \frac{\rho \ell_1}{A_1}$, now $\ell_2 = 2\ell_1$

$$A_2 = \pi (r_2)^2 = \pi (2r_1)^2 = 4\pi r_1^2 = 4A_1$$

$$\therefore R_2 = \frac{\rho (2\ell_1)}{4A_1} = \frac{\rho \ell_1}{2A_1} = \frac{R}{2}$$

\therefore Resistance is halved, but specific resistance remains the same.

43. (d) $E = V + Ir$

$$V = 12 - 3 = 9 \text{ volt}$$

44. (c) $I = neAV_d$

$$V_d = \frac{I}{neA} = 5 \times 10^{-3} \text{ m/sec}$$

45. (d) Since due to wrong connection of each cell the total emf reduced to 2ϵ then for wrong connection of three cells the total emf will be reduced to $(n\epsilon - 6\epsilon)$ whereas the total or equivalent resistance of cell combination will be nr .