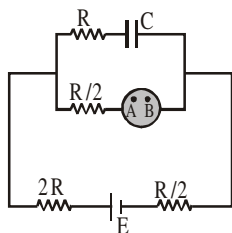


CAPACITANCE & CAPACITOR

1. Capacity of an isolated sphere is increased n times when it is enclosed by an earthed concentric sphere. The ratio of their radii would be:

(1) $\frac{n^2}{n-1}$ (2) $\frac{n}{n-1}$ (3) $\frac{2n}{n+1}$ (4) $\frac{2n+1}{n+1}$


2. A conducting solid sphere is joined in an electrical circuit as shown in figure-



Two imaginary points A and B are taken inside the sphere. For given conditions-

- (1) $V_A > V_B$
 - (2) $V_A < V_B$
 - (3) $V_A = V_B$
 - (4) Data insufficient

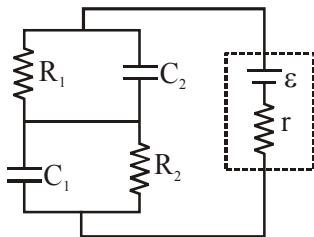3. In the given circuit, $R_1 = 2\Omega$, $R_2 = 3\Omega$, $r = 1\Omega$, $\varepsilon = 6V$, $C_1 = 1\mu F$ and $C_2 = 2\mu F$. In steady state the ratio of energy stored in the capacitors C_2 and C_1 is




- (1) $\frac{6}{9}$ (2) $\frac{9}{6}$ (3) $\frac{8}{9}$ (4) $\frac{9}{9}$

4. There are 8 drops of a conducting fluid. Each has radius r and they are charged to potential 1 volt. They are then combined to form a bigger drop. Find potential of big drop.

- (1) 1 V (2) 4 V (3) 2 V (4) 8 V

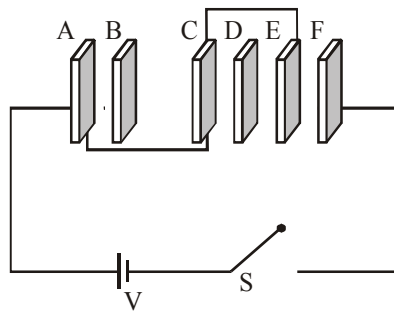5. A,B,C,D,E and F are conducting plates each of area A, and any two consecutive plates are separated by a distance d. The net energy stored in the system after the switch S is closed is :-



$$(1) \frac{3\varepsilon_0 A}{2d} V^2 \qquad (2) \frac{5\varepsilon_0 A}{12d} V^2$$

$$(3) \quad \frac{\varepsilon_0 A}{2d} V^2 \qquad (4) \quad \frac{\varepsilon_0 A}{d} V^2$$


6. When an additional charge of $2C$ is given to a capacitor, energy stored in it is increased by 21%. The original charge of the capacitor is :-

7. Three capacitors C_1 , C_2 and C_3 are connected to a battery as shown in figure. The three capacitors have equal capacitances. Which capacitor stores the most energy :-

(1) \mathbf{C}_1


(2) C_2

(3) C_3

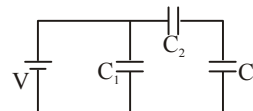

- (4) All three capacitors store the same amount of energy

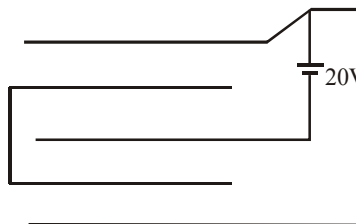8. Five identical plates of dimension $5\text{ cm} \times 8\text{ m}$ are placed at separation of 8.85 mm from each other. If they are connected through a battery which provides constant potential difference of 20V as shown, then find the total charge given by battery.




(1) $8 \times 10^{-9} \text{ C}$

(2) $16 \times 10^{-9}\text{C}$

(3) $4 \times 10^{-9} \text{ C}$


(4) $12 \times 10^{-9} \text{ C}$

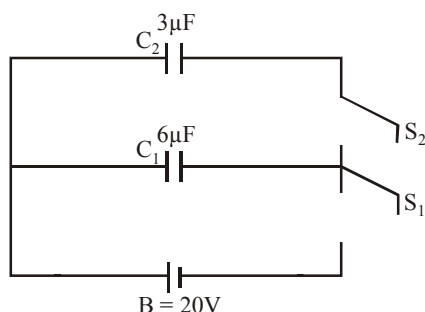9. In the circuit shown in fig. $C_1 = 6\mu\text{F}$, $C_2 = 3\mu\text{F}$ and battery $B = 20\text{V}$. The switch S_1 is first closed. It is opened after long time and S_2 is closed. What is the final charge on C_2 ?




(1) $120\mu\text{C}$ (2) $80\mu\text{C}$ (3) $40\mu\text{C}$ (4) $20\mu\text{C}$

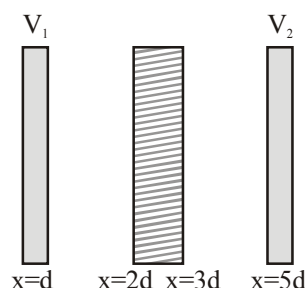10. Two identical thin metal plates has potential V_1 and V_2 ($V_1 > V_2$). A neutral metal slab is placed between these two plates. Find potential of right surface of metal slab




- (1) $\frac{V_1 + V_2}{2}$ (2) $\frac{2V_1 + V_2}{3}$
 (3) $\frac{V_1 - V_2}{3}$ (4) $\frac{V_1 + 2V_2}{3}$

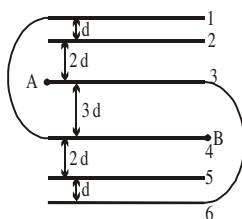11. There are six plates of equal area A and the plates are arranged as shown in figure. The equivalent capacitance between points A and B is $\frac{\alpha \epsilon_0 A}{d}$. Find value of α .




- (1) 1 (2) 2 (3) 3 (4) 4

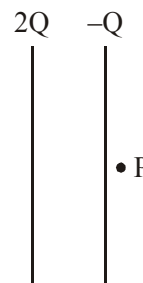12. In figure, the plates of a parallel plate capacitor have unequal charges. Its capacitance is C . P is a point outside the capacitor and close to the plate of charge $-Q$. The distance between the plates is d . Then which of following is incorrect:-




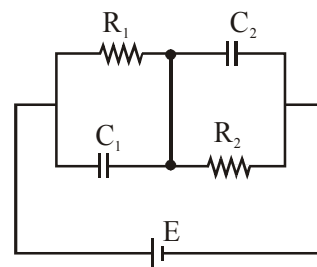- (1) a point charge at point P will experience electric force due to the capacitor
 (2) the potential difference between the plates will be $3Q/2C$
 (3) the energy stored in the electric field in the region between the plates is $9Q^2/8C$
 (4) the force on one plate due to the other plate is $Q^2/2\pi\epsilon_0 d^2$
13. For the circuit shown in figure the ratio of energy stored in capacitor (1) to that of in capacitor (2) is



- (1) $\frac{R_1 C_1}{R_2 C_2}$ (2) $\frac{R_1 C_2}{R_2 C_1}$ (3) $\frac{R_1^2 C_1}{R_2^2 C_2}$ (4) $\frac{R_1 C_1^2}{R_2 C_2^2}$
14. A proton, deuteron and α -particle are accelerated by same potential difference. They enter between parallel plates of a capacitors in direction perpendicular to electric field, then deflection of:-
- (1) Proton is maximum
 (2) Deuteron is maximum
 (3) α -particle is maximum
 (4) All particle will be same

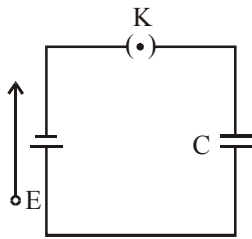15. A parallel plate capacitor is connected to a battery as shown in figure. Consider two situations:




A: Key K is kept closed and plates of capacitors are moved apart using insulating handle.


B: Key K is opened and plates of capacitors are moved apart using insulating handle.

Choose the **CORRECT** option :-

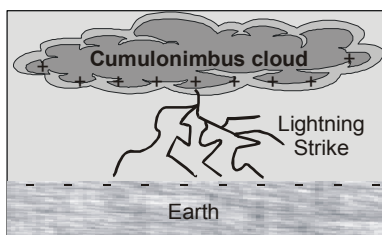
- (1) In A : Q remains same but C changes.
 - (2) In B : V remains same but C changes.
 - (3) In A : V remains same and hence Q changes.
 - (4) In B : Q remains same and hence V remains constant.
16. A cumulonimbus cloud is 5 km long and 2 km wide and has its base 1 km above the surface of the earth as shown here. Consider the cloud and earth to be a parallel plate capacitor with air as the dielectric. Then the capacitance of the cloud-earth combination is-



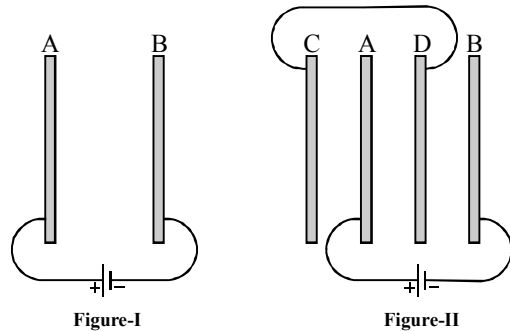- (1) $8.8 \mu\text{F}$
 - (2) $8.08 \mu\text{F}$
 - (3) $0.088 \mu\text{F}$
 - (4) $0.88 \mu\text{F}$
17. A parallel plate capacitor is connected to a battery which builds up an electric field of 60 V/cm between the plates as shown in figure-I. Now two initially neutral plates that are connected are positioned as shown in figure-II. The plates are at equal distances from each other. Find the electric field strength between the plates B and D.



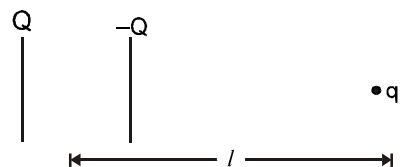- (1) 8 kV/m
 - (2) 6 kV/m
 - (3) 4 kV/m
 - (4) 3 kV/m
18. A parallel plate capacitor of plate area 0.2 m^2 and spacing 10^{-2} m is charged to 10^3 volt and then disconnected from the battery, and pull apart to double the plate spacing
- (1) Final charge on the capacitor becomes two times of initial
 - (2) Final charge becomes half of initial value.
 - (3) Final voltage on the capacitor will remain 10^3 Volts .
 - (4) Final voltage on the capacitor is $2 \times 10^3 \text{ Volts}$.
19. An electron is in equilibrium between two horizontal plates of a charged capacitor. If the plates are interchanged in position. It means electric field is reversed then the acceleration of the electron will be :-
- (1) Details are not complete
 - (2) g
 - (3) $2g$
 - (4) 5 m/sec^2
20. The plates of small size of a parallel plate capacitor are charged as shown. The force on the charged particle of ' q ' at a distance ' l ' from the capacitor is : (Assume that the distance between the plates is $d \ll l$)




- (1) zero
- (2) $\frac{Qqd}{2\pi\epsilon_0\ell^3}$
- (3) $\frac{Qqd}{\pi\epsilon_0\ell^3}$
- (4) $\frac{Qqd}{4\pi\epsilon_0\ell^3}$

21. A parallel plate capacitor is to be designed with a voltage rating 1 kV using a material of dielectric constant 3 and dielectric strength about 10^7 V/m. What minimum area of plates is required to have a capacitance 50 pF :-


- (1) 1.9 cm^2 (2) 40 cm^2
(3) 62 cm^2 (4) 35 cm^2

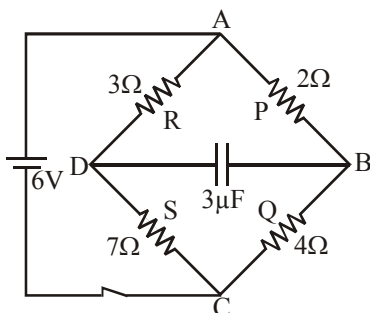22. In steady state, the energy stored in the capacitor as shown in figure is :-




- (1) 80 nJ (2) 20 nJ (3) 100 nJ (4) 60 nJ

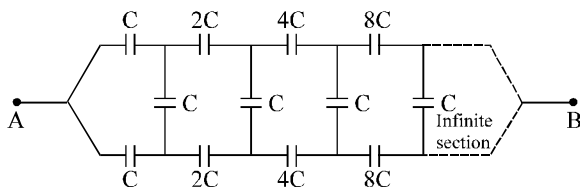23. Find the equivalent capacitance of the circuit between point A and B.




- (1) $\frac{C}{3}$ (2) $\frac{C}{8}$ (3) C (4) $\frac{C}{32}$

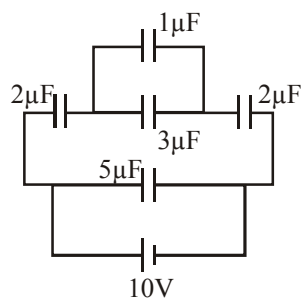24. The ratio of potential difference between $1 \mu\text{F}$ and $5 \mu\text{F}$ capacitors -



- (1) 1 : 2 (2) 4 : 5
(3) 1 : 5 (4) 1 : 4

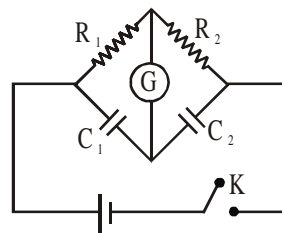25. In the circuit, if no current flows through the galvanometer when the key K is closed, the bridge is balanced. The balancing condition for bridge is




- (1) $\frac{C_1}{C_2} = \frac{R_1}{R_2}$ (2) $\frac{C_1}{C_2} = \frac{R_2}{R_1}$
(3) $\frac{C_1^2}{C_2^2} = \frac{R_1^2}{R_2^2}$ (4) $\frac{C_1^2}{C_2^2} = \frac{R_2}{R_1}$

26. A parallel plate capacitor of capacitance C is connected to a battery and is charged to a potential difference V . Another capacitor of capacitance $2C$ is connected to another battery and is charged to potential difference $2V$. The charging batteries are now disconnected and the capacitors are connected in parallel to each other in such a way that the positive terminal of one is connected to the negative terminal of the other. The final energy of the configuration is—


- (1) Zero (2) $\frac{25CV^2}{6}$ (3) $\frac{3CV^2}{2}$ (4) $\frac{9CV^2}{2}$

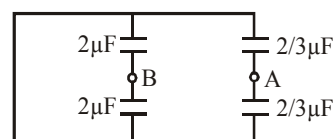27. The equivalent capacitance of the circuit across the terminals A and B is equal to :-




- (1) $0.5 \mu\text{F}$ (2) $2 \mu\text{F}$
(3) $1 \mu\text{F}$ (4) none of these

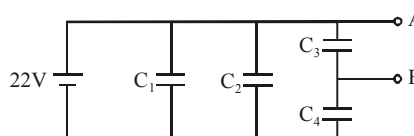28. In fig. given $C_1 = 3\mu\text{F}$, $C_2 = 5\mu\text{F}$, $C_3 = 9\mu\text{F}$, and $C_4 = 13\mu\text{F}$. What is the potential difference between points A and B?




- (1) 13 V (2) 9 V (3) 0 V (4) 11 V

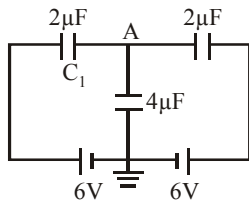
29. Three capacitors are connected as shown in fig. Then the charge on capacitor C_1 is :-



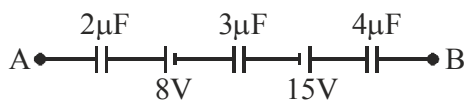
- (1) $6\mu\text{C}$ (2) $12\mu\text{C}$ (3) $18\mu\text{C}$ (4) $24\mu\text{C}$
30. The potential of the point A is greater than that of B by 19 volt. What is the potential difference in volts across the $3\mu\text{F}$ capacitor ?



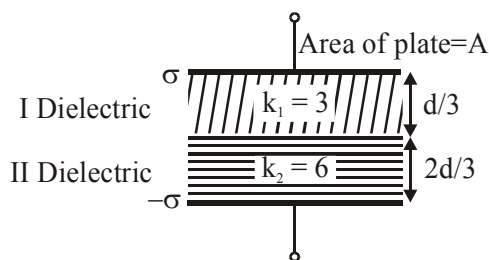- (1) 7 (2) 8 (3) 23 (4) 4
31. In the figure shown σ is the surface charge density on the upper metallic plate



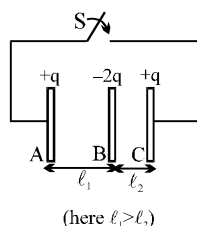
- (1) The ratio of energy density in I dielectric to II dielectric is 2
 (2) The ratio of energy density in I dielectric to II dielectric is 4
 (3) The ratio of energy density in I dielectric to II dielectric is 1
 (4) None of these
32. Three long conducting plate A, B & C having charges $+q$, $-2q$ & $+q$ as shown in figure. Here plate A and C are fixed. If the switch S is closed the middle plate (B) will start moving in



- (1) Left direction
 (2) Right direction
 (3) will not move
 (4) First move leftward & then rightward
33. Two parallel plate capacitors of capacitance C_0 and $2C_0$ are connected in parallel and charged to a potential difference V_0 . Now the battery is disconnected and the region between the capacitor plates of capacitance C_0 is completely filled with a dielectric of dielectric constant K . The potential difference across the capacitors, now becomes :

(1) $\frac{V_0}{(3K+1)}$ (2) $\frac{3V_0}{(K+2)}$ (3) $\frac{2V_0}{K}$ (4) $\frac{V_0}{(2K+1)}$

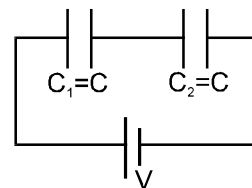34. Two identical capacitor C_1 and C_2 are connected in series with a battery. They are fully charged. Now a dielectric slab is inserted between the plates of C_2 . The potential difference across C_1 will :




- (1) increase
 (2) decrease
 (3) remain same
 (4) depend on internal resistance of the cell
35. Two identical plates of a parallel plate capacitor are given charges $+q$ and $-3q$. If σ_1 and σ_2 are the charge densities on outer and inner faces of the first plate then,

(1) $\sigma_1 = \sigma_2$ (2) $\sigma_1 = \frac{-\sigma_2}{2}$

(3) $\sigma_1 = \frac{\sigma_2}{2}$ (4) $\sigma_2 = \frac{\sigma_1}{2}$

36. If dielectric constant and dielectric strength be denoted by K and X respectively, then a material suitable for use as a dielectric in a capacitor must have
- (1) high K and high X (2) high K and low X
 (3) low K and high X (4) low K and low X

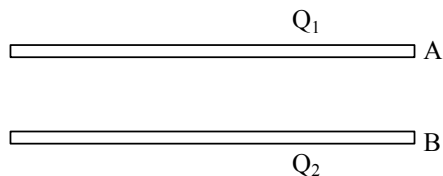37. Two conducting plates A and B are parallel. A is given a charge Q_1 and B is given a charge Q_2 . The charge on inner side of B is -



- (1) $\frac{Q_1 - Q_2}{2}$
 (2) $\frac{Q_2 - Q_1}{2}$
 (3) $\frac{(Q_1 + Q_2)}{2}$
 (4) $\frac{-(Q_1 + Q_2)}{2}$


38. A capacitor has some dielectric between its plates, and the capacitor is connected to a dc source. The battery is now disconnected and then the dielectric is removed, then :-

- (1) capacitance will increase
 (2) energy stored will decrease
 (3) electric field will increase
 (4) voltage will decrease

39. In a parallel plate capacitor with air between the plates each plate has an area of $6 \times 10^{-3} \text{ m}^2$ and the distance between the plates is 3 mm. Now this capacitor is connected to a 100 V supply. Now supply is disconnected and a mica sheet (of dielectric constant = 6) is inserted between the plates. Find the voltage across capacitor :-


- (1) 100 V (2) 600 V
 (3) $\frac{50}{3}$ V (4) $\frac{100}{3}$ V

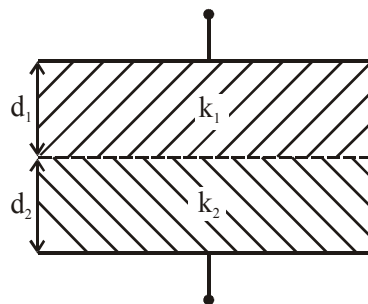40. A parallel plate capacitor is made of two dielectric blocks in series. One of the block has thickness d_1 and dielectric constant k_1 and the other has thickness d_2 and dielectric constant k_2 as shown in figure. This arrangement can be thought as a dielectric slab of thickness $d = (d_1 + d_2)$ and effective dielectric constant k . The value of k is :-




- (1) $\frac{k_1 d_1 + k_2 d_2}{d_1 + d_2}$ (2) $\frac{k_1 d_1 + k_2 d_2}{k_1 + k_2}$
 (3) $\frac{k_1 k_2 (d_1 + d_2)}{k_1 d_2 + k_2 d_1}$ (4) $\frac{2k_1 k_2}{k_1 + k_2}$

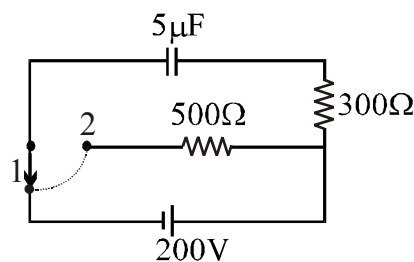41. A capacitor of capacitance $5\mu\text{F}$ is connected to a source of constant emf of 200V for a long time, then the switch was shifted to contact 2 from contact 1. The total amount of heat generated in the 500Ω resistance, thereafter is:-




- (1) $1/32 \text{ J}$ (2) $3/32 \text{ J}$
 (3) $2/32 \text{ J}$ (4) $5/32 \text{ J}$

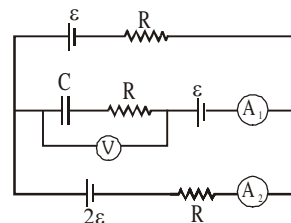42. In the given circuit, ammeters A_1 and A_2 are ideal and the voltmeter (V) is having very large resistance. In the steady state reading of ammeters A_1 , A_2 and voltmeter (V) will be respectively




- (1) $0, \frac{\varepsilon}{2R}$ and $\frac{\varepsilon}{2}$ (2) $0, \frac{\varepsilon}{R}$ and $\frac{\varepsilon}{2}$
 (3) $0, \frac{\varepsilon}{2R}$ and $\frac{5\varepsilon}{2}$ (4) $0, \frac{\varepsilon}{2R}$ and $\frac{3\varepsilon}{2}$

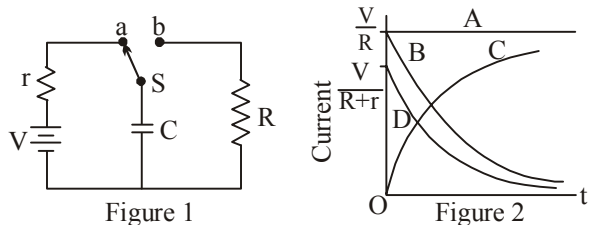
43. The capacitor shown in figure 1 is charged by connecting switch S to contact 'a' for a long time. If switch S is thrown to contact 'b' at time $t = 0$, which of the curves in figure 2 represents the magnitude of the current through the resistor R as a function of time?



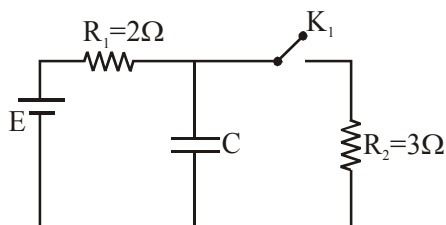
- (1) A (2) B (3) C (4) D
44. In the circuit shown in the figure K_1 is open. The charge on capacitor C in steady state is q_1 . Now key is closed and at steady state charge on C is q_2 . The ratio of charges q_1/q_2 is



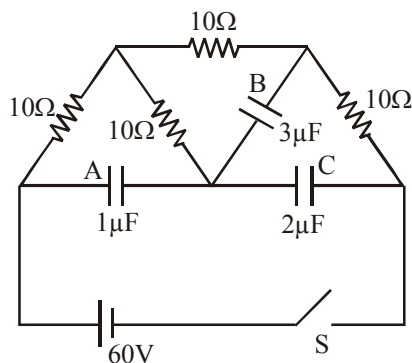- (1) 5/3 (2) 3/5 (3) 1 (4) 2/3
45. In the given figure, the switch S is closed at time $t = 0$. Q_A , Q_B and Q_C are charges on the capacitor A, capacitor B and capacitor C in the steady state respectively. Choose the correct statement :-




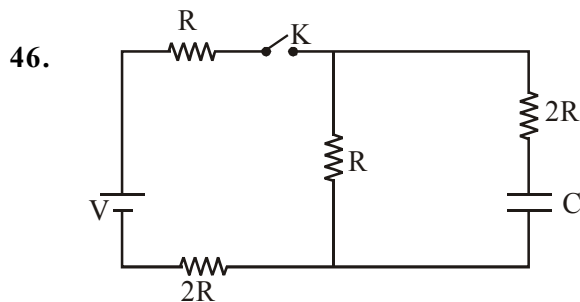- (1) $Q_A < Q_B < Q_C$
 (2) $Q_A < Q_C < Q_B$
 (3) $Q_C < Q_A < Q_B$
 (4) $Q_C < Q_B < Q_A$




Find time constant for given circuit :-

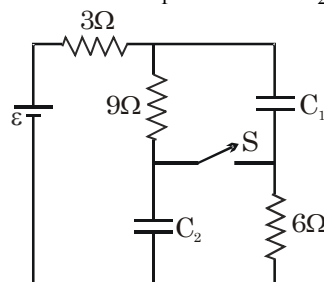- (1) $\frac{11RC}{4}$ (2) $\frac{8RC}{3}$ (3) $\frac{7RC}{3}$ (4) $\frac{9RC}{4}$
47. In above question, find time constant when key is open :
- (1) $\frac{8RC}{3}$ (2) $\frac{7RC}{3}$ (3) $3RC$ (4) $\frac{3RC}{2}$
48. In the circuit shown there is steady state with the switch closed. The switch is opened at $t = 0$. Choose the incorrect option.
 (Given : $\varepsilon = 24V$, $C_1 = 3F$ and $C_2 = 2F$)





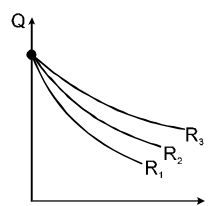- (1) The voltage across C_1 before the switch is open is 12V.
 (2) The voltage across C_1 after a long time after the switch is open is 12V.
 (3) The voltage across C_2 after a long time after the switch is open is 24V.
 (4) The voltage across C_2 before the switch is open is 8V.
49. Three identical capacitors are given a charge Q each and they are then allowed to discharge through resistance R_1 , R_2 and R_3 separately. Their charges, as a function of time are shown in the graph below. The smallest of the three resistances is



- (1) R_3 (2) R_2
 (3) R_1 (4) cannot be predicted

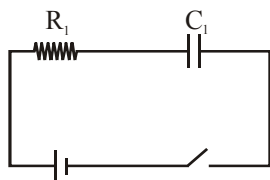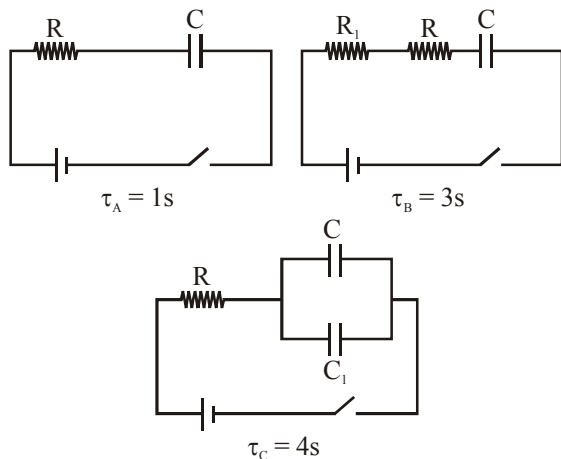- (1) ∞
 - (2) $\log_e 2$
 - (3) $\log_{10} 2$
 - (4) Zero



- (1) 2 sec (2) 4 sec
(3) 6 sec (4) 1 sec

- (1) 3×10^{-6} J (2) 6×10^{-6} J
(3) 4×10^{-6} J (4) 18×10^{-6} J

- (1) 30 cm (2) 20 cm
(3) 10 cm (4) 15 cm

Que.	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	2
Ans.	2	1	3	2	3	4	1	1	3	2	1	4	3	4	3	3	1	4	3	2
Que.	21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	4
Ans.	1	4	3	3	2	3	3	1	1	2	1	2	2	1	2	1	2	3	3	3
Que.	41	42	43	44	45	46	47	48	49	50	51	52	53							
Ans.	3	1	2	1	1	1	3	2	3	4	3	4	1							