
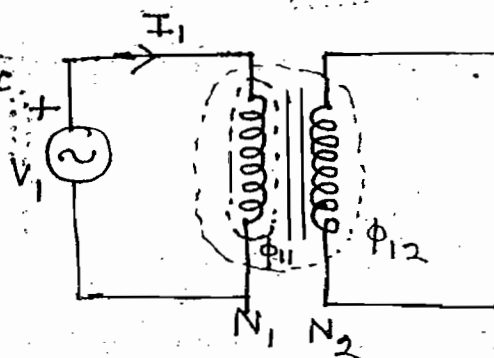


Magnetic Coupled Circuits:-

Case-(1):-

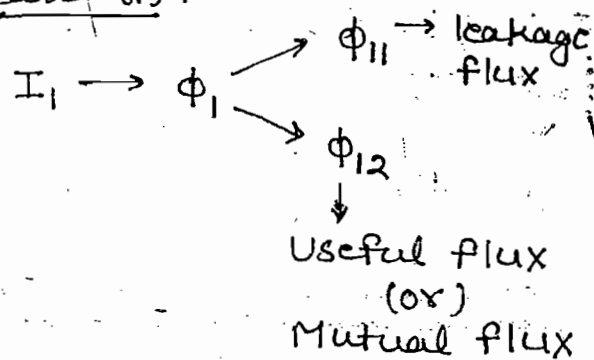

$$e_1 \propto \frac{d\phi_1}{dt}$$

$$e_1 = -N_1 \frac{d\phi_1}{dt}$$

$$e_1 = -N_1 \frac{d\phi_1}{di_1} \cdot \frac{di_1}{dt} \quad \left(L = \frac{N\phi}{i} \right)$$

$$e_1 = -L_1 \frac{di_1}{dt}$$

Self induced emf

$$e_2 \propto \frac{d\phi_{12}}{dt}$$

$$e_2 = -N_2 \frac{d\phi_{12}}{dt}$$

$$e_2 = -N_2 \frac{d\phi_{12}}{di_1} \frac{di_1}{dt}$$


$$e_2 = -M_{21} \frac{di_1}{dt}$$

Mutual Induced emf

$$\left(M_{21} = \frac{N_2 \phi_{12}}{i_1} \right)$$

Mutual inductance of second inductor w.r.t. 1

Case-(II):-

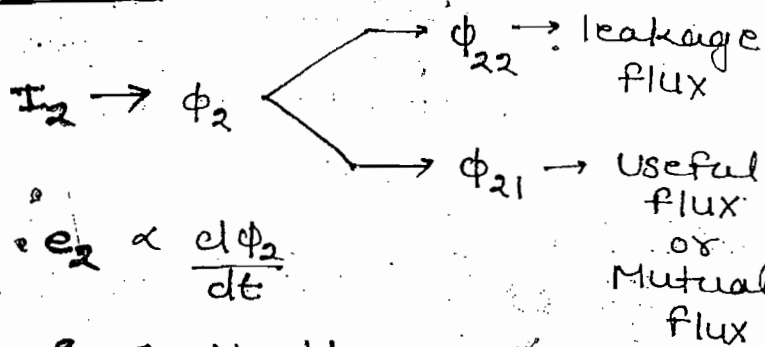


$$e_2 = -N_2 \frac{d\phi_2}{dt}$$

$$e_2 = -N_2 \frac{d\phi_2}{di_2} \frac{di_2}{dt} \quad \left(L = \frac{N\phi}{i} \right)$$

$$e_2 = -L_2 \frac{di_2}{dt}$$

Self induced emf

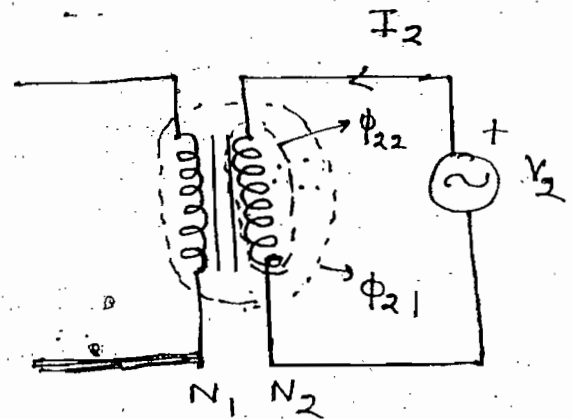

$$e_1 \propto \frac{d\phi_{21}}{dt}$$

$$e_1 = -N_1 \frac{d\phi_{21}}{dt}$$

$$e_1 = -N_1 \frac{d\phi_{21}}{di_2} \cdot \frac{di_2}{dt}$$


$$(M_{12} = \frac{N_1 \phi_{21}}{i_2})$$

$$e_1 = -M_{12} \frac{di_2}{dt}$$

Mutual induced emf


If current is flowing in any one of inductor then the sign of self & mutually induced voltage is same

Note:-

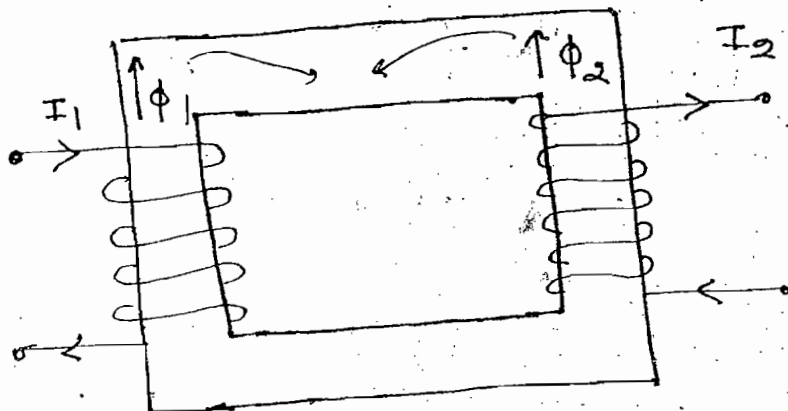


In above figure flux of the two inductors are completely closed path in opposite direction. Hence sign of mutually induced voltage is opposite to sign of self induced voltage


Dot convention:-

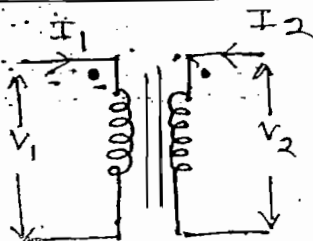


(I)

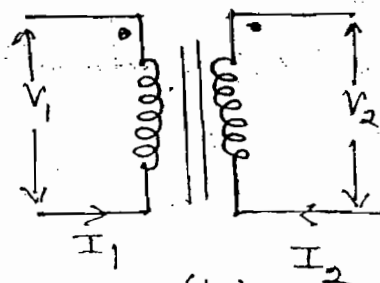

(II)

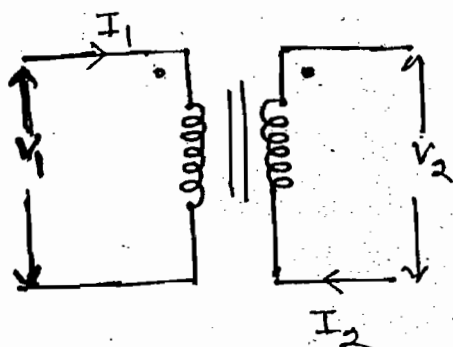

(III)

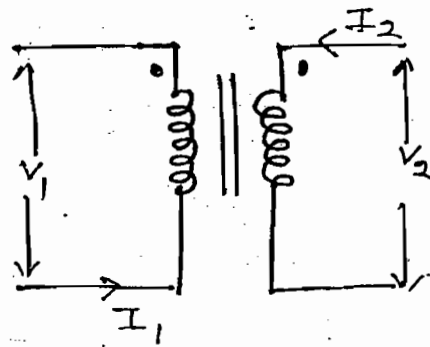

(IV)

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$M_{12} = M_{21} = M$
Valid for (I) & (II)

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

Valid for (III) & (IV)


Note:-

- When either both currents are entering or both are leaving at dotted terminal sign of mutually induced voltage is same as the sign of self induced voltage.
- When one current is entering and other current is leaving at dotted terminal sign of the mutually induced voltage is opposite to sign of self induced voltage.

Coefficient of Coupling / Coupling Factor:-

$$k = \frac{\text{Useful flux}}{\text{Total flux}}$$
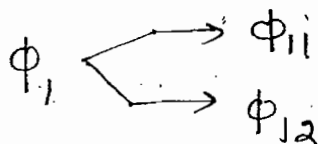
$$\rightarrow k_1 = k_2 \rightarrow \text{condition}$$



$$k_1 = \frac{\Phi_{12}}{\Phi_1}$$

14/11/21



$$k_2 = \frac{\phi_{21}}{\phi_2}$$

$$K = \sqrt{k_1 k_2}$$

For ideal system $K=1$ and for practical system the range of K is 0 to 1

$$M_{21} = \frac{N_2 \phi_{12}}{i_1}$$

$$M_{12} = \frac{N_1 \phi_{21}}{i_2}$$

$$M_{12} = M_{21} = M$$

$$M^2 = M_{12} M_{21}$$

$$\Rightarrow M^2 = \frac{N_1 \phi_{12}}{i_1} \cdot \frac{N_2 \phi_{21}}{i_2} \quad \text{--- (1)}$$

$$\phi_{12} = k_1 \phi_1 \quad \text{--- (II)}$$

$$\phi_{21} = k_2 \phi_2 \quad \text{--- (III)}$$

substitute eq- (II) & (III) in eq- (1)

$$M^2 = k_1 k_2 \frac{N_1 \phi_1}{i_1} \cdot \frac{N_2 \phi_2}{i_2}$$

$$M^2 = K^2 L_1 L_2$$


$$\Rightarrow \boxed{M = K \sqrt{L_1 L_2}}$$

$$V = L_1 \frac{di}{dt} + M \frac{di}{dt} + L_2 \frac{di}{dt} + M \frac{di}{dt}$$

$$L_{eq} \frac{di}{dt} = (L_1 + L_2 + 2M) \frac{di}{dt}$$


$$L_{eq} = L_1 + L_2 + 2M$$

→ Series Aiding

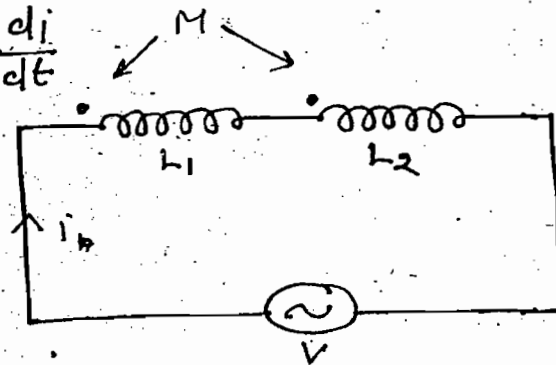


→ Series Opposing:-

$$L_{eq} = L_1 + L_2 - 2M$$

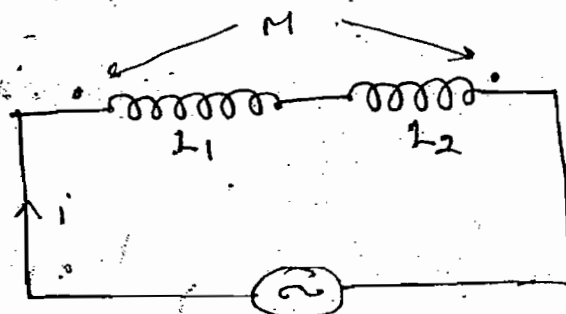


→ Parallel Aiding:-
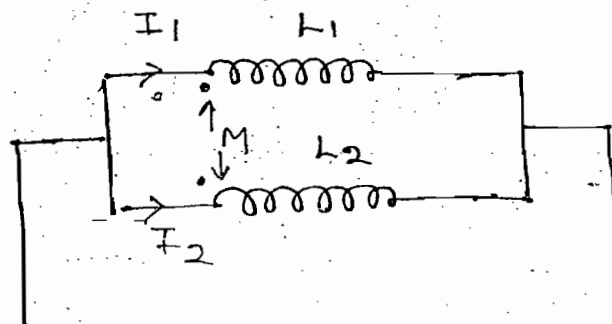
$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$




→ Parallel Opposing:-
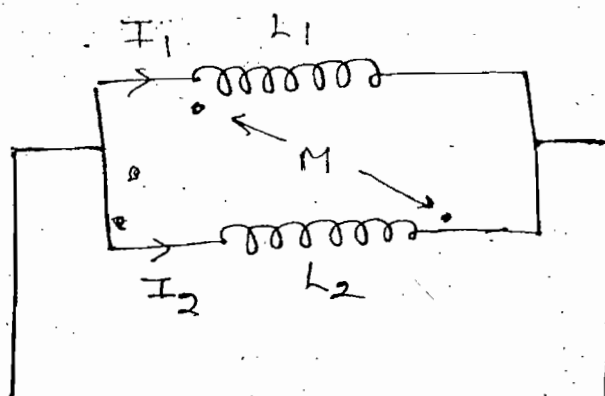
$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$



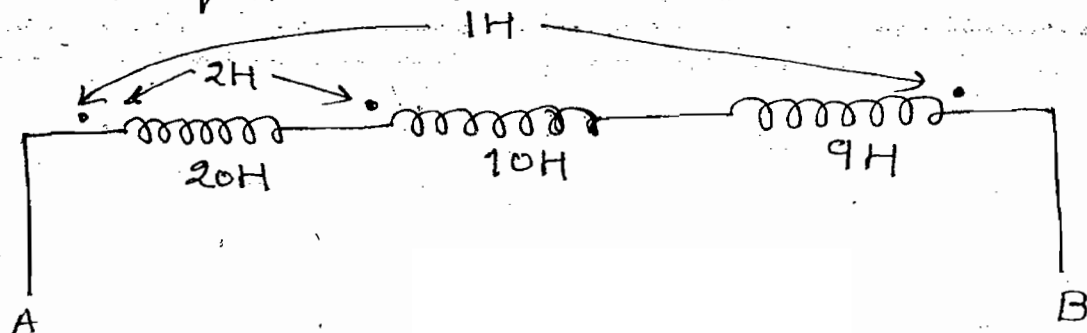
Ques:- Find equivalent inductance w.r.t A and B



Soln:- $L_{eq} = L_1 + L_2 + L_3 \pm 2M_1 \pm 2M_2 \pm 2M_3$

$\Rightarrow L_{eq} = 20 + 10 + 9 + 2(2) + 0 - 2(1)$

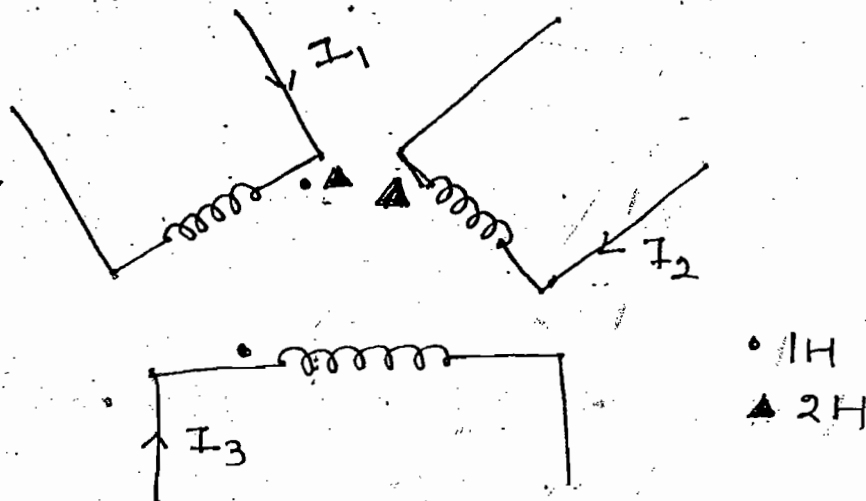ques:- Develop inductance matrix of the figure shown




Soln:- Diagonal points denotes self inductance

$$L = \begin{bmatrix} L_{11} & L_{12} & L_{13} \\ L_{21} & L_{22} & L_{23} \\ L_{31} & L_{32} & L_{33} \end{bmatrix}$$

$$L = \begin{bmatrix} 15 & -2 & 1 \\ -2 & 20 & 0 \\ 1 & 0 & 10 \end{bmatrix}$$

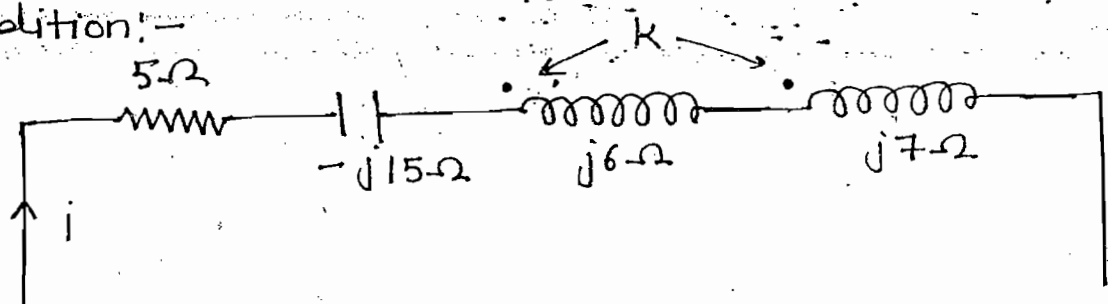ques:- Find the value of K under resonance condition:-



Soln:-

$$2\pi f (L_{eq} = L_1 + L_2 + 2M)$$

$$M = k \sqrt{L_1 L_2}$$

$$\Rightarrow 2\pi f M = 2\pi f k \sqrt{L_1 L_2}$$




$$X_M = k \sqrt{X_1 X_2}$$

$$X_{eq} = X_1 + X_2 + 2X_M$$

$$\Rightarrow X_{eq} = X_1 + X_2 + 2k \sqrt{X_1 X_2}$$

$$\Rightarrow 15 = 6 + 7 + 2k \sqrt{6 \times 7}$$
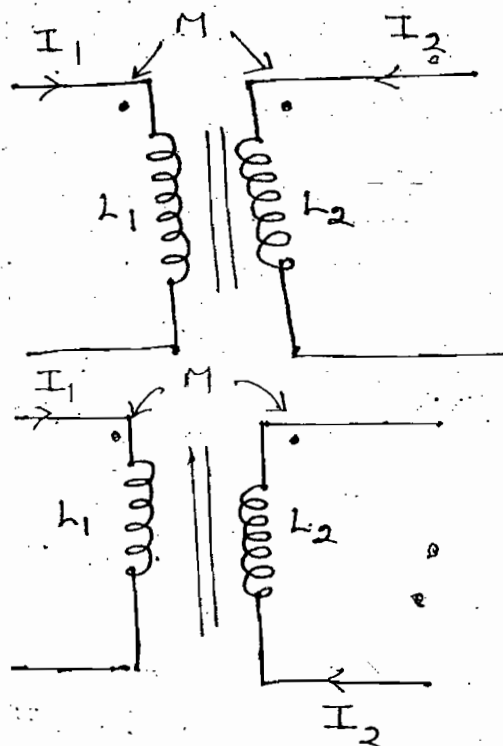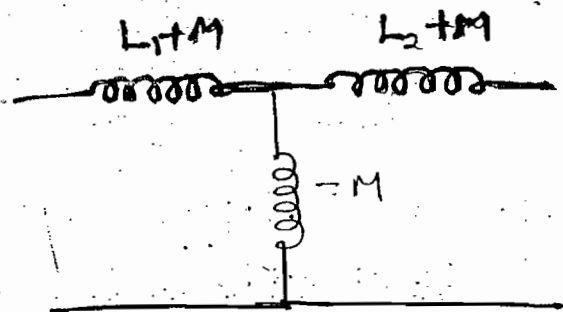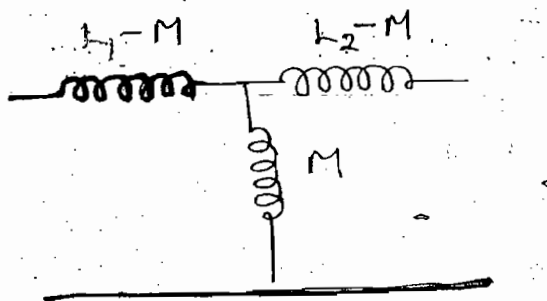
$$\Rightarrow \boxed{k = \frac{1}{\sqrt{42}}} \quad \text{Ans}$$




$$\boxed{W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm M I_1 I_2}$$


+ $\rightarrow$ Fig-(I) -ve $\rightarrow$ Fig(II)

Energy stored in the coupled coils.


Ques:- Find L_{eq} w.r.t A and B

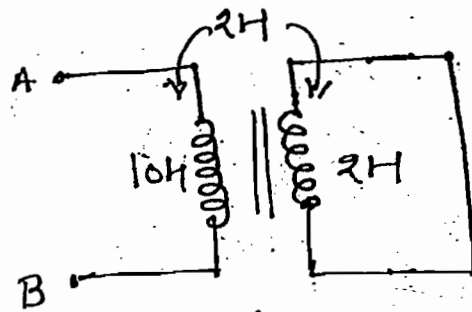

Soln:-

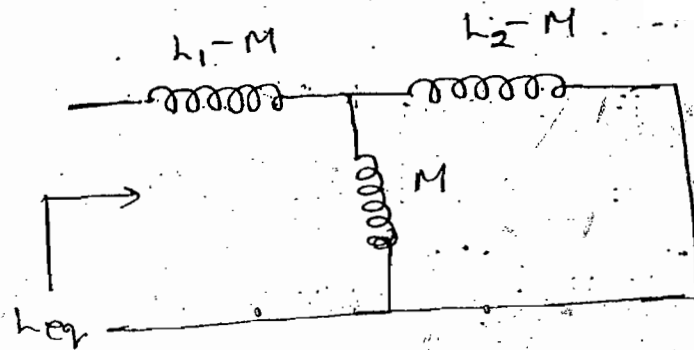
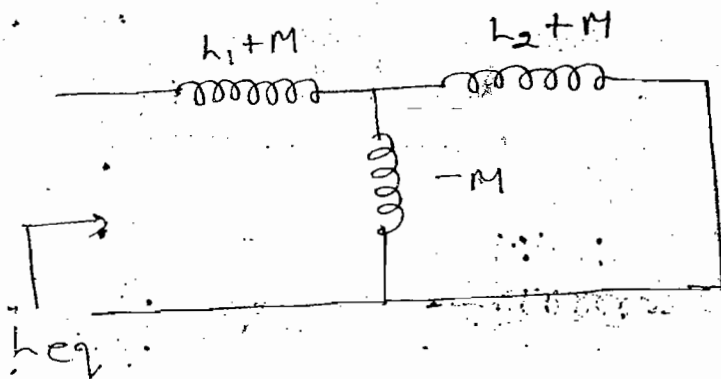
$$L_{eq} = L_1 - M + \frac{M(L_2 - M)}{L_2 - M + M} = L_1 - \frac{M^2}{L_2}$$





$$L_{eq} = (L_1 + M) + \frac{(-M)(L_2 + M)}{L_2 + M - M}$$

$$L_{eq} = L_1 - \frac{M^2}{L_2}$$

$$\Rightarrow L_{eq} = 10 - \frac{2^2}{2} = 8H, \text{ Ans}$$

Graph Theory:-

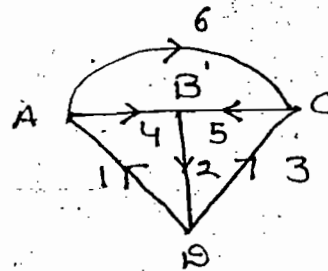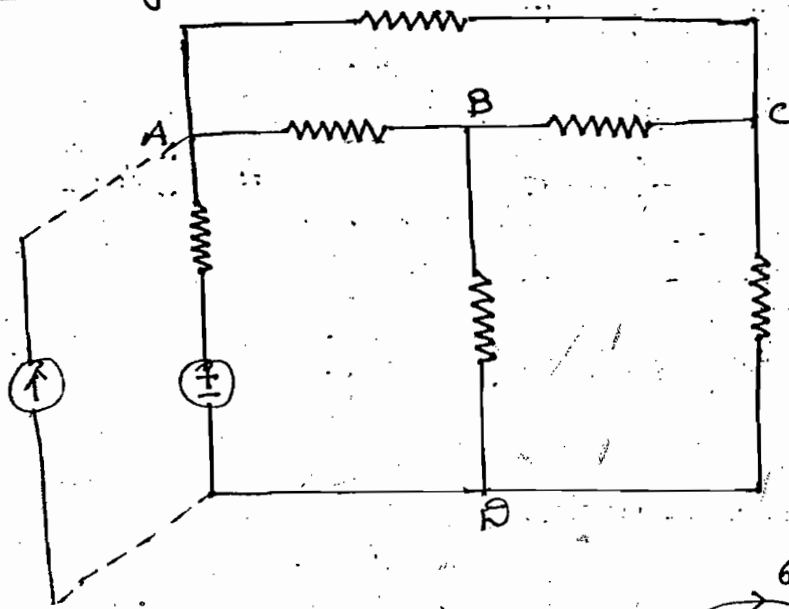

→ N/w topology is the study of the N/w properties by investigating interconnection b/w branches and nodes, it mainly concentrate on the geometry of the N/w

→ In the N/w topology any N/w is replace by graph. To develop graph of each element is replace by either straight line or arc of the semi-circle, voltage source is replace by s.c and current source is replace by o.c and graph retains all the nodes of original N/w

→

$$\text{No. of branches of N/w} \geq \text{No. of branch of graph.}$$

Augmented Incidence Matrix :-

	1	2	3	4	5	6
A	-1			+1		+1
B		+1		-1	-1	
C			-1		+1	-1
D	+1	-1	+1			

$= [A_a]$

Reduced Incidence Matrix :-

	1	2	3	4	5	6
A	-1			+1		+1
B		+1		-1	-1	
C			-1		+1	-1
D	X	X	X	X	X	X

$= [A]$


D $\rightarrow$ Ref - Node or Datum Node


$\rightarrow$ All the information regarding the graph can be represented mathematically in concise form is called as Augmented incidence matrix

$\rightarrow$ For a given graph Augmented incidence matrix is unique

Tree :-

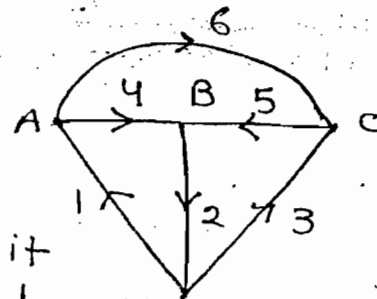$\rightarrow$ Tree is a connected sub-graph. It connects all the nodes of the N/w but it doesn't consist of any closed path



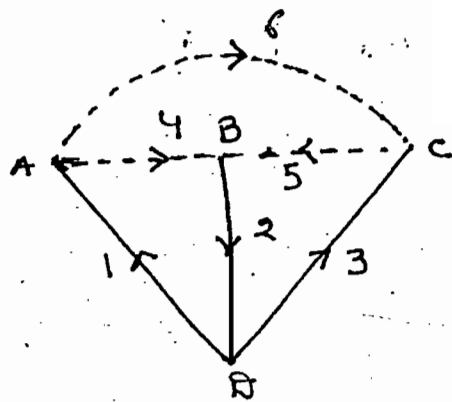

Tree $\{1, 2, 3\}$

$$\begin{aligned} \text{Total Tree Branches} &= N-1 \\ &= 4-1 = 3 \end{aligned}$$

→ The set of branches which are disconnected to form a tree is called as co-tree or complementary tree

Co-Tree $\{4, 5, 6\}$

→ The branch which form a tree is called as tree branch (Twig)

→ Total no. of tree branches $= N-1$

→ The branch which is disconnected to form a tree is called as link (chord)

→ Total no. of links $(l) = b - (N-1)$

N/w where $b =$ total No. of branches of the

→ Tree is not unique

$$\text{Total no. of tree} = N^{N-2} = 4^{4-2} = 16$$



→ Total No. of possible tree $= N^{N-2}$

Note:-

→ The above formula can be applied

(a) When connection is present b/w all the node

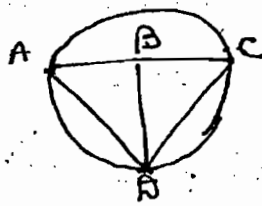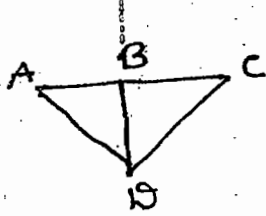(b) When no repeated branch is present b/w the node



→ Total no. of possible tree for any graph
 $= \det(AA^T)$

where A = Reduced incidence matrix

Node Pair Voltages:-


Total no. of node pair voltages = $\frac{N(N-1)}{2}$

eg:- $\frac{V_{AB} \quad V_{AC} \quad V_{BA} \quad V_{BC} \quad V_{BD} \quad V_{CD}}{6}$

Edges = Branches


Total no. of edges (branches) = $\frac{N(N-1)}{2} = \frac{4 \times 3}{2} = 6$

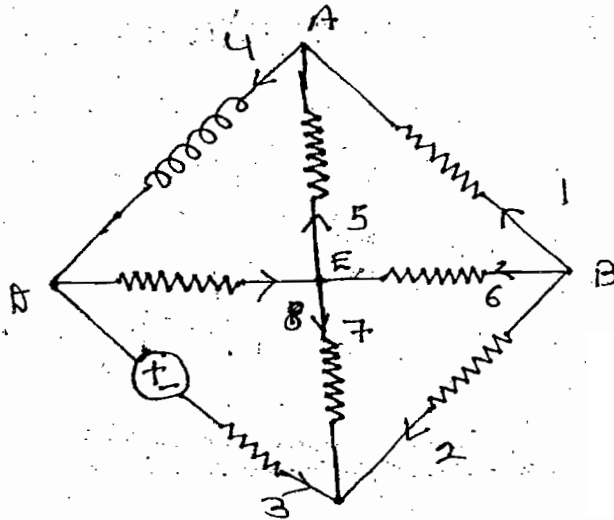ques:- Develop Tie-set matrix of the N/w shown




Step-1:-

Develop the graph for the given N/w

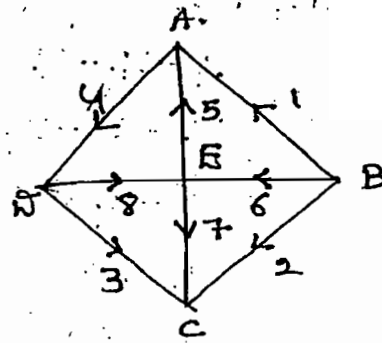

Step-(ii):-

Develop a tree for the graph

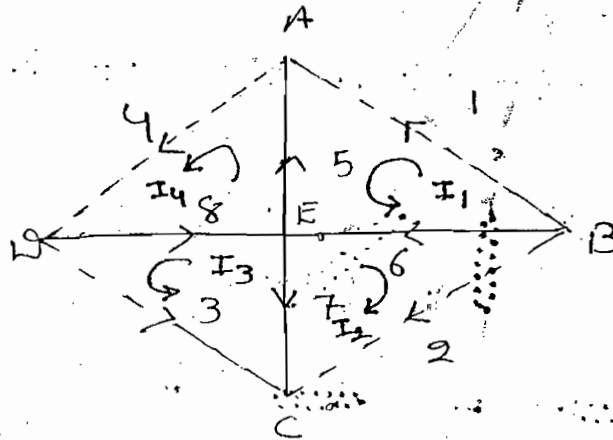

Step-(iii):-

Identify total no. of basic loop / fundamental loop (f-loop) or independent loops

→ Basic loop should consist of only one link

→ Total no. of basic loop = total no. of links

$$\text{i.e. } l = b - (N - 1)$$

→ Basic loop direction is same as link current

direction

	V_1	V_2	V_3	V_4	V_5	V_6	V_7	V_8
	1	2	3	4	5	6	7	8
I_1	+1			-	-1	-1	-	
I_2		+1				-1	-1	
I_3			+1				-1	-1
I_4				+1	+1			+1

= [C]

KVL Equations:-

$$V_1 - V_5 - V_6 = 0$$


$$V_2 - V_6 - V_7 = 0$$

$$V_3 - V_7 - V_8 = 0$$

$$V_4 + V_5 + V_8 = 0$$


$$[C] = [U : C_b]$$

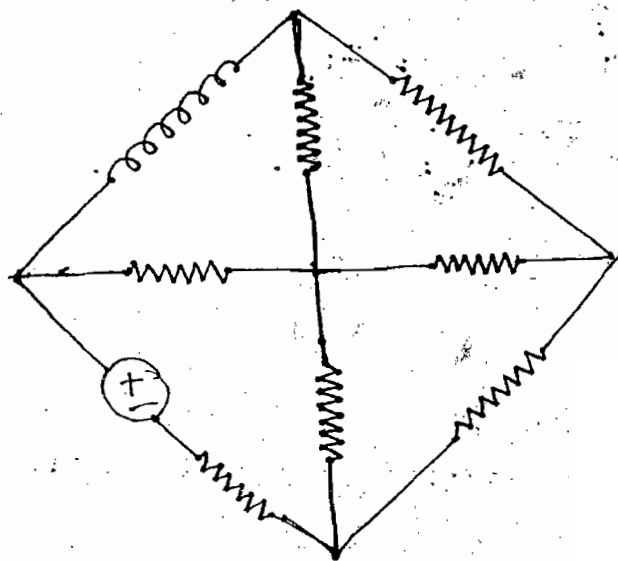ques:- Develop cut-set matrix of the N/w shown




Step-(i):-

Develop a graph for the given N/w

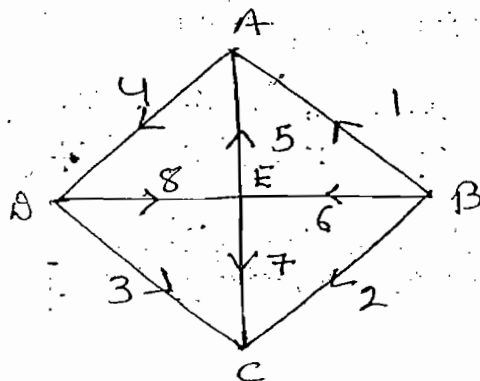

Step-(ii):-

Develop a tree for a graph

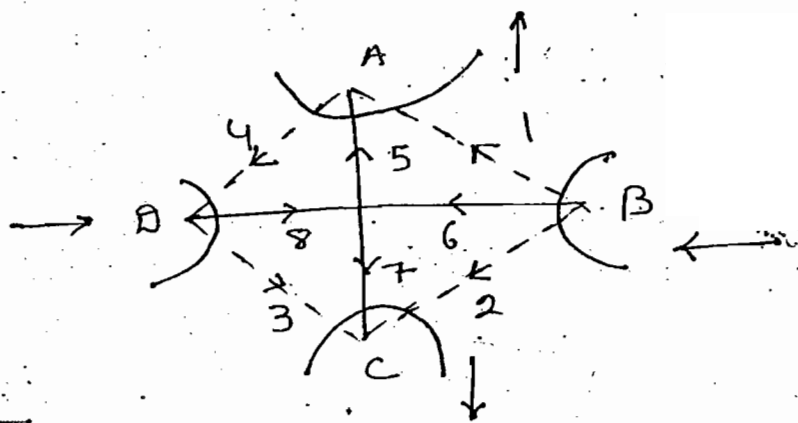

Step-(III):-

Identify total no. of basic cut-sets or fundamental cut-sets / f-cut-sets

→ Basic cut-sets should consist of only one tree branch

→ Total No. of basic cut-sets = total No. of tree branches

$$I \cdot C = N - 1$$

→ Basic cut-set direction as same as a tree branch current direction

	I_1	I_2	I_3	I_4	I_5	I_6	I_7	I_8
	1	2	3	4	5	6	7	8
A	+1			-1	+1			
B	+1	+1				+1		
C		+1	+1				+1	
D			+1	-1				+1

= [B]

KCL Equations:-

$$I_1 - I_4 + I_5 = 0$$

$$I_1 + I_2 + I_6 = 0$$

$$I_2 + I_3 + I_7 = 0$$

$$I_3 - I_4 + I_8 = 0$$

$$[B] = [B_q \quad U]$$

$$[C] = [U : C_b]$$



Tie-set


$$[B] = [B_d : U]$$



cut-set

$$\begin{aligned} [C_b] &= -[B_d]^T \\ [B_d] &= -[C_b]^T \end{aligned}$$

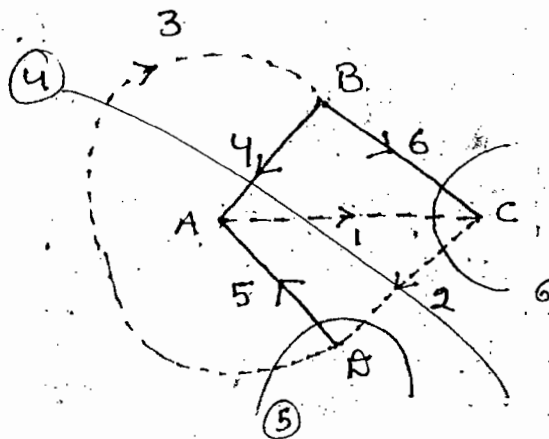Ques:- Develop cut-set matrix of the graph shown



Soln:-


**

	1	2	3	4	5	6
4	-1	+1	-1	+1	..	
5		-1	+1		+1	
6	+1	-1				+1

Ques:- Identify total no. of cut-sets of the graph shown

(a) 3 (b) 4

(c) 5 (d) 6

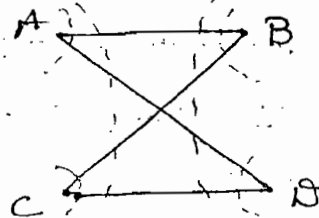



Note:-

- cut-sets may consist of one tree branch or more than one tree branch
- Basic cut-sets consist of only one tree branch

Conclusion:-

- Total no. of possible tree = N^{N-2}
- Tie-set matrix is not unique, total no. of possible tie-set matrix = N^{N-2}
- cut-set matrix is not unique, Total no. of possible cut-set matrix = N^{N-2}
- Rank of Tie-set matrix = total no. of links
i.e. $l = b - (N - 1)$
- Rank of cut-set matrix = total no. of tree branches
 $= N - 1$
- Rank of Incidence Matrix = $N - 1$

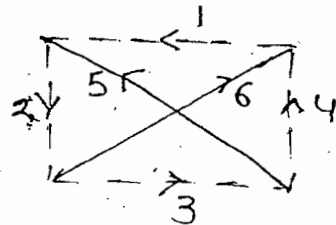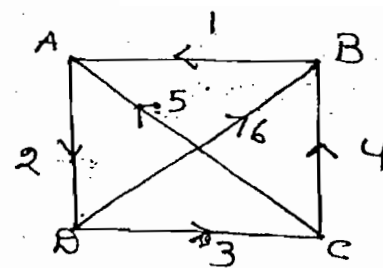- The given figure is invalid tree. Since no connection is present b/w tree branches



Quality:-

- R $\longleftrightarrow$ G
- L $\longleftrightarrow$ C
- V $\longleftrightarrow$ I
- Series $\longleftrightarrow$ Parallel
- O.C $\longleftrightarrow$ S.C
- KVL $\longleftrightarrow$ KCL

loop $\longleftrightarrow$ Node
(Mesh)


Tie-set $\longleftrightarrow$ Cut-set

Thevenin's $\longleftrightarrow$ Norton's


Foster-I form $\longleftrightarrow$ Foster-II form
(Series) (Parallel)

$$\frac{dV}{dt} \longleftrightarrow \frac{dI}{dt}$$
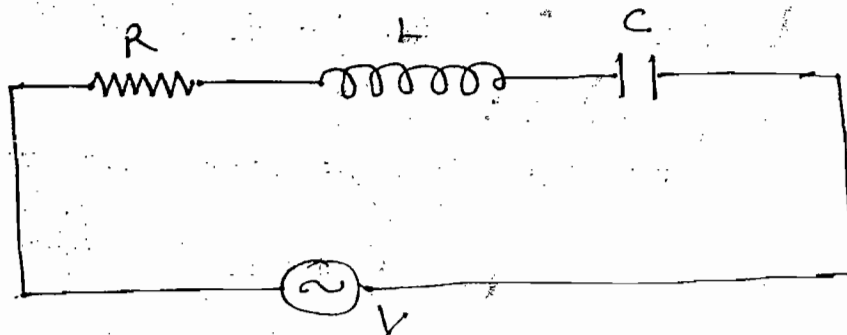
$$\int V dt \longleftrightarrow \int I dt$$



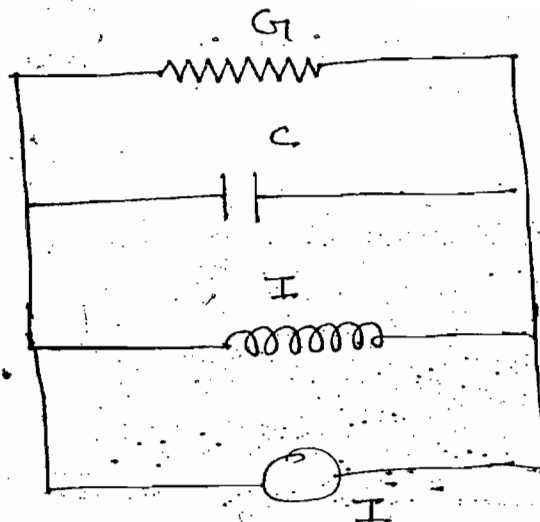
$$V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt \rightarrow \text{KVL}$$




$$I = VG + C \frac{dV}{dt} + \frac{1}{L} \int V dt \rightarrow \text{KCL}$$

Quality does not mean the equivalence but it means that mathematical representation of both N/w are identical.

Ques:- Develop dual of the N/w shown

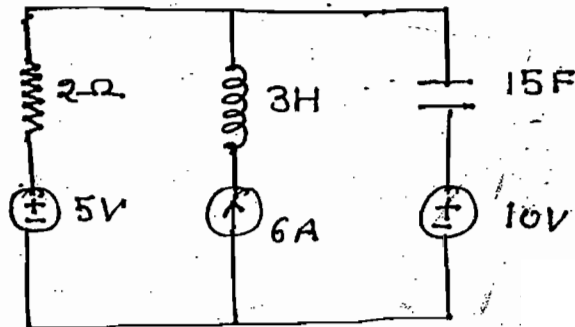

Soln:-

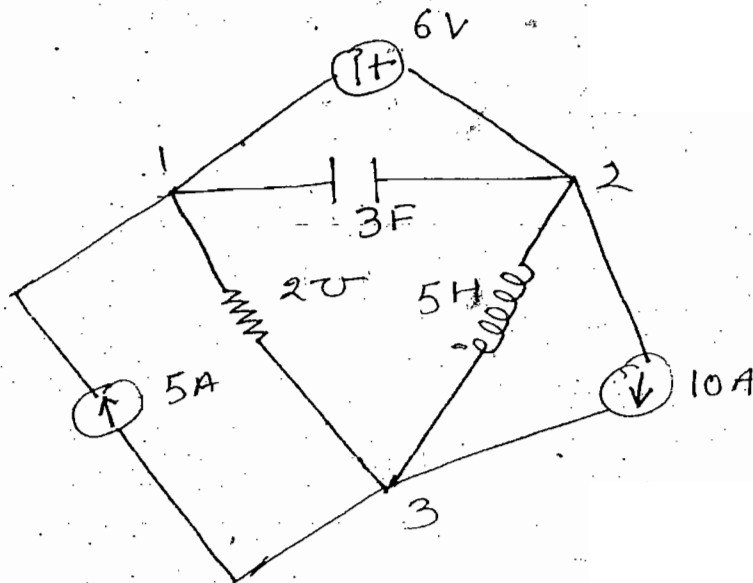

Note:-

- When voltage source circulate a current in clockwise direction arrow mark of the current source is indicated towards respective node
- When current source circulate a current in clockwise direction the sign is assign to respective node