
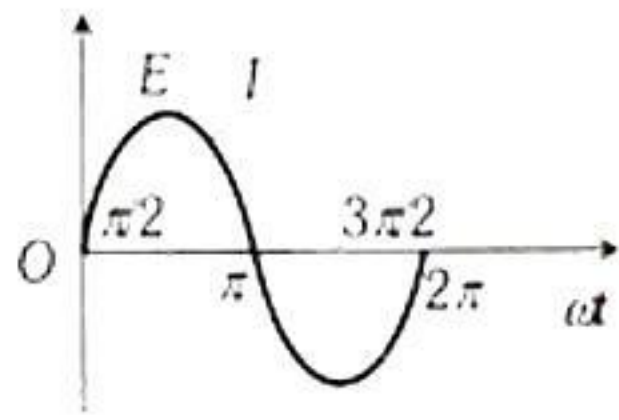


- Q.1** In a series LR-circuit, the inductive reactance is equal to the resistance R of the circuit. An emf $E=E_0\cos(\omega t)$ is applied to the circuit. The power consumed in the circuit is
- (a) E_0^2/R
 - (b) $E_0^2/2R$
 - (c) $E_0^2/4R$
 - (d) $E_0^2/8R$
- Q.2** One 60 V, 100 W bulb is to be connected to 100 V, 50 Hz ac- source. The potential drop across the inductor is ($f=50$ Hz)
- (a) 80 V
 - (b) 40 V
 - (c) 10 V
 - (d) 20 V
- Q.3** An AC voltage source of variable angular frequency and fixed amplitude V connected in series with a capacitance C and an electric bulb of resistance R (inductance zero). When ω is increased
- (a) The bulb glows dimmer
 - (b) The bulb glows brighter
 - (c) Net impedance of circuit is unchanged
 - (d) Total impedance of the circuit increases
- Q.4** An alternating e. m. f. of angular frequency ω is applied across an inductance. The instantaneous power developed across it has an angular frequency
- (a) $\omega/4$
 - (b) $\omega/2$
 - (c) ω
 - (d) 2ω

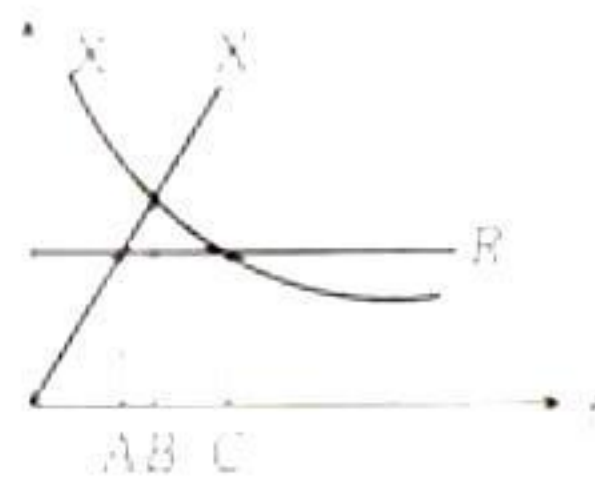- Q.5** The variation of the instantaneous current $I(t)$ and the instantaneous emf $E(t)$ in a circuit is as shown in the following fig. Which of the following statements is correct



- (a) The voltage lags behind the current by $\pi/2$
- (b) The voltage leads the current by $\pi/2$
- (c) The voltage and the current are in phase
- (d) The voltage leads the current by π
- Q.6** The figure shows variation of R, X_L and X_C with frequency f in a series L,C,R circuit. Then for what frequency point, the circuit is inductive.



- (a) A
- (b) B
- (c) C
- (d) A and B
- Q.7** When AC source is connected across series R-C combination, the ac- current may lead ac-voltage by
- (a) 0°
- (b) 180°
- (c) 30°
- (d) 90°
- Q.8** In a purely resistive a.c. circuit, the current
- (a) is in phase with the e.m.f.
- (b) leads the e.m.f. by a difference of π_{radians} phase
- (c) leads the e.m.f. by a phase difference of $\pi/2$ radians
- (d) lags behind the e.m.f. by phase difference of $\pi/4$ radians

- Q.9** A capacitor of capacitance C has reactance X . If capacitance and frequency become double, then the capacitive reactance will be
- (a) $2X$
 - (b) $4X$
 - (c) $X/2$
 - (d) $X/4$
- Q.10** Reactance of a capacitor of capacitance C for an alternating current of frequency $400/\pi$ Hz is 25Ω . The value of C is
- (a) $25\mu\text{F}$
 - (b) $50\mu\text{F}$
 - (c) $75\mu\text{F}$
 - (d) $100\mu\text{F}$
- Q.11** The core of a transformer is laminated, so as to
- (a) make it light weight
 - (b) make it robust and strong
 - (c) increase the secondary voltage
 - (d) reduce energy loss due to eddy current
- Q.12** The ratio of no. of turns of primary coil to secondary coil in a transformer is 2:3. If a cell of 6 V is connected across the primary coil, then voltage across the secondary coil will be
- (a) 3 V
 - (b) 6 V
 - (c) 9 V
 - (d) 12 V
- Q.13** In a transformer, the no. of turns of primary and secondary coil are 500 and 400 respectively. If 220 V is supplied to the primary coil, then ratio of currents in primary and secondary coils is
- (a) 4:5
 - (b) 5:4
 - (c) 5:9
 - (d) 9:5

Q.14 220 V, 50 Hz, AC is applied to a resistor. The instantaneous value of voltage is

- (a) $220\sqrt{2} \sin 100\pi t$
- (b) $220 \sin 100\pi t$
- (c) $220\sqrt{2} \sin 50\pi t$
- (d) $220 \sin 50\pi t$

Q.15 An inductance and a resistance are connected in series with an AC potential. In this circuit

- (a) the current and the potential difference across the resistance lead the PD across the inductance by phase angle $\pi/2$
- (b) the current and the potential difference across the resistance lag behind PD across the inductance by an angle $\pi/2$
- (c) the current and the potential difference across the resistance lag behind the PD across the inductance by an angle π
- (d) the PD across the resistance lags behind the PD across the inductance by an angle $\pi/2$ but the current in the resistance leads the PD across inductance by $\pi/2$

Q.16 An AC voltage is applied to a resistance R and an inductor L in series. If R and the inductive reactance are both equal to 3Ω , the phase difference (in rad) between the applied voltage and the current in the circuit is

- (a) $\pi/4$
- (b) $\pi/2$
- (c) zero
- (d) $\pi/6$

Q.17 In a circuit containing R and L, as the frequency of the impressed AC increases, the impedance of the circuit

- (a) decreases
- (b) increases
- (c) remains unchanged
- (d) first increases and then decreases

Q.18 When an AC voltage is applied to an L-C-R circuit, then

- (a) I and V are out of phase with each other in R
- (b) I and V are in phase in L with in C, they are out of phase
- (c) I and V are out of phase in both, C and L
- (d) I and V are out of phase in L and in phase in C

- Q.19** In a L-C-R series circuit, the potential difference between the terminals of the inductance is 60 V, between the terminals of the capacitor is 30 V and that across the resistance is 40 V. Then, supply voltage will be equal to the
- (a) 50 V
 - (b) 70 V
 - (c) 130 V
 - (d) 10 V
- Q.20** An L-C-R series circuit, connected to a source E, is at resonance. Then,
- (a) the voltage across R is zero
 - (b) the voltage across R equals applied voltage
 - (c) the voltage across C is zero
 - (d) the voltage across C equals applied voltage
- Q.21** A sinusoidal voltage of peak value 300 V and an angular frequency $\omega=400 \text{ rads}^{-1}$ is applied to series L-C-R circuit, in which $R=3\Omega$, $L=20\text{mH}$ and $C=625\mu\text{F}$ The peak current in the circuit is
- (a) $30\sqrt{2} \text{ A}$
 - (b) 60 A
 - (c) 100 A
 - (d) $60\sqrt{2} \text{ A}$

SOLUTION

ALTERNATING CURRENT

(PHYSICS)

DPP – 01
CLASS – 12th
TOPIC – REVISION-01

Sol.1	(C)
Sol.2	(A)
Sol.3	(B)
Sol.4	(D)
Sol.5	(B)
Sol.6	(C)
Sol.7	(C)
Sol.8	(A)
Sol.9	(D)
Sol.10	(D)
Sol.11	(D)
Sol.12	(C)
Sol.13	(A)
Sol.14	(A)
Sol.15	(B)
Sol.16	(A)
Sol.17	(B)
Sol.18	(C)
Sol.19	(A)
Sol.20	(B)
Sol.21	(B)