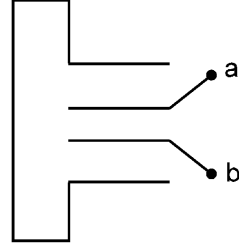


- 293.** Four metallic plates each with a surface area  $A$  of one side and placed at a distance  $d$  from each other. the plates are connected as shown in the fig. Then the capacitance of the system between a and b is -

- (A)  $\frac{3\epsilon_0 A}{d}$  (B)  $\frac{2\epsilon_0 A}{d}$   
(C)  $\frac{2\epsilon_0 A}{3d}$  (D)  $\frac{3\epsilon_0 A}{2d}$



- 294.** Two identical parallel plate capacitors are placed in series and connected to a constant voltage source of  $V_0$  volt. If one of the capacitors is completely immersed in a liquid with dielectric constant  $K$ , the potential difference between the plates of the other capacitor will change to -


- (A)  $\frac{K+1}{K}V_0$  (B)  $\frac{K}{K+1}V_0$  (C)  $\frac{K+1}{2K}V_0$  (D)  $\frac{2K}{K+1}V_0$

- 295.** A number of capacitors each of capacitance  $1\ \mu\text{F}$  and each one of which get punctured if a potential difference just exceeding  $500$  volt is applied, are provided. Then an arrangement suitable for giving a capacitor of  $2\ \mu\text{F}$  across which  $3000$  volt may be applied requires at least-

- (A) 18 component capacitors (B) 36 component capacitors  
(C) 72 component capacitors (D) 144 component capacitors

- 296.** In the given circuit  $C_1 = C$ ,  $C_2 = 2C$ ,  $C_3 = 3C$ . If charge at the capacitor  $C_2$  is  $Q$ . Then the charge at the capacitor  $C_3$  will be -

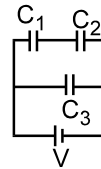- (A)  $\frac{3Q}{2}$  (B)  $\frac{9Q}{2}$   
(C)  $\frac{Q}{3}$  (D)  $\frac{Q}{6}$



- 297.** A capacitor of  $2\ \mu\text{F}$  is charged to its maximum emf of  $2\text{V}$  and is discharged through a resistance of  $10^4\Omega$ . Current in the circuit after  $0.02\text{ s}$  will be-

- (A)  $10^{-4}\text{A}$  (B)  $1.4 \times 10^5\text{ A}$   
(C)  $7.4 \times 10^{-5}\text{A}$  (D)  $3.7 \times 10^{-5}\text{A}$

- 298.** A battery charges a parallel plate capacitor of thickness ( $d$ ) so that an energy  $[U_0]$  is stored in the system. A slab of dielectric constant ( $K$ ) and thickness ( $d$ ) is then introduced between the plates of the capacitor. The new energy of the system is given by -


- (A)  $KU_0$  (B)  $K^2 U_0$  (C)  $\frac{U_0}{K}$  (D)  $U_0/K^2$

- 299.** Two spheres of radii  $R_1$  and  $R_2$  have equal charge are joint together with a copper wire. If the potential on each sphere after they are separated to each other is  $V$ , then

initial charge on any sphere was ( $k = \frac{1}{4\pi\epsilon_0}$ ) -


- (A)  $\frac{V}{k}(R_1 + R_2)$  (B)  $\frac{V}{2k}(R_1 + R_2)$  (C)  $\frac{V}{3k}(R_1 + R_2)$  (D)  $\frac{V}{k} \frac{(R_1 R_2)}{(R_1 + R_2)}$

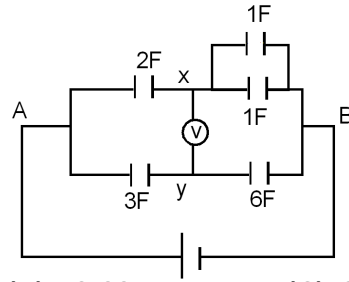- 300.** Calculate the reading of voltmeter between X and Y then  $(V_x - V_y)$  is equal to -




- (A) 10 V      (B) 13.33V      (C) 3.33 V      (D) 10.33 V

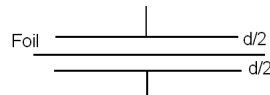- 301.\*** A sheet of aluminium foil of negligible thickness is placed between the plates of a capacitor of capacitance  $C$  as shown in the figure then capacitance of capacitor becomes




- (A)  $2C$       (B)  $C$       (C)  $C/2$       (D) zero
- 302.** In above problem if foil is connected to any one plate of capacitor by means of conducting wire then capacitance of capacitor becomes -
- (A)  $2C$       (B)  $C$       (C)  $C/2$       (D) zero
- 303.** A circuit is shown in the figure below. Find out the charge of the condenser having capacity  $5\mu F$

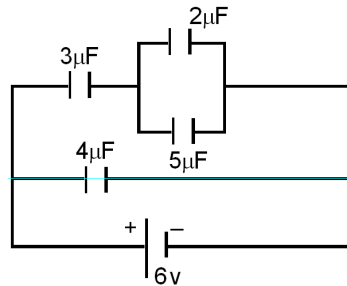- (A) 4.5 micro coulomb  
(B) 6.0 micro coulomb  
(C) 9.0 micro coulomb  
(D) 30 micro coulomb




- 304.** Three capacitors A, B and C are connected to a battery of 25volt as shown in the figure. The ratio of charges on capacitors A

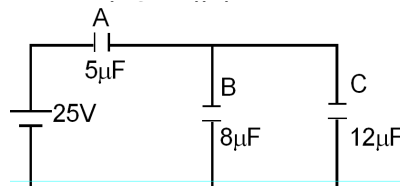- (A) 5 : 2 : 3      (B) 5 : 3 : 2  
(C) 2 : 5 : 3      (D) 2 : 3 : 5




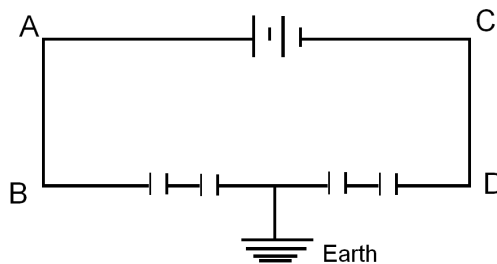- 305.** Four equal capacitors, each with a capacitance  $(C)$  are connected to a battery of E.M.F 10volts as shown in the adjoining figure. The mid point of the capacitor system is connected to earth. Then the potentials of B and D are respectively -



- (A) +10volts, zero volts      (B) +5volts, -5 volts  
(C) -5 volts, +5volts      (D) zero volts, 10 volts

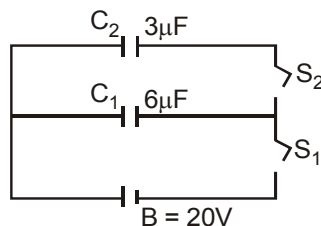
- 306.** In the circuit shown here  $C_1 = 6\mu\text{F}$ ,  $C_2 = 3\mu\text{F}$  and battery  $B = 20\text{V}$ . The Switch  $S_1$  is first closed. It is then opened and afterwards  $S_2$  is closed. What is the charge finally on  $C_2$



- (A)  $120\mu\text{C}$  (B)  $80\mu\text{C}$  (C)  $40\mu\text{C}$  (D)  $20\mu\text{C}$

- 307.** A capacitor of capacity  $C_1$  is charged to the potential of  $V_0$ . On disconnecting with the battery, it is connected with a capacitor of capacity  $C_2$  as shown in the adjoining figure. The ratio of energies before and after the connection of switch  $S$  will be

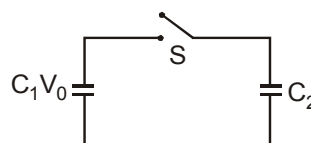- (A)  $(C_1 + C_2)/C_1$  (B)  $C_1/(C_1 + C_2)$   
(C)  $C_1C_2$  (D)  $C_1/C_2$




- 308.** A charge of  $2 \times 10^{-2} \text{ C}$  moves at 30 revolution per second in a circle of diameter 0.80 m. The current linked with the circuit will be -  
(A) 0.1 A (B) 0.2 A (C) 0.4 A (D) 0.6 A

- 309.** The current in a copper wire is increased by increasing the potential difference between its end. Which one of the following statements regarding  $n$ , the number of charge carriers per unit volume in the wire and  $v$  the drift velocity of the charge carriers is correct -  
(A)  $n$  is unaltered but  $v$  is decreased (B)  $n$  is unaltered but  $v$  is increased  
(C)  $n$  is increased but  $v$  is decreased (D)  $n$  is increased but  $v$  is unaltered

- 310.** Consider two conducting wires of same length and material, one wire is solid with radius  $r$ . The other is a hollow tube of outer radius  $2r$  while inner  $r$ . The ratio of resistance of the two wires will be -  
(A) 1 : 1 (B) 1 : 2 (C) 1 : 3 (D) 1 : 4

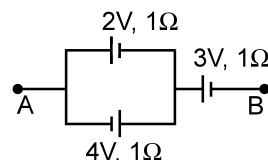- 311.** The potential difference between points A and B is -  
(A) 2 V (B) 6 V  
(C) 4 V (D) 3 V



- 312.** If a copper wire is stretched to make its radius decrease by 0.1%, then the percentage increase in resistance is approximately -  
(A) 0.1% (B) 0.2% (C) 0.4% (D) 0.8%

- 313.** The number of dry cells, each of e.m.f. 1.5 volt and internal resistance  $0.5 \Omega$  that must be joined in series with a resistance of 20 ohm so as to send a current of 0.6 ampere through the circuit is -  
(A) 2 (B) 8 (C) 10 (D) 12

- 314.** The sides of a rectangular block are 2cm, 3cm and 4 cm. The ratio of maximum to minimum resistance between its parallel faces is -  
(A) 4 (B) 3 (C) 2 (D) 1

- 315.** A long resistance wire is divided into  $2n$  parts. Then  $n$  parts are connected in series and the other  $n$  parts in parallel separately. Both combinations are connected to identical supplies. Then the ratio of heat produced in series to parallel combinations will be -  
(A) 1 : 1 (B) 1 :  $n^2$  (C) 1 :  $n^4$  (D)  $n^2$  : 1

- 316.** Two bulbs 100 W, 250 V and 200 W, 250 V are connected in parallel across a 500 V line. Then-
- (A) 100 W bulb will fused
  - (B) 200 W bulb will fused
  - (C) Both bulbs will be fused
  - (D) No bulb will fused

- 317.\*** Two tungsten lamps with resistance  $R_1$  and  $R_2$  respectively at full incandescence are connected first in parallel and then in series, in a lighting circuit of negligible internal resistance. It is given that  $R_1 > R_2$ .

Which lamp will glow more brightly when they are connected in parallel ?

- (A) Lamp having lower resistance
  - (B) Lamp having higher resistance
  - (C) Both the lamps
  - (D) None of the two lamps
- 318.\*** In the previous question which lamp will glow more brightly when they are in connected in series ?
- (A) Lamp having lower resistance
  - (B) Lamp having higher resistance
  - (C) Both the lamps
  - (D) None of the two lamps