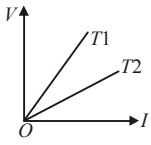



CURRENT ELECTRICITY

MCQs with One Correct Answer

- At what temperature will the resistance of a copper wire becomes three times its value at 0°C ? (Temperature coefficient of resistance of copper is $4 \times 10^{-3}/^\circ\text{C}$)
 - 600°C
 - 500°C
 - 450°C
 - 400°C
- The voltage V and current I graphs for a conductor at two different temperatures T_1 and T_2 are shown in the figure. The relation between T_1 and T_2 is
 
 - $T_1 > T_2$
 - $T_1 < T_2$
 - $T_1 = T_2$
 - $T_1 = \frac{1}{T_2}$
- A cell of emf E is connected across a resistance R . The potential difference between the terminals of the cell is found to be V volt. Then the internal resistance of the cell must be
 - $(E - V)R$
 - $\frac{(E - V)}{V}R$
 - $\frac{2(E - V)R}{E}$
 - $\frac{2(E - V)V}{R}$
- Forty electric bulbs are connected in series across a 220 V supply. After one bulb is fused the remaining 39 are connected again in series across the same supply. The illumination will be
 - more with 40 bulbs than with 39
 - more with 39 bulbs than with 40
 - equal in both the cases
 - None of these

- In a Wheatstone's bridge, three resistances P , Q and R connected in the three arms and the fourth arm is formed by two resistances S_1 and S_2 connected in parallel. The condition for the bridge to be balanced will be
 - $\frac{P}{Q} = \frac{2R}{S_1 + S_2}$
 - $\frac{P}{Q} = \frac{R(S_1 + S_2)}{S_1 S_2}$
 - $\frac{P}{Q} = \frac{R(S_1 + S_2)}{2S_1 S_2}$
 - $\frac{P}{Q} = \frac{R}{S_1 + S_2}$

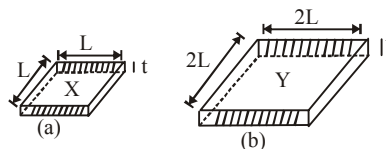
- Figure shows two squares, X and Y, Cut from a sheet of metal of uniform thickness t . X and Y have sides of length L and $2L$, respectively.




The resistance R_x and R_y of the squares are measured between the opposite faces shaded in Fig. What is the value of R_x/R_y ?

- $1/4$
 - $1/2$
 - 1
 - 2
- Two different conductors have same resistance at 0°C . It is found that the resistance of the first conductor at $t_1^\circ\text{C}$ is equal to the resistance of the second conductor at $t_2^\circ\text{C}$. The ratio of the temperature coefficients of resistance of the conductors, $\frac{\alpha_1}{\alpha_2}$ is
 - $\frac{t_1}{t_2}$
 - $\frac{t_2 - t_1}{t_2}$
 - $\frac{t_2 - t_1}{t_1}$
 - $\frac{t_2}{t_1}$

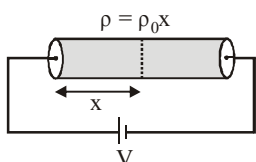8. An electrical cable of copper has just one wire of radius 9 mm. Its resistance is 5 ohm. This single copper wire of the cable is replaced by 6 different well insulated copper wires of same length in parallel, each of radius 3 mm. The total resistance of the cable will now be equal to
- (a) 7.5 ohm (b) 45 ohm
(c) 90 ohm (d) 270 ohm
9. A cylindrical solid of length L and radius a is having varying resistivity given by $\rho = \rho_0 x$, where ρ_0 is a positive constant and x is measured from left end of solid. The cell shown in the figure is having emf V and negligible internal resistance. The magnitude of electric field as a function of x is best described by



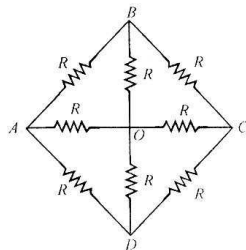- (a) $\frac{2V}{L^2} x$ (b) $\frac{2V}{\rho_0 L^2} x$
(c) $\frac{V}{L^2} x$ (d) None of these
10. In the network shown, each resistance is equal to R . The equivalent resistance between adjacent corners A and D is
- (a) R
(b) $\frac{2}{3} R$
(c) $\frac{3}{7} R$
(d) $\frac{8}{15} R$
11. A current source drives a current in a coil of resistance R_1 for a time t . The same source drives current in another coil of resistance R_2 for same time. If heat generated is same, find internal resistance of source. [given $R_1 > R_2$]



- (a) $\frac{R_1 R_2}{R_1 + R_2}$ (b) $R_1 + R_2$
(c) zero (d) $\sqrt{R_1 R_2}$
12. The length of a wire of a potentiometer is 100 cm, and the e.m.f. of its standard cell is E volt. It is employed to measure the e.m.f. of a battery

whose internal resistance is 0.5Ω . If the balance point is obtained at $\ell = 30$ cm from the positive end, the e.m.f. of the battery is

- (a) $\frac{30E}{100.5}$ (b) $\frac{30E}{(100 - 0.5i)}$
(c) $\frac{30(E - 0.5i)}{100}$ (d) $\frac{30E}{100}$

where i is the current in the potentiometer wire.

13. Two electric bulbs rated P_1 watt V volts and P_2 watt V volts are connected in parallel and V volts are applied to it. The total power will be

- (a) $(P_1 + P_2)$ watt (b) $(\sqrt{P_1 P_2})$ watt
(c) $\left(\frac{P_1 P_2}{P_1 + P_2}\right)$ watt (d) $\left(\frac{P_1 + P_2}{P_1 P_2}\right)$ watt

14. In an experiment of potentiometer for measuring the internal resistance of primary cell a balancing length ℓ is obtained on the potentiometer wire when the cell is open circuit. Now the cell is short circuited by a resistance R . If R is to be equal to the internal resistance of the cell the balancing length on the potentiometer wire will be

- (a) ℓ (b) 2ℓ
(c) $\ell/2$ (d) $\ell/4$

15. In a conductor, if the number of conduction electrons per unit volume is $8.5 \times 10^{28} \text{ m}^{-3}$ and mean free time is 25 fs (femto second), its approximate resistivity is: ($m_e = 9.1 \times 10^{-31} \text{ kg}$)

- (a) $10^{-6} \Omega \text{ m}$ (b) $10^{-7} \Omega \text{ m}$
(c) $10^{-8} \Omega \text{ m}$ (d) $10^{-5} \Omega \text{ m}$


16. Drift speed of electrons, when 1.5 A of current flows in a copper wire of cross section 5 mm^2 , is v . If the electron density in copper is $9 \times 10^{28} / \text{m}^3$ the value of v in mm/s close to (Take charge of electron to be $= 1.6 \times 10^{-19} \text{ C}$)

- (a) 0.02 (b) 3
(c) 2 (d) 0.2


17. A cell of internal resistance r drives current through an external resistance R . The power delivered by the cell to the external resistance will be maximum when :

- (a) $R = 0.001 r$ (b) $R = 1000 r$
(c) $R = 2r$ (d) $R = r$

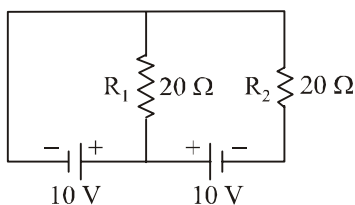18. In the given circuit the cells have zero internal resistance. The currents (in Amperes) passing through resistance R_1 and R_2 respectively, are:



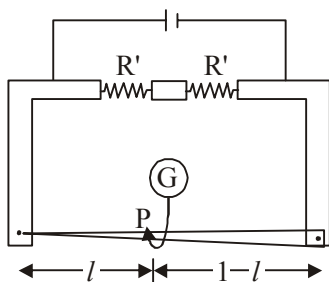
- (a) 1, 2 (b) 2, 2
(c) 0.5, 0 (d) 0, 1
19. In a building there are 15 bulbs of 45 W, 15 bulbs of 100 W, 15 small fans of 10 W and 2 heaters of 1 kW. The voltage of electric main is 220 V. The minimum fuse capacity (rated value) of the building will be:
- (a) 10 A (b) 25 A
(c) 15 A (d) 20 A
20. In a meter bridge, the wire of length 1 m has a non-uniform cross-section such that, the variation $\frac{dR}{dl}$ of its resistance R with length l is $\frac{dR}{dl} \propto \frac{1}{\sqrt{l}}$. Two equal resistances are connected as shown in the figure. The galvanometer has zero deflection when the jockey is at point P. What is the length AP?




- (a) 0.2m (b) 0.3m
(c) 0.25m (d) 0.35m

Numeric Value Answer

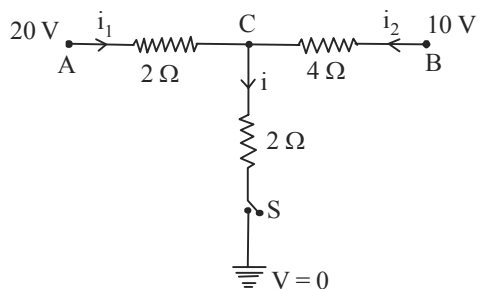21. When the switch S, in the circuit shown, is closed then the value of current i (in ampere) will be:




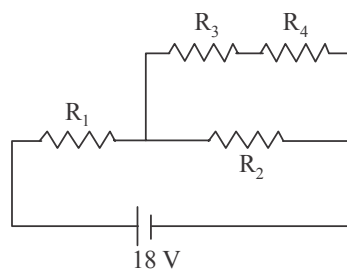22. A 100 watt bulb working on 200 volt has resistance R and a 200 watt bulb working on 100 volt has resistance S . If the R/S is $\frac{8}{x}$. Find the value of x .
23. A copper wire is stretched to make it 0.5% longer. The percentage change in its electrical resistance if its volume remains unchanged is:
24. In the given circuit the internal resistance of the 18 V cell is negligible. If $R_1 = 400\Omega$, $R_3 = 100\Omega$ and $R_4 = 500\Omega$ and the reading of an ideal voltmeter across R_4 is 5 V, then the value of R_2 (in Ω) will be:



25. A uniform metallic wire has a resistance of 18Ω and is bent into an equilateral triangle. Then, the resistance (in Ω) between any two vertices of the triangle is:
26. A 2 W carbon resistor is color coded with green, black, red and brown respectively. The maximum current (in mA) which can be passed through this resistor is:

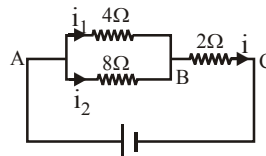27. A current of 2 mA was passed through an unknown resistor which dissipated a power of 4.4 W. Dissipated power (in watt) when an ideal power supply of 11 V is connected across it is:
28. The amount of charge Q passed in time t through a cross-section of a wire is $Q = (5t^2 + 3t + 1)$ coulomb.
The value of current (in ampere) at time $t = 5$ s is
29. A current of 1 mA flows through a copper wire. How many electrons will pass through a given point in each second?
30. In the circuit shown in Fig, the current in $4\ \Omega$ resistance is 1.2 A. What is the potential difference (in volt) between B and C?



ANSWER KEY

1	(b)	4	(b)	7	(d)	10	(d)	13	(a)	16	(a)	19	(d)	22	(1)	25	(4)	28	(53)
2	(a)	5	(b)	8	(a)	11	(d)	14	(c)	17	(d)	20	(c)	23	(1)	26	(20)	29	(6.25×10^{15})
3	(b)	6	(c)	9	(a)	12	(d)	15	(c)	18	(c)	21	(5)	24	(300)	27	(11×10^{-5})	30	(3.6)