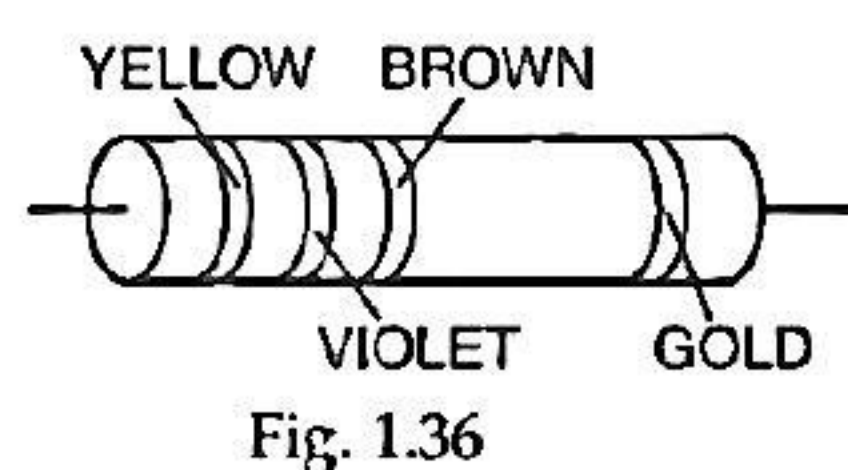


**Q.1** A potential difference of 200 volt is maintained across a conductor of resistance 100 ohm. Calculate the number of electrons flowing through it in one second. Charge on electron,  $e = 1.6 \times 10^{-19}$  C.

**Q.2** A wire of resistance 5 ohm is drawn out so that its length is increased to twice its original length. Calculate its new resistance.

**Q.3** Calculate the electrical conductivity of the material of a conductor of length 3 m, area of cross-section  $0.2 \text{ mm}^2$  having a resistance of 2 ohm.

**Q.4** A carbon resistor has coloured strips as shown in Fig. 1.36. What is its resistance?



**Q.5** How will you represent a resistance of  $37,00 \Omega \pm 10\%$  by colour code?

**Q.6** A series combination of three resistors takes a current of 2 A from a 24 V supply. If the resistors are in the ratio 1 : 2 : 3, find the values of the unknown resistors.

**Q.7** A parallel combination of three resistors takes a current of 5 A from a 20 V supply. If the two resistors are of 10 ohm and 8 ohm, find the value of third one.

**Q.8** A resistor of  $5\Omega$  resistance is connected in series with a parallel combination of a number of resistors each of  $6\Omega$ . If the total resistance of the combination is  $7\Omega$ , how many resistors are in parallel ?

**Q.9** Five resistors are connected as shown in Fig. 1.37. Find the equivalent resistance between the points A and C

**Q.10** Three resistances of  $30 \Omega$  each are connected to form a triangle. A cell of e.m.f. 2 V and negligible internal resistance is connected between any two vertices [Fig.1.39]. Find the current through the cell.

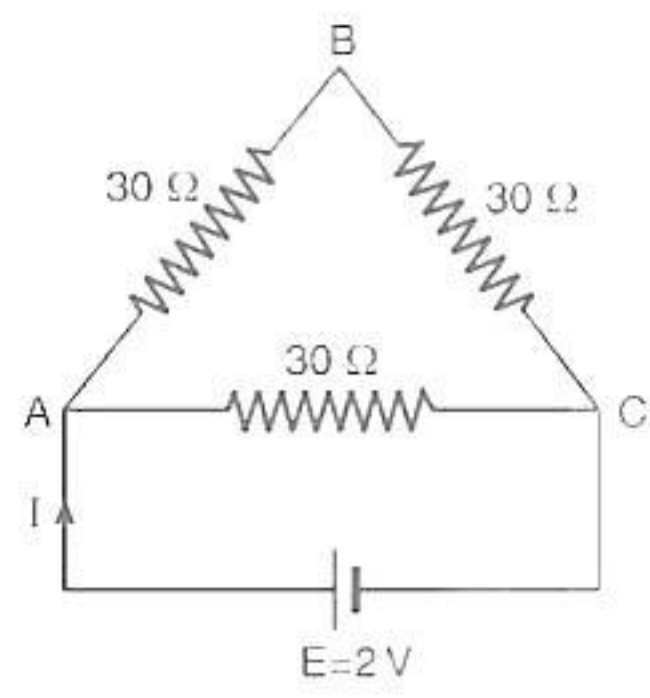


Fig. 1.39

# SOLUTION

(PHYSICS)

## Current Electricity

---

DPP – 02

CLASS – 12<sup>th</sup>

### TOPIC – Ohm's Law & Series Parallel Combination

**Sol.1** Here,  $V = 200$  volt;  $R = 100$  ohm;  $e = 1.6 \times 10^{-19}$  C

$$\text{Now, } I = \frac{V}{R} = \frac{200}{100} = 2 \text{ ampere}$$

The charge flowing in 1 s,

$$q = I t = 2 \times 1 = 2 \text{ C}$$

Therefore, the number of electrons flowing through the conductor in 1s,

$$n = \frac{q}{e} = \frac{2}{1.6 \times 10^{-19}} = 1.25 \times 10^{19}$$

**Sol.2** Let  $l$  be the length and  $A$ , the area of cross-section of the wire. If  $p$  is the resistivity of its material, then

$$R = \rho \frac{l}{A} \quad \dots\dots\dots (i)$$

Suppose that when length of the wire is increased to  $l' (= 2l)$ , its area of cross-section becomes  $A'$ . As the volume of the wire must remain the same, we have

$$A l = A' l' \quad \text{or} \quad A' = \frac{A l}{2 l} = \frac{A}{2}$$

Let  $R'$  be the new resistance of the wire. Then,

$$R' = \rho \frac{l'}{A'} = \rho \frac{2 l}{A/2} = 4 \rho \frac{l}{A}$$

From the equations (i) and (ii), we have

$$R' = 4 R = 4 \times 5 = 20 \, \Omega \quad \therefore R = 5 \, \Omega$$

**Sol.3** Here,  $l = 3$  m;  $A = 0.02 \text{ mm}^2 = 0.2 \times 10^{-6} \text{ m}^2$ ;

$$R = 2 \, \Omega$$

$$\text{Now, } R = \rho \frac{l}{A} \quad \text{or} \quad \rho = \frac{R A}{l}$$

Also, the conductivity of the wire,  $\sigma = \frac{1}{\rho}$



Or 
$$\sigma = \frac{l}{R A} = \frac{3}{2 \times 0.2 \times 10^{-6}} = 7.5 \times 10^6 \text{ S m}^{-1}$$

**Sol.4** Corresponding to first two colour bands of yellow and violet colours, the figures are 4 and 7.

Corresponding to the third band of brown colour, the multiplier is  $10^1$  i.e. 10. Therefore, the given carbon resistor is of value  $47 \times 10$  i.e.  $470 \Omega$ . Since the band showing the tolerance is golden, the value of resistor,

$$R = 470 \Omega \pm 5\%$$

**Sol.5** Here,  $R = 3700 \Omega \pm 10\% = 37 \times 10^2 \Omega \pm 10\% \Omega$

According to colour code of carbon resistance, the colour of bands corresponding to figures 3 and 7 are orange and violet respectively and corresponding to multiplier  $10^2$ , the colour of band is red. Finally, corresponding to tolerance of 10%, the colour of band is silver.

Hence, the resistance of  $37,000 \Omega \pm 10\%$  will be represented by the bands of colour orange, violet, red and silver.

**Sol.6** Here,  $E = 24 \text{ V}; I = 2 \text{ A}$

$$\therefore R_s = \frac{24}{2} = 12 \Omega$$

Let  $R_1$ ,  $R_2$  and  $R_3$  be the resistances of the three unknown resistors. The resistors are in the ratio 1 : 2 : 3 Let  $R_1 = R$ ,  $R_2 = 2R$  and  $R_3 = 3R$ .

$$\text{Now, } R_s = R_1 + R_2 + R_3 \quad \text{or } 12 = R + 2R + 3R$$

$$\text{Or } 6R = 12 \quad \text{or } R = 2$$

$$\text{Hence, } R_1 = 2 \Omega, R_2 = 4 \Omega \text{ and } R_3 = 6 \Omega$$

**Sol.7** Here,  $E = 20 \text{ V}; I = 5 \text{ A}$

$$\therefore R_p = \frac{20}{5} = 4 \Omega$$

Let  $R$  be the unknown resistance. Then,

$$\text{or } \frac{1}{R_p} = \frac{1}{R} + \frac{1}{10} + \frac{1}{8} \quad \text{or } \frac{1}{4} = \frac{1}{R} + \frac{1}{10} + \frac{1}{8}$$

$$\text{or } \frac{1}{R} = \frac{1}{4} - \frac{1}{10} - \frac{1}{8} = \frac{1}{40}$$

$$\text{or } R = 40 \, \Omega$$

**Sol.8** Let  $n$  resistors each of  $6 \, \Omega$  be connected in parallel and then the combination be connected in parallel and then the combination be connected in series with resistor of  $6 \, \Omega$ . The resistance of the parallel combination of  $n$  resistors, each of  $6 \, \Omega$ , is given by

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{6} + \frac{1}{6} \dots n \text{ times} = \frac{n}{6}$$

$$\text{or } R_p = \frac{6}{n} \, \Omega$$

As this parallel combination is connected in series with the resistor of  $5 \, \Omega$ , the total resistance of the combination is given by

$$R = R_p + 5 = \frac{6}{n} + 5$$

Since resistance of the combination is  $7 \, \Omega$ , it follows that

$$\text{or } \frac{6}{n} + 5 = 7 \quad \text{or } \frac{6}{n} = 2$$

$$n = 3$$

**Sol.9** The resistances of segments AB and BC are in series. If  $R_1$  is effective resistance of the part ABC of the circuit, then

$$R_1 = 9 + 5 = 14 \, \Omega$$

Also, the resistances of segment AD and DC are in series. If  $R_2$  is effective resistance of the part ADC of the circuit, then

$$R_2 = 3 + 7 = 10 \, \Omega$$

The resistances  $R_1$ ,  $10 \, \Omega$  (of segment AC) and  $R_2$  are in parallel. If  $R$  is the effective resistance of the circuit, then

$$\frac{1}{R} = \frac{1}{14} + \frac{1}{10} + \frac{1}{10} = \frac{5+7+7}{70} = \frac{19}{70}$$

$$\text{or } R = \frac{70}{19} \, \Omega$$

**Sol.10** The resistances AB and BC are in series. Therefore, their effective resistance,

$$R_1 = 30 + 30 = 60 \, \Omega$$

The effective resistance  $R_1$  ( $= 60 \, \Omega$ ) and the resistance AC ( $= 30 \, \Omega$ ) are in parallel. Therefore, the equivalent resistance of the network is given by

$$R = \frac{60 \times 30}{60 + 30} = 20 \, \Omega$$

If  $I$  is current through the cell, then

$$I = \frac{E}{R} = \frac{2}{20} = 0.1 \text{ A}$$