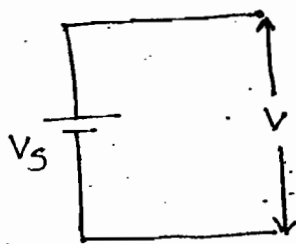



Lecture - 2

PHOTOSTAT
Mob


Ideal Voltage Source



D.C

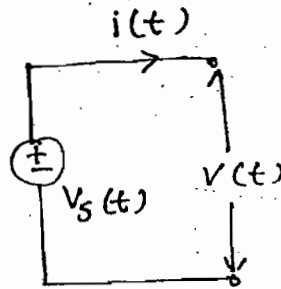


A.C

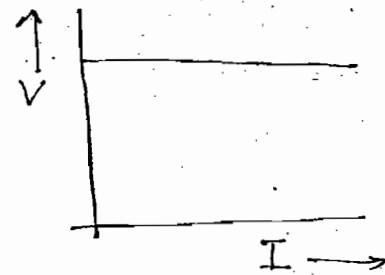


$$\rightarrow R_S = 0$$

$\rightarrow V_S(t) \rightarrow$ either AC or DC if $t \rightarrow$ specify then AC


Practical Voltage Source

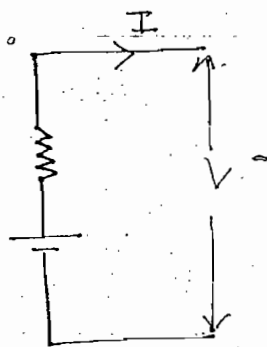

DC

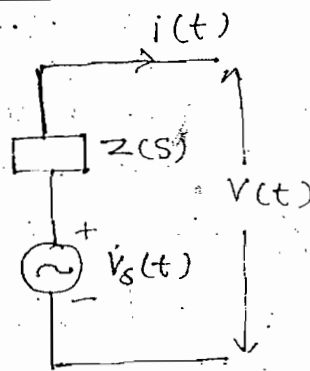

AC

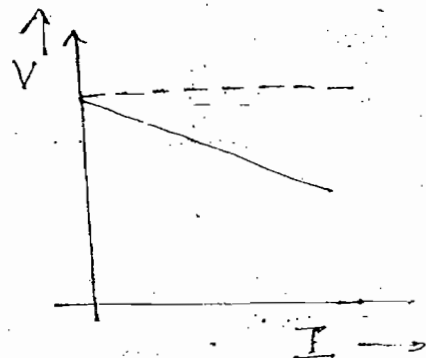

$$V_S = V + IR_S$$

$$V = V_S - IR_S$$

$\rightarrow$ Ideal voltage source delivers energy at a specified voltage (V) it is independent on current deliver by a source











$\rightarrow$ Internal resistance of ideal voltage source is zero

$\rightarrow$ Practical voltage source delivers energy at a specified voltage (V) which depends on current deliver by the source.

→ Linear → characteristic passes through origin and inc. linearly


→ Independent voltage source does not obey the ohm's law. Since V - I characteristic is non-linear.

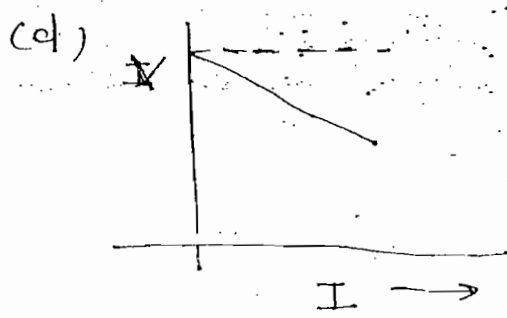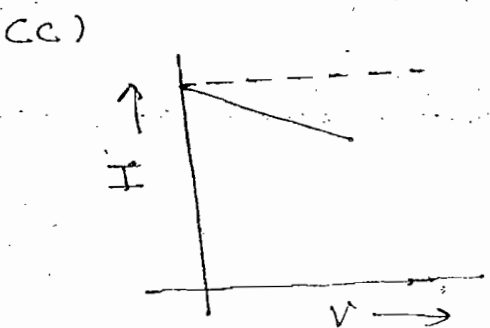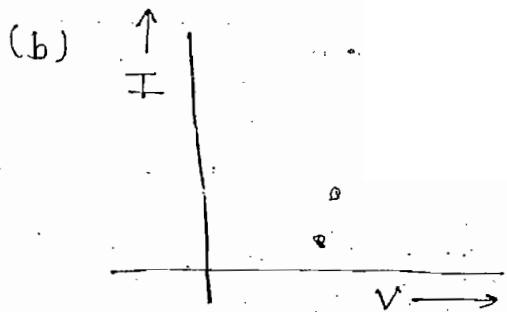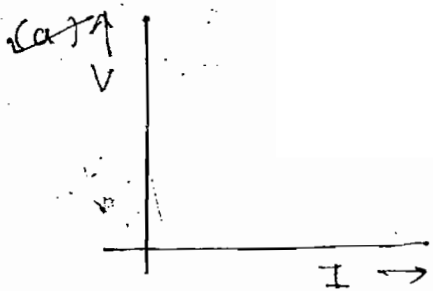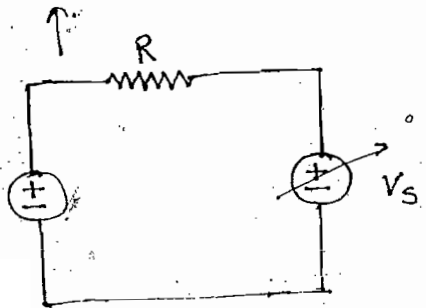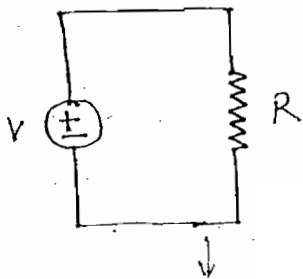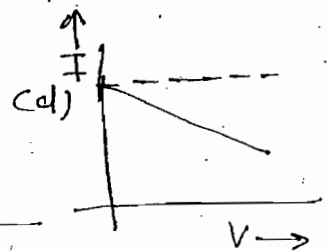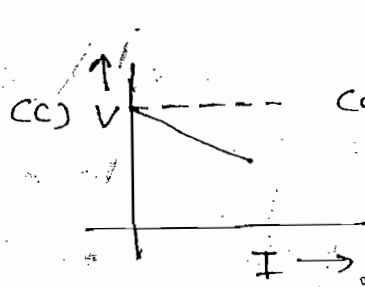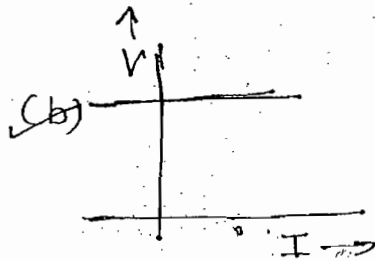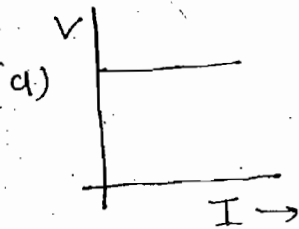Ques:- Identify V - I characteristic of ideal voltage source




Note:-


(i)

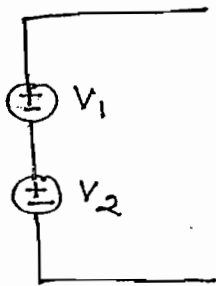



$\approx$

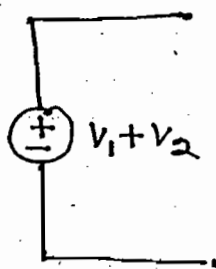


(ii)

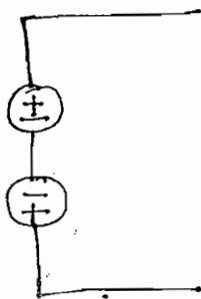


$\approx$

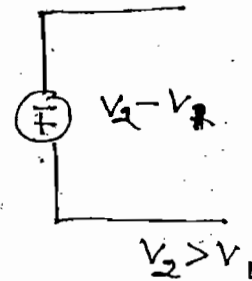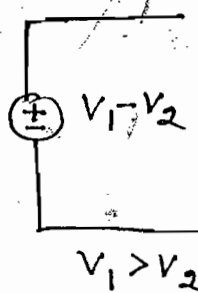


(iii)

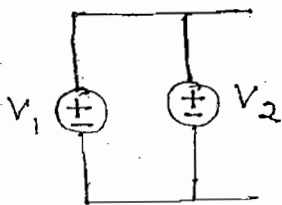


$\approx$

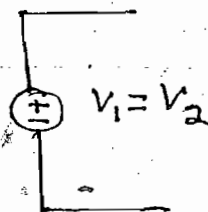


(iv)

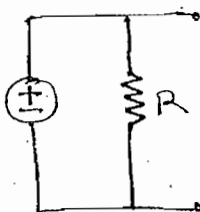


$\approx$

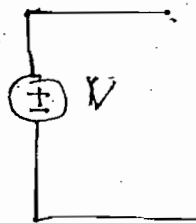

(v)

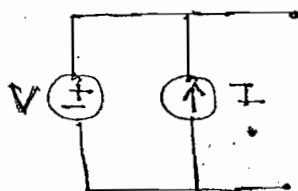


$\approx$

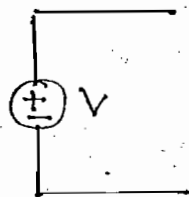

Ques:- Find current in the 2Ω resistor


(a) 5A (b) 10A

(c) 15A (d) None of
Not satisfying
KVL

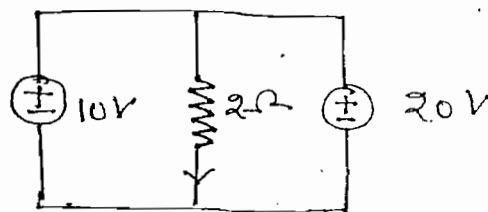


1/1

Note:-

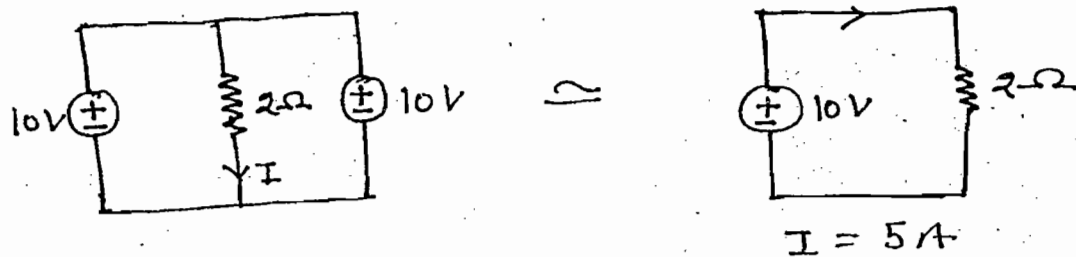


By using superposition theorem

Case - I

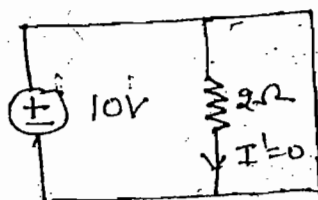


Case - II

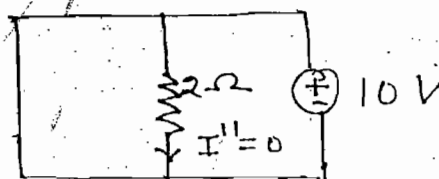

$$I = I' + I'' = 0$$

→ For the above circuit superposition theorem can't be applied since case-(I) & case-(II) circuits are not satisfying KVL

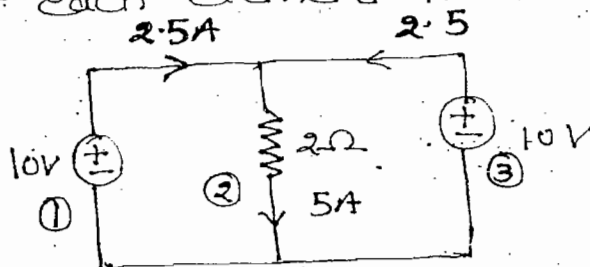Ques:- Find power of each element in the circuit given below



Soln:-

$$P_1 = 10 \times 2.5 = 25 \text{ W (Delivering)}$$


$$P_3 = 10 \times 2.5 = 25 \text{ W (Del.)}$$

$$P_2 = I^2 R = 5^2 \times 2 = 50 \text{ W (Absorbing)}$$

Note:-


$$I_S = 10 + 2 = 12A$$

$$P_S = 20 \times 12 = 240W$$

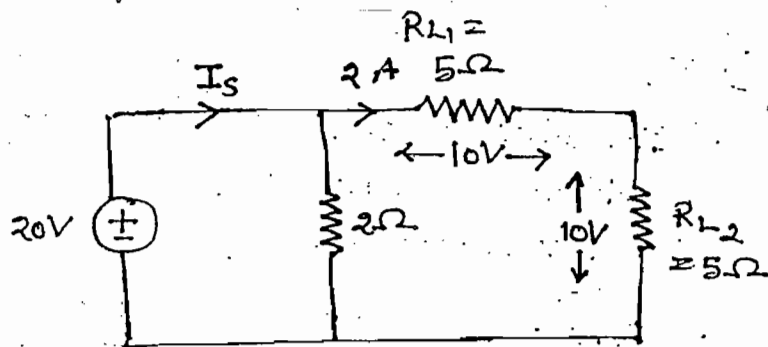

$$I_S' = 2A$$

$$P_S' = 20 \times 2 = 40W$$

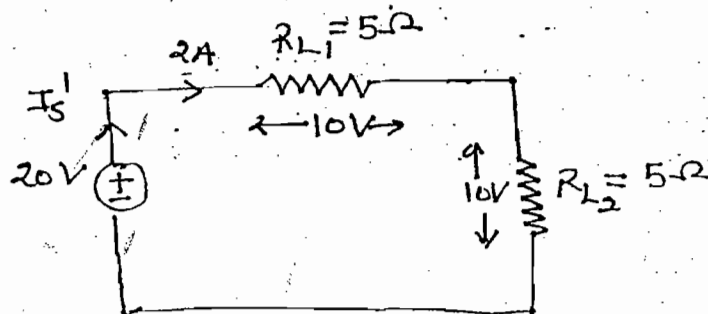

→ In the above circuit 2Ω resistance can be neglected while calculating either load current or load voltages


→ In the above circuit 2Ω resistance can't be neglected while calculating either source current or source power

$$I_S \neq 0.5 = 2$$

$$\Rightarrow I_S = 1.5A$$

$$P_S = 20 \times 1.5$$


$$= 30W$$

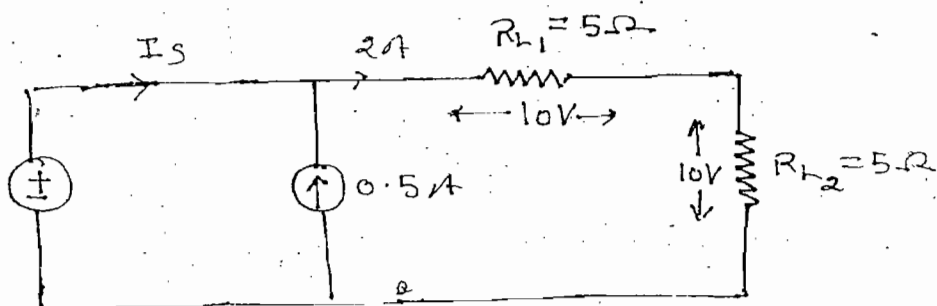

$$I_S' = 2A$$

$$P_S' = 20 \times 2$$

$$= 40W$$

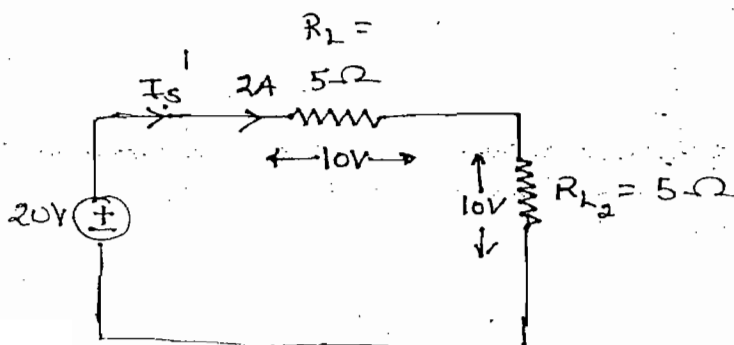


Note:-


→ In the above circuit current source can be neglected while calculating either load current or load voltage.

→ In the above circuit current source can't be neglected while calculating either voltage source current or voltage source power.


Current (I): -

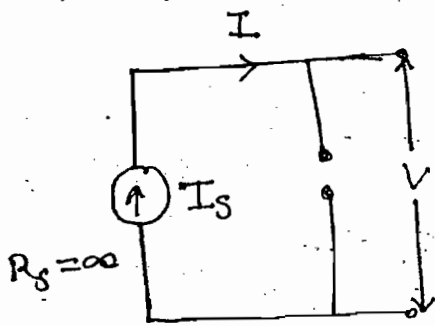




Ideal DC
current source

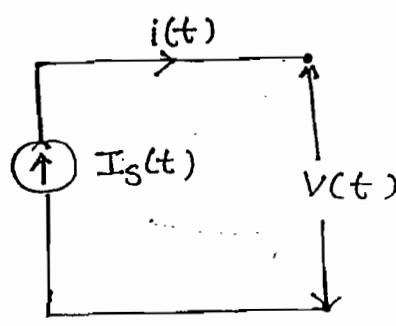

Ideal AC
current source

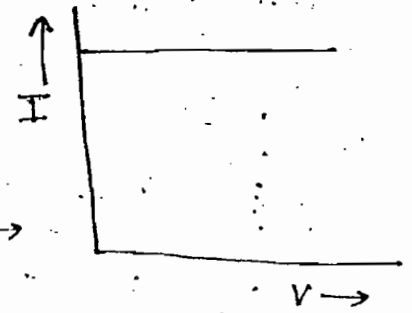

Practical current source: -

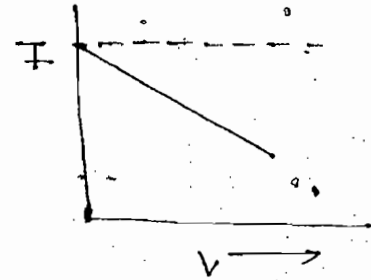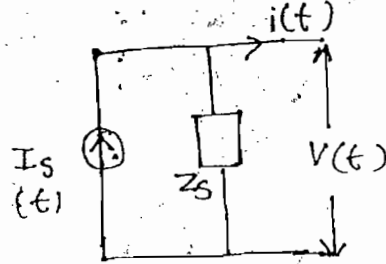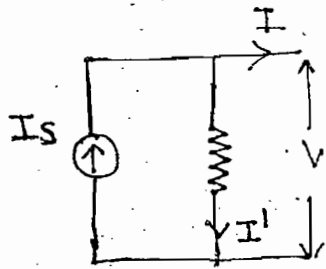






$$I_s = I + I'$$

$$I = I_s - I'$$






$$I = I_s - \frac{V}{R_s}$$

- Ideal current source deliver energy at specified current (I) which is independent on voltage across source
- Internal resistance of ideal current source = ∞
- Practical current source deliver energy at specified current (I) which depends on voltage across source
- Independent current source doesn't obey the ohm's law since $\nabla_{I,V}$ V-I characteristics are non-linear

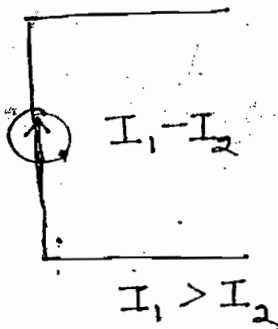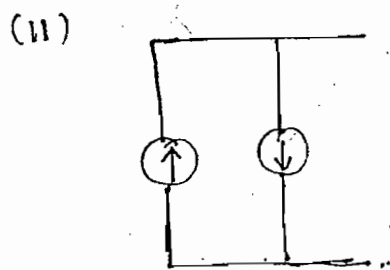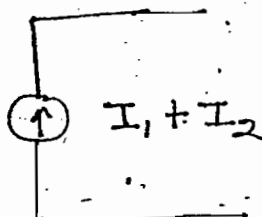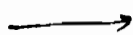
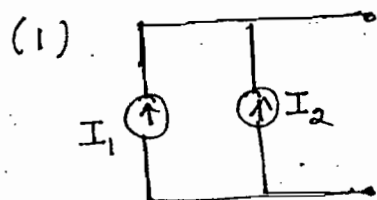
→ In the practical system no independent current source are exist but dependent current source are exist.





OR

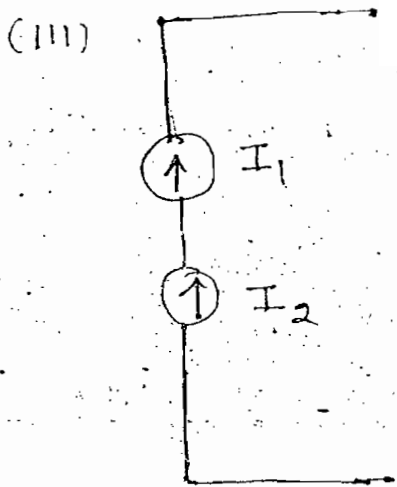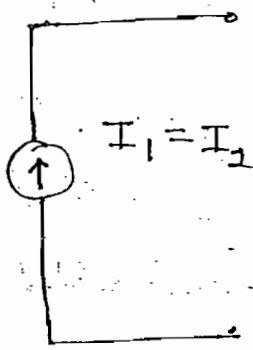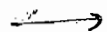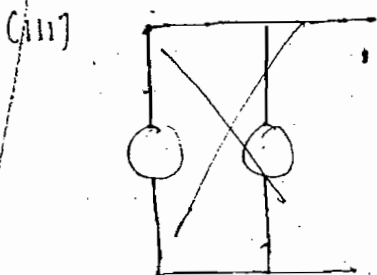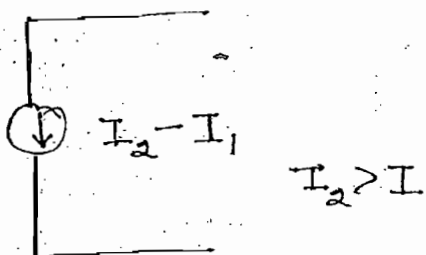


(iv)

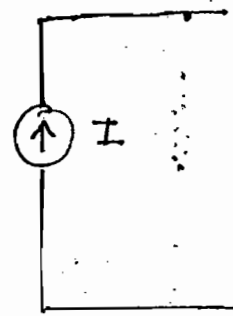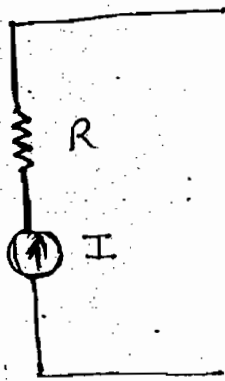

(v)

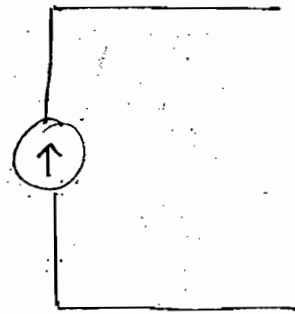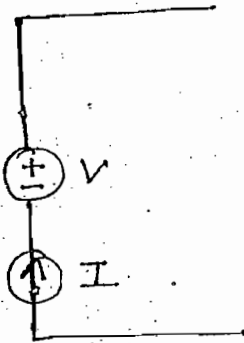

Ques:-

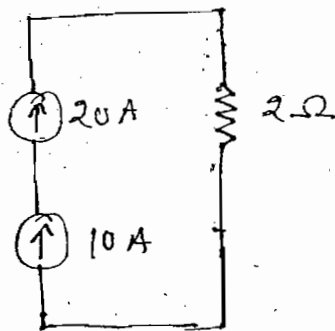

(a) 10 A

(b) 20 A


(c) 30 A

(d) None of these
OR Not satisfied
KCL

Note:-


With respect to KCL current flowing through all the series element should be equal

Ques:-

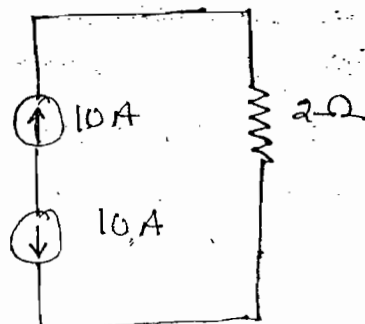

What is the current through 2Ω resistor?

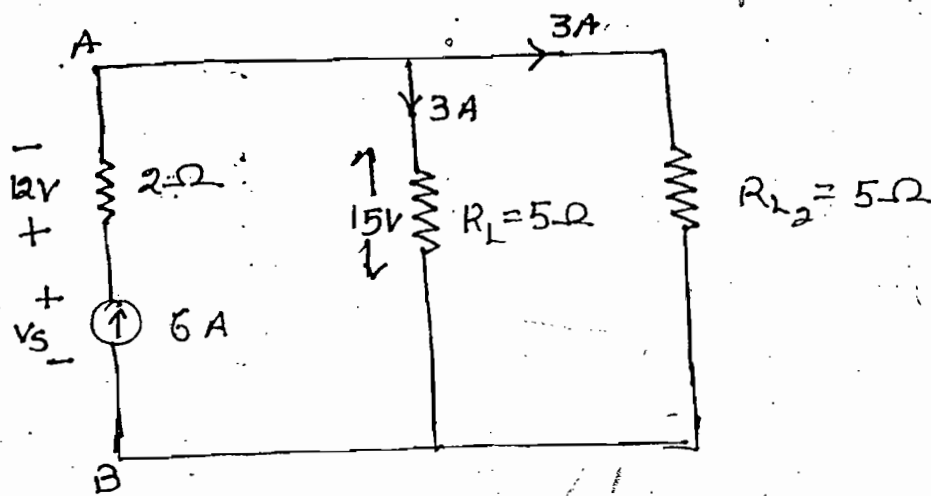Soln:- Not satisfied KCL
bec. polarities are
opposite.




$$V_{AB} = V_S - 12$$

$$\Rightarrow 15 = V_S - 12$$

$$\Rightarrow V_S = 27$$
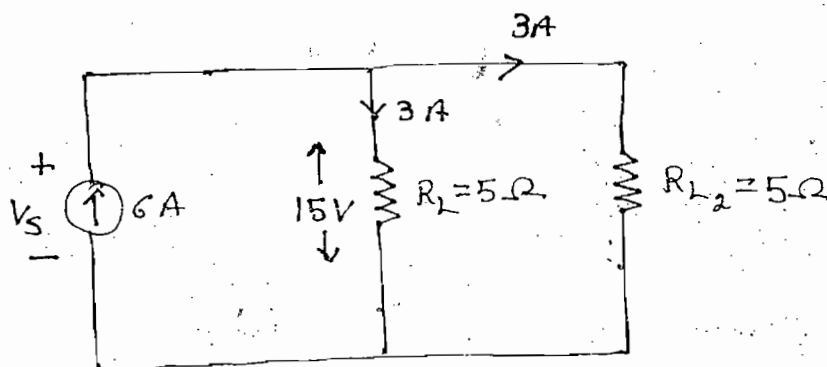
$$\therefore P_S = 27 \times 6 = 162 \text{ W}$$



$$V_S' = 15V \quad P_S' = 15 \times 6 = 90W$$

Note:-

- In the above circuit 2Ω resistance can be neglected either by calculating load current or load voltage.
- In the above circuit 2Ω resistance can't be neglected by calculating either voltage across current source or power of the current source.




Note:-

- In above circuit voltage source can be neglected by calculating either load current or load voltage
- In the above circuit voltage source cannot be neglected ~~to~~ either calculating voltage across current source or power of the current source

KCL:-

- Based on law of conservation of charge

$$I_1 + I_3 + I_6 = I_2 + I_4 + I_5$$

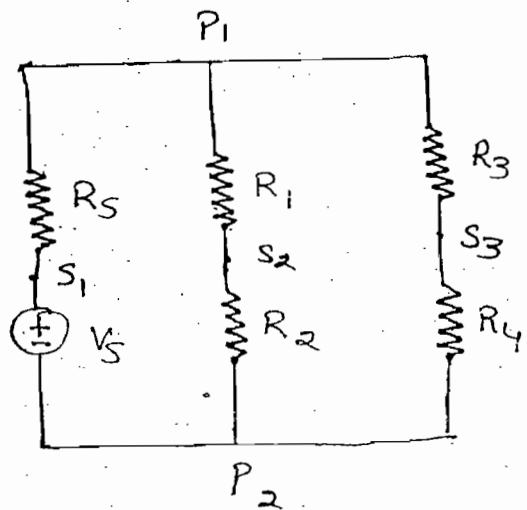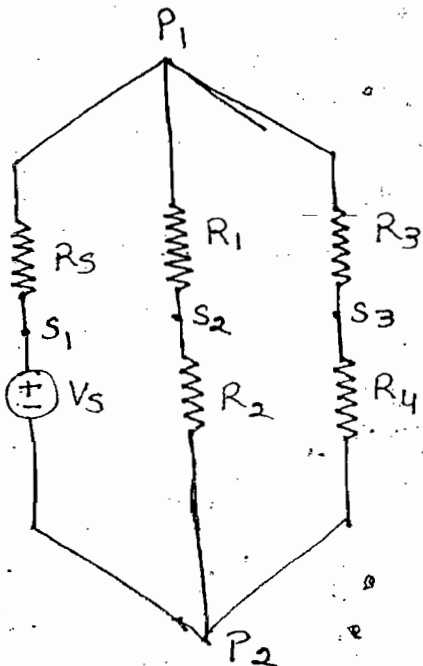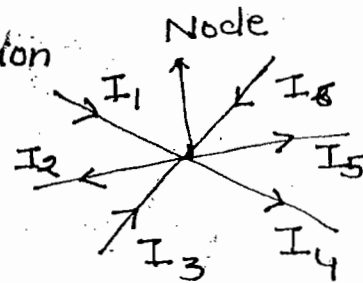


- KCL states that algebraic sum of currents meeting at a point is equal to zero.
- When two elements are connected together then common point is called as simple node
- When more than two elements are connected together then common point is called as principal node.

Current division technique:-

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$I_1 = I \frac{R_2}{R_1 + R_2}$$


$$I_2 = I \frac{R_1}{R_1 + R_2}$$

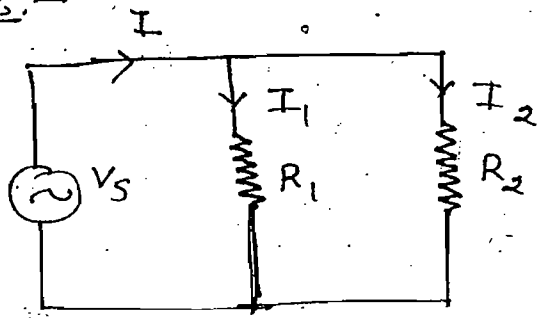

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$I_1 = I \frac{L_2}{L_1 + L_2}$$


$$I_2 = I \frac{L_1}{L_1 + L_2}$$

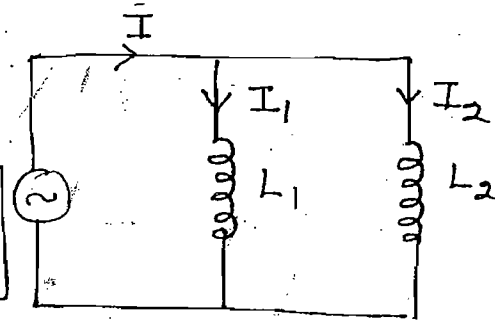


$$C_{eq} = C_1 + C_2$$

$$I_1 = I \frac{C_1}{C_1 + C_2}$$

$$I_2 = I \frac{C_2}{C_1 + C_2}$$

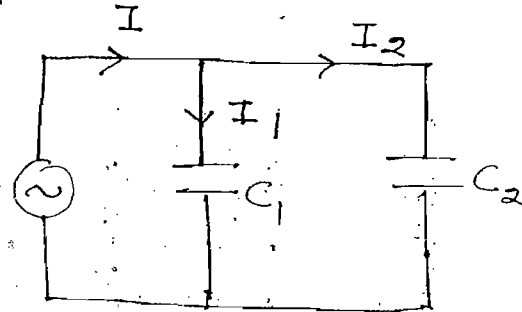

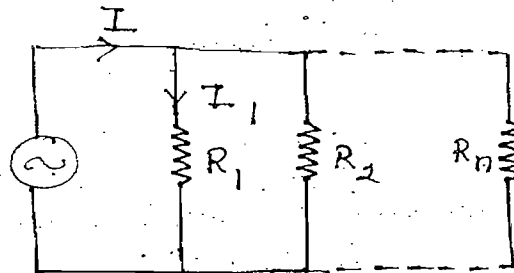
$$I_1 = I \frac{1/R_1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$



KVL :-


→ KVL works based on the principle of law of conservation of energy

$$V_1 + V_2 + V_3 - V_s = 0$$

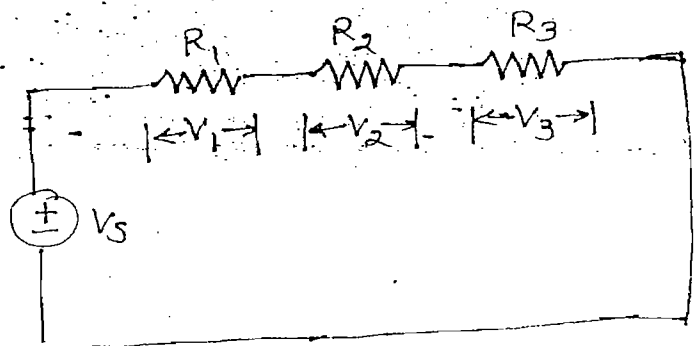


$$V_{S1} - V_1 - V_{S3} + V_2 = 0$$

$$V_{S1} + V_2 = V_1 + V_{S3}$$

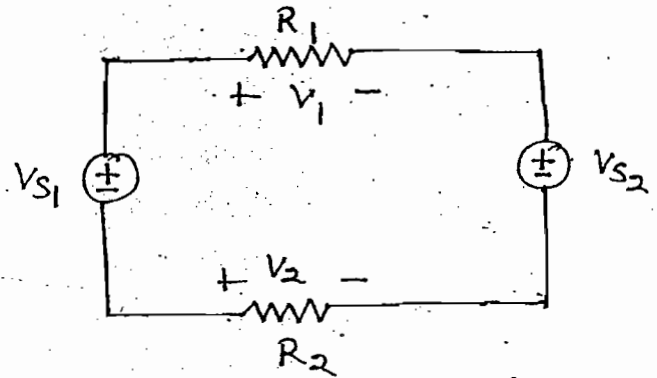

→ KVL states that algebraic sum of voltages in a closed loop is equal to zero

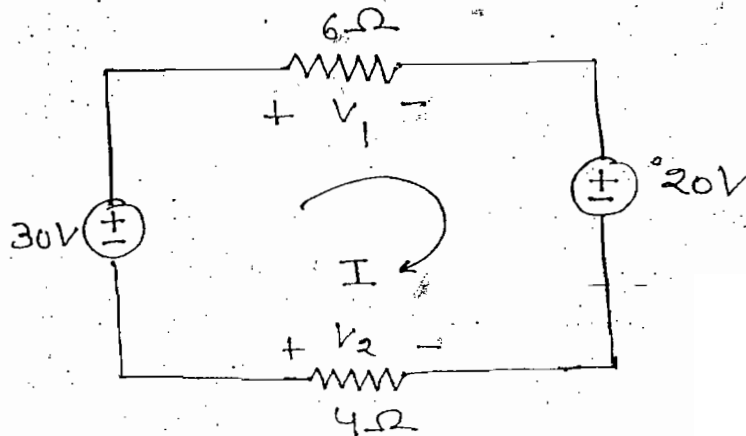Ques:- Find V_1 & V_2 of the circuit shown



Soln:-

$$V_1 = 6I \quad V_2 = -4I$$

$$30 - V_1 + 20 - V_2 = 0$$

$$\Rightarrow -30 + 6I + 20 - (-4I) = 0$$

$$\Rightarrow I = 1A$$


$$V_1 = 6V \quad \& \quad V_2 = -4V$$

Voltage Division Technique:-

$$R_{eq} = R_1 + R_2$$

$$V_1 = V_s \frac{R_1}{R_1 + R_2}$$


$$V_2 = V_s \frac{R_2}{R_1 + R_2}$$

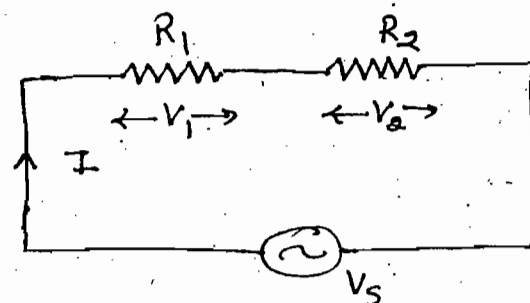

$$L_{eq} = L_1 + L_2$$

$$V_1 = V_s \frac{L_1}{L_1 + L_2}$$


$$V_2 = V_s \frac{L_2}{L_1 + L_2}$$

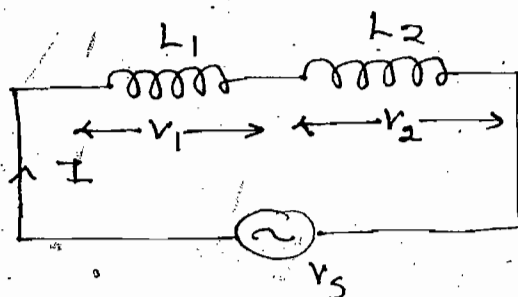


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$V_1 = V_s \frac{C_2}{C_1 + C_2}$$

$$V_2 = V_s \frac{C_1}{C_1 + C_2}$$

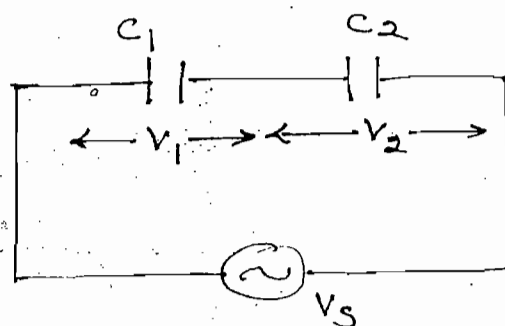


Conclusions:-

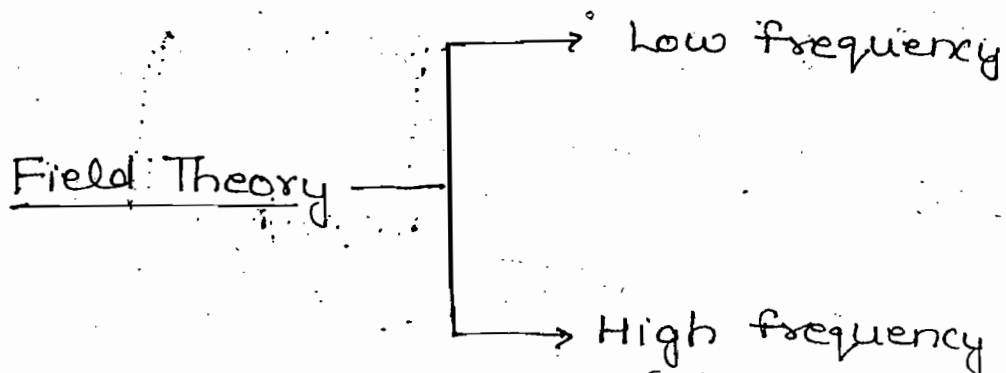



Network Theory → Low frequency

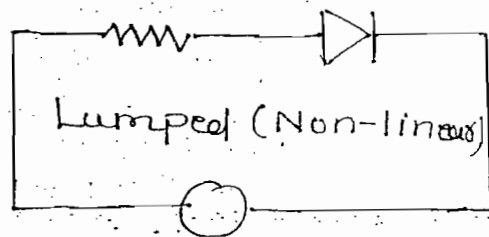- Field theory can be applied for low or high frequency application
- In field theory accurate results are obtained but developing mathematical equation is complex
- Network theory is applied only for low frequency applications
- In the network theory approximate results are obtained and developing mathematical equation is simple
- KVL and KCL fails for high frequencies application



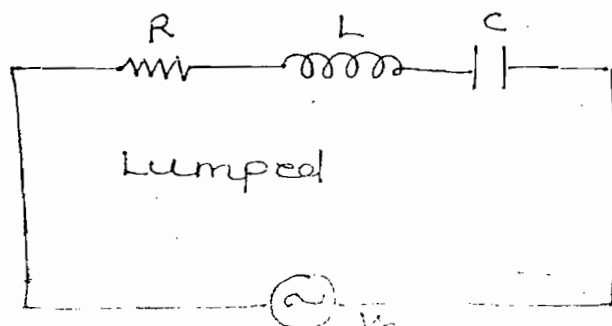
$$V_s = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$



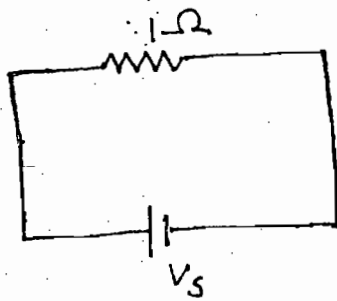


Lumped
(Linear)

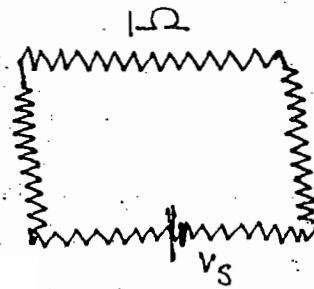

Distributed

$$J = \sigma E$$


(Ohm's Law)

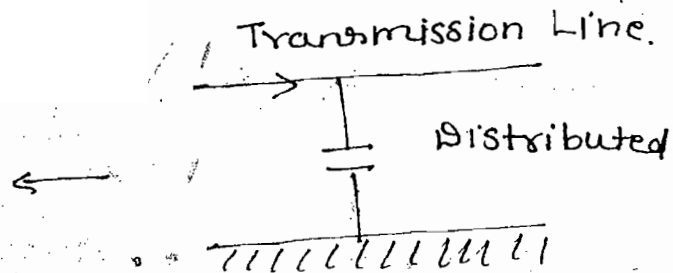

- Ohm's law can be applied lumped (linear) and distributed parameters
- KVL and KCL fails for distributed parameters since in the distributed parameters electrically it is not possible to separate resistance, inductance and capacitance effects
- KVL and KCL are applied for lumped parameters (Linear, non-linear, uni-directional, bi-directional, time variant and invariant elements)


Ques:-

$$L_{eq} = ?$$

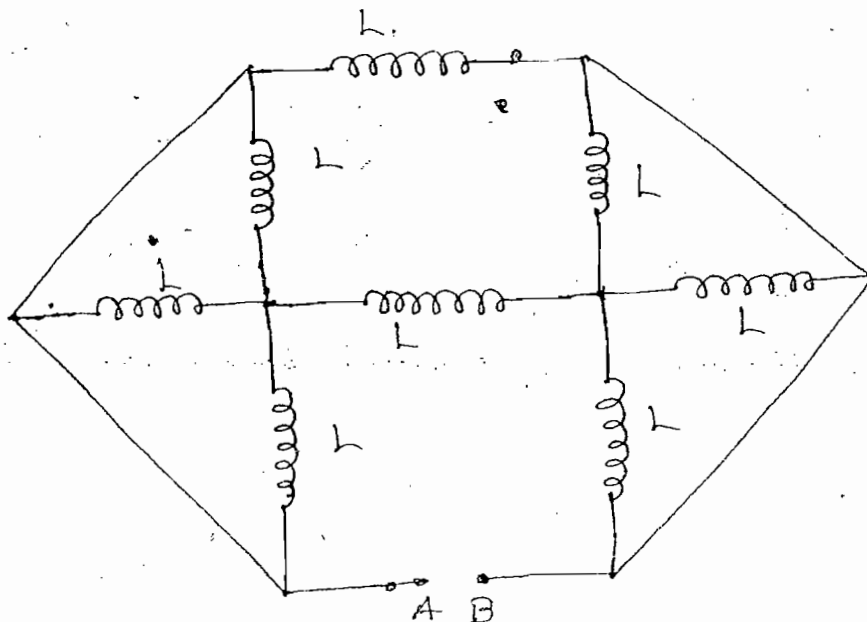


Note:-


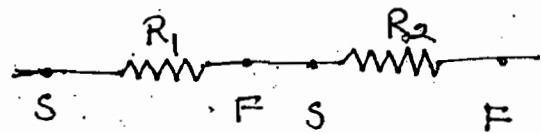
- (i) one joint
- (ii) $I \rightarrow$ same



- (i) Twice
- (ii) $V \rightarrow$ same

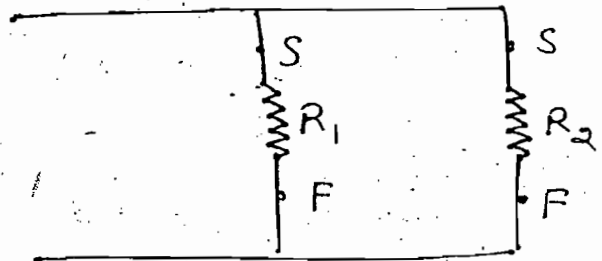



Soln:-

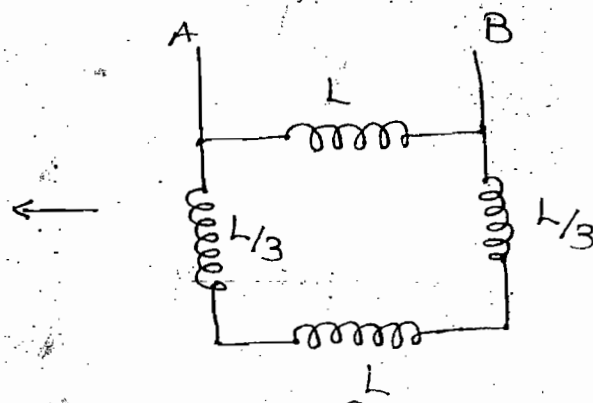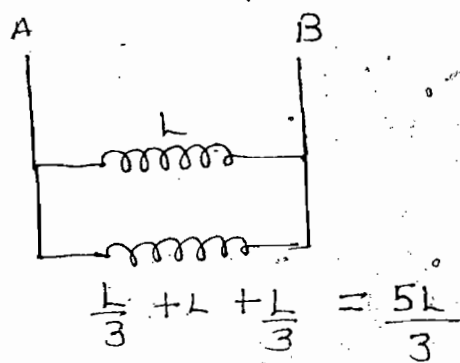

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2} = \frac{5L}{8}, \text{Ans}$$


Ques:- Find equivalent capacitance w.r.t A & B

Soln:-

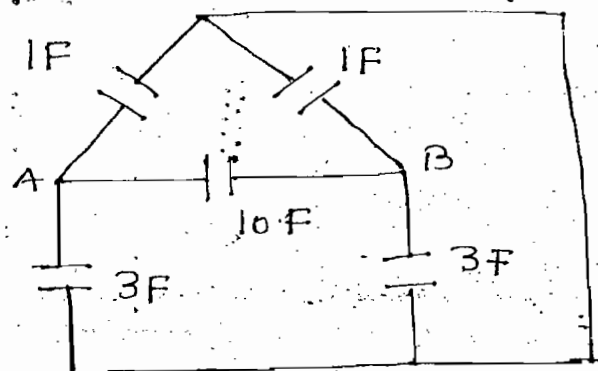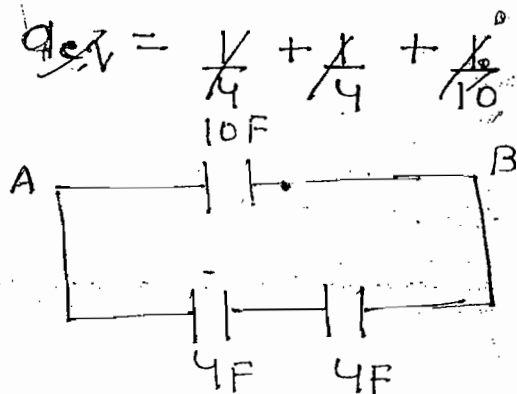

$$C_{eq} = 10 + 2 = 12 F$$

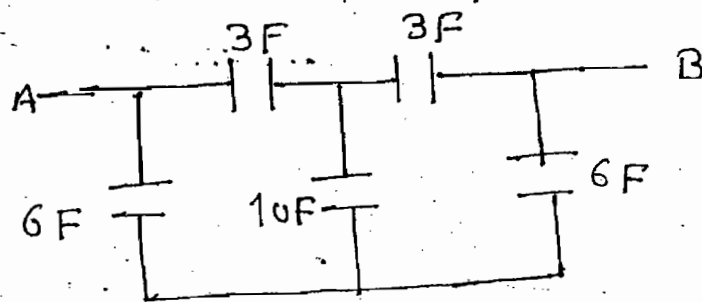
Ques:- Find equivalent capacitance w.r.t A & B




Soln:-

Balanced bridge


$$Z_1 Z_4 = Z_2 Z_3$$

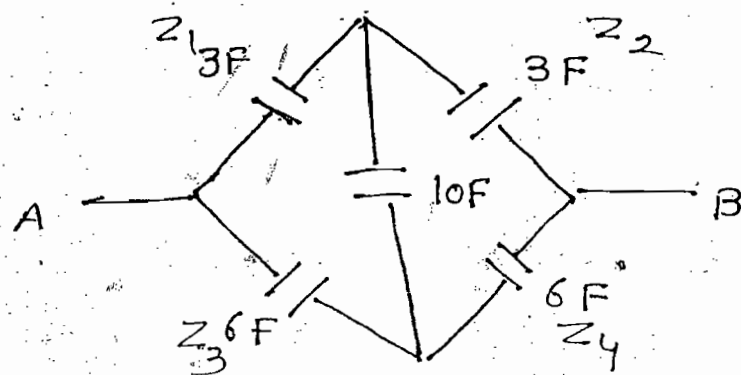


$$C_{eq} = 3 + 1.5 = 4.5F, \text{ Ans}$$

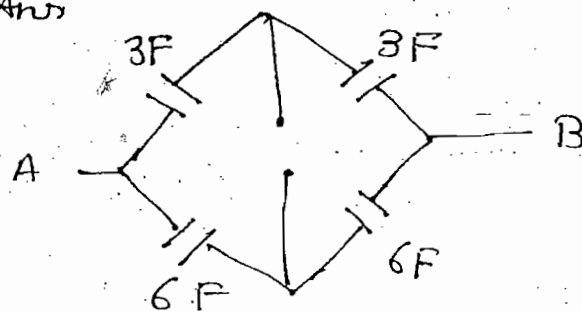


Ques:- Find I of the circuit shown

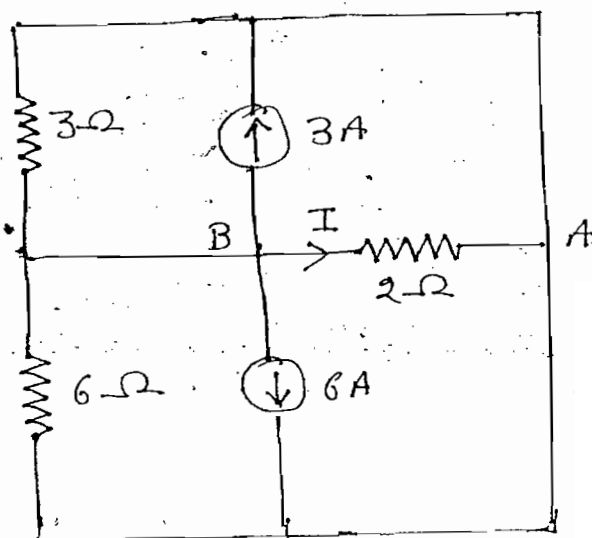


Soln:-

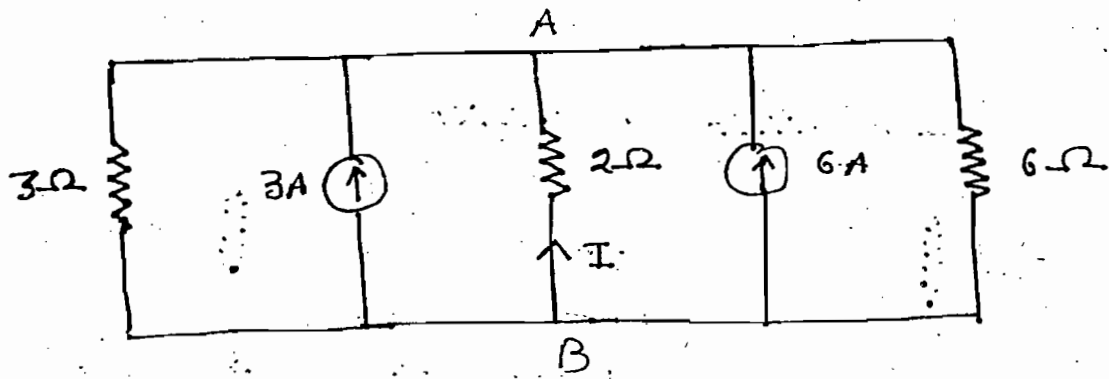

$$I = -4.5A$$

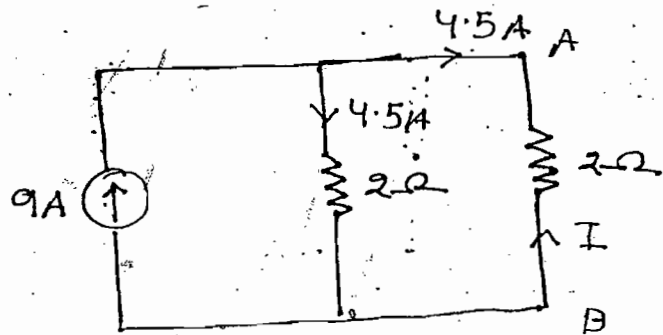

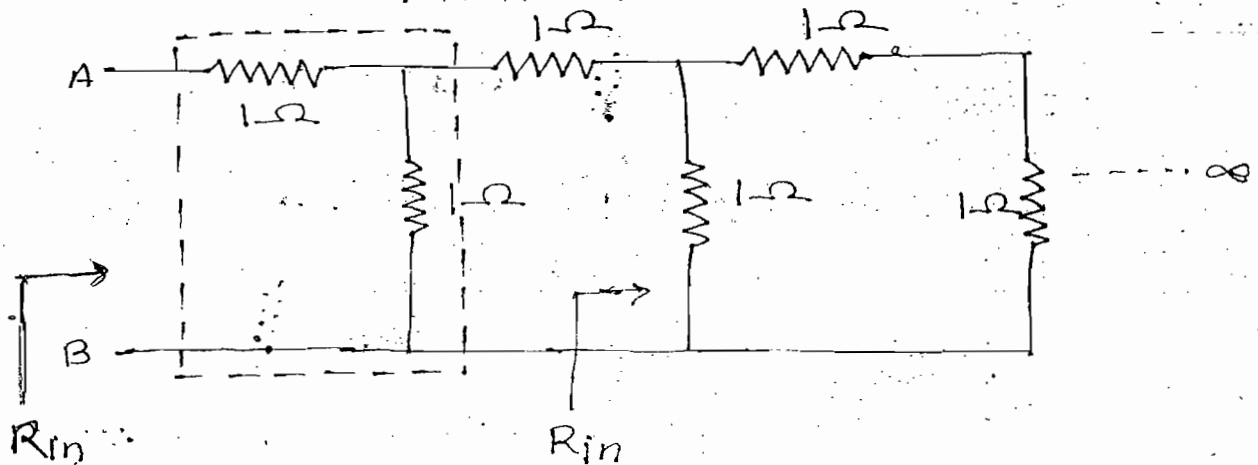Ques:- Find the equivalent resistance w.r.t A & B



Soln:-


$$R_{in} = 1 + \frac{1 \times R_{in}}{1 + R_{in}}$$

$$R_{in} = \frac{1 + R_{in} + R_{in}}{1 + R_{in}}$$


$$\Rightarrow R_{in}^2 - R_{in} - 1 = 0$$

$$R_{in} = \frac{1 + \sqrt{5}}{2}$$

, Ans

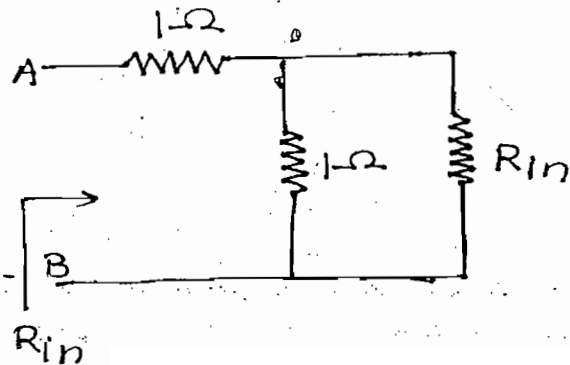

Ques:- Find I of the circuit shown


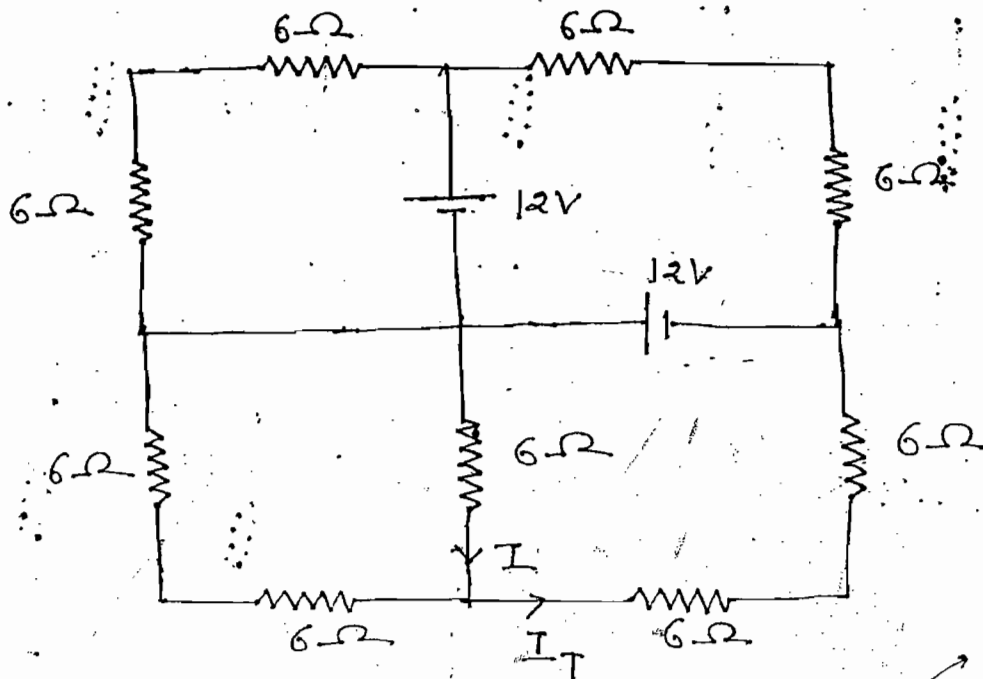


Soln:-

$$I_T = \frac{12}{4+12}$$

$$I = I_T \frac{12}{12+6}$$
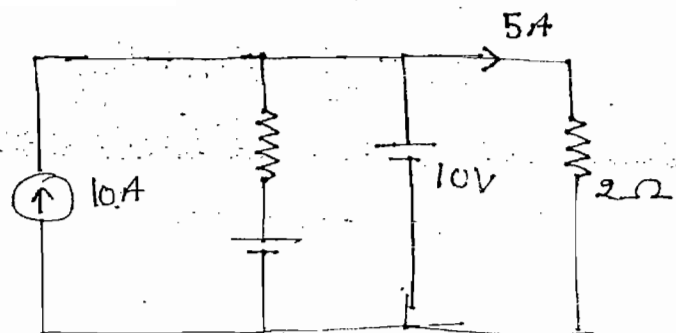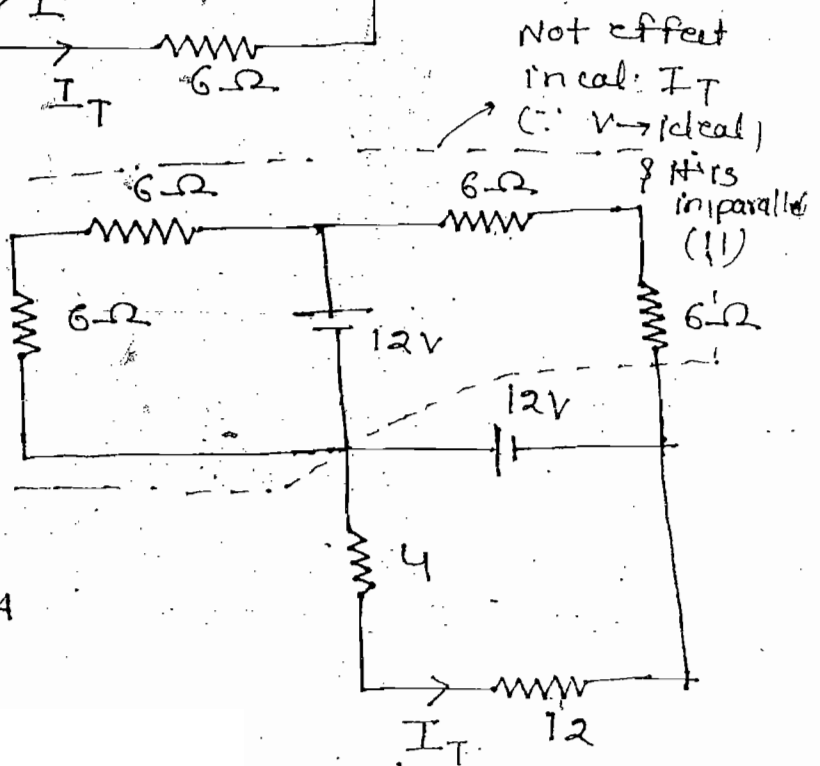
$$= \frac{12}{16} \times \frac{12}{18} = 0.5A$$




ques:- When two capacitance $40F$ & $20F$ are connected in series with a source voltage $90V$

When two capacitor charged fully then they are connected in parallel. Find voltage across capacitor in parallel branch.

(a) $40V$ (b) $60V$ (c) $45V$ (d) $30V$

Soln:-

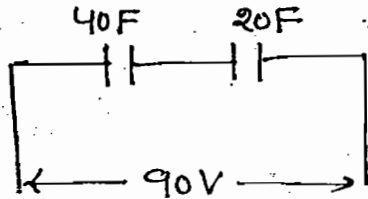

$$C_{eq} = \frac{40 \times 20}{40 + 20} = \frac{40}{3}$$

$$Q = C_{eq} V = \frac{40}{3} \times 90 = 1200C$$


$$Q_T = 1200 + 1200 = 2400C$$

$$Q_T = 2400$$

$$C_{eq} = 40 + 20 = 60$$

$$V = \frac{Q_T}{C_{eq}} = \frac{2400}{60}$$


$$= 40V, \text{ Ans}$$





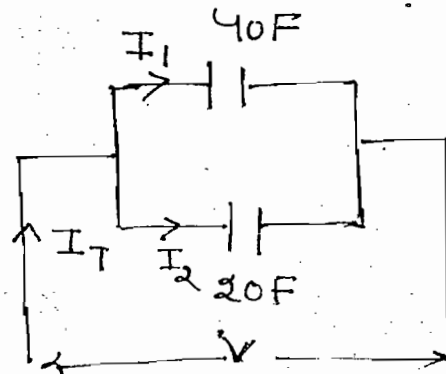


ques:-


Note:-

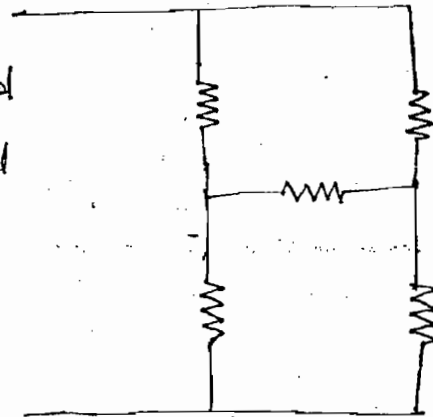When elements are connected not in series nor in parallel network is reduced by Star-delta transformation



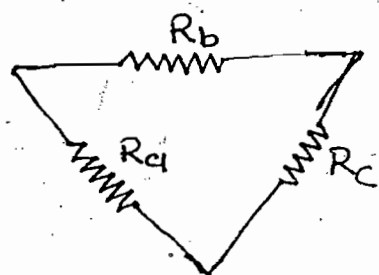 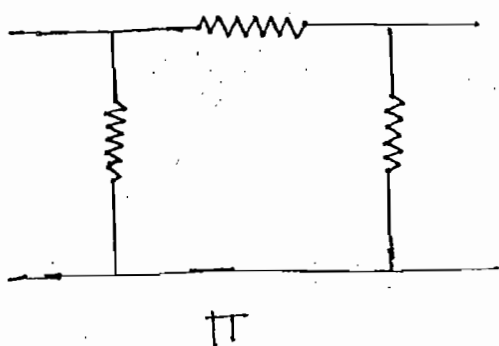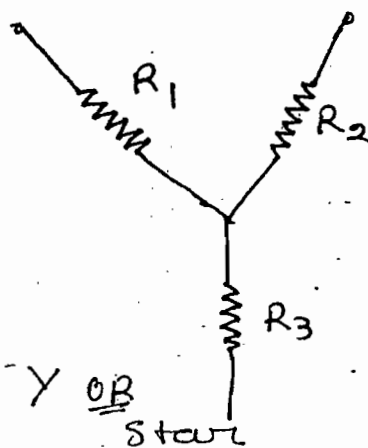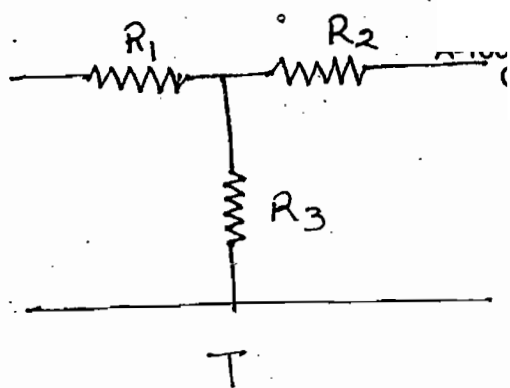

Delta or Mesh

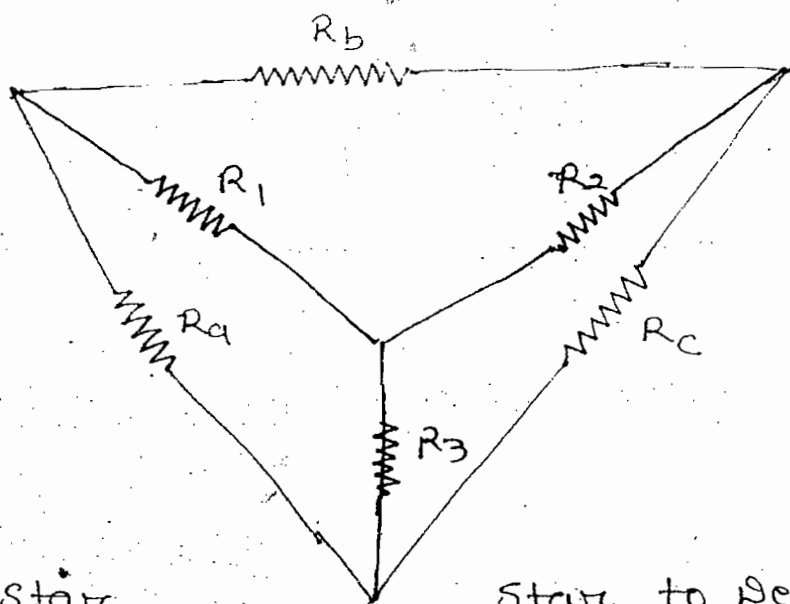

Delta to Star

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$


Star to Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

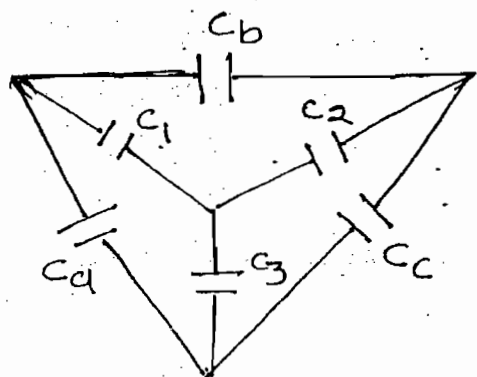→ The procedure of transformation either from delta to star or star to delta for the resistor, inductor and impedance is same



Delta to Star:-

$$\frac{1}{C_1} = \frac{\frac{1}{C_a} \cdot \frac{1}{C_b}}{\frac{1}{C_a} + \frac{1}{C_b} + \frac{1}{C_c}}$$

$$\frac{1}{C_2} = \frac{\frac{1}{C_b} \cdot \frac{1}{C_c}}{\frac{1}{C_a} + \frac{1}{C_b} + \frac{1}{C_c}}$$

$$\frac{1}{C_3} = \frac{\frac{1}{C_a} \cdot \frac{1}{C_c}}{\frac{1}{C_a} + \frac{1}{C_b} + \frac{1}{C_c}}$$

Star to Delta:-

$$\frac{1}{C_a} = \frac{\frac{1}{C_1} \frac{1}{C_2} + \frac{1}{C_2} \frac{1}{C_3} + \frac{1}{C_3} \frac{1}{C_1}}{\frac{1}{C_2}}$$

$$\frac{1}{C_b} = \frac{\frac{1}{C_1} \frac{1}{C_2} + \frac{1}{C_2} \frac{1}{C_3} + \frac{1}{C_3} \frac{1}{C_1}}{\frac{1}{C_3}}$$

$$\frac{1}{C_c} = \frac{\frac{1}{C_1} \frac{1}{C_2} + \frac{1}{C_2} \frac{1}{C_3} + \frac{1}{C_3} \frac{1}{C_1}}{\frac{1}{C_1}}$$