

CLASS TEST

PHYSICS

CLASS TEST # 30


SECTION-I

Single Correct Answer Type


5 Q. [3 M (-1)]

1. From a sphere of electrical conductivity K two planes cut a piece such that first plane passes through the centre of sphere and second parallel to first one at distance $R/2$ from centre then resistance between A and B.

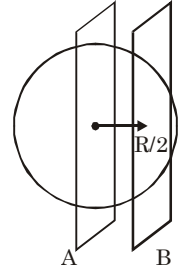- (A) $\frac{1}{\pi KR}$ (B) $\frac{\sqrt{3}}{\pi KR}$
(C) $\frac{\ln 3}{2\pi KR}$ (D) None




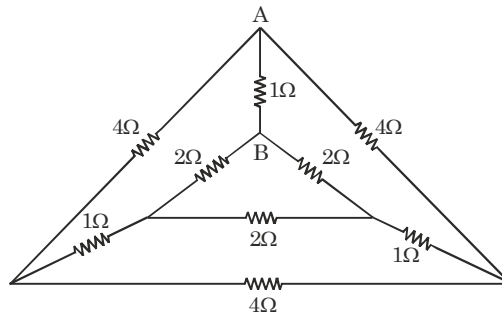2. Consider the circuit as shown in figure. The equivalent resistance between A and B is



- (A) $\frac{9}{7}\Omega$ (B) $\frac{1}{9}\Omega$ (C) $\frac{7}{9}\Omega$ (D) None

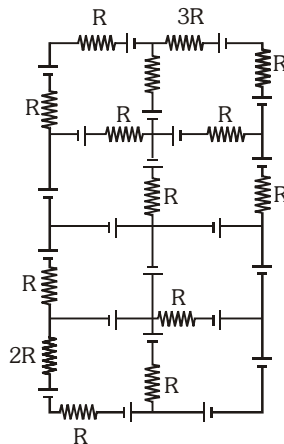
3. In the shown circuit all batteries have equal emf E . Current through the $2R$ resistance is




- (A) $\frac{3E}{2R}$ (B) $\frac{2E}{3R}$ (C) $\frac{E}{3R}$ (D) zero

4. A prism is made of wire mesh with each side having equal resistance R . A battery of 6 volt and zero resistance is connected across E and F as shown in the figure. The current in the branch AB, if R is equal to 5Ω , is :-

- (A) 0.6 A (B) 0.8 A
(C) 0.4 A (D) 2 A

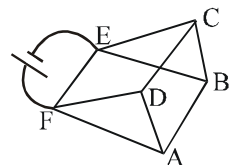

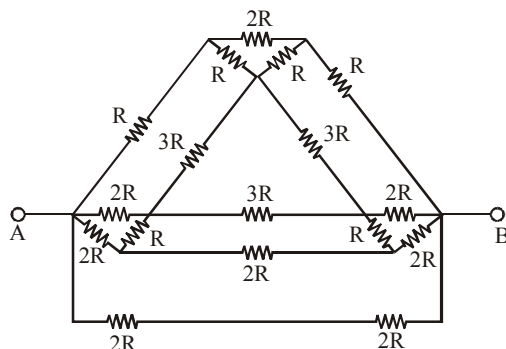5. Find equivalent resistance between A & B.



- (A) $\frac{R}{11}$ (B) $\frac{12R}{11}$ (C) R (D) $4R$

Multiple Correct Answer Type

4 Q. [4 M (-1)]


6. A metal sphere of radius a is surrounded by a concentric metal sphere of inner radius of b , where $b > a$. The space between the spheres is filled with a material whose electrical conductivity σ varies with the electric field strength E as $\sigma = kE$ where k is a constant. A potential difference V is maintained between spheres.

- (A) For $a < r < b$, current is $4\pi r^2 kE^2$
 (B) For $a < r < b$, current is $2\pi r^2 kE^2$

(C) Potential difference between spheres is $V = \sqrt{\frac{I}{4\pi k}} \ln\left(\frac{b}{a}\right)$ where I is total current

(D) Potential difference between spheres is $V = \sqrt{\frac{I}{2\pi k}} \ln\left(\frac{b}{a}\right)$ where I is total current

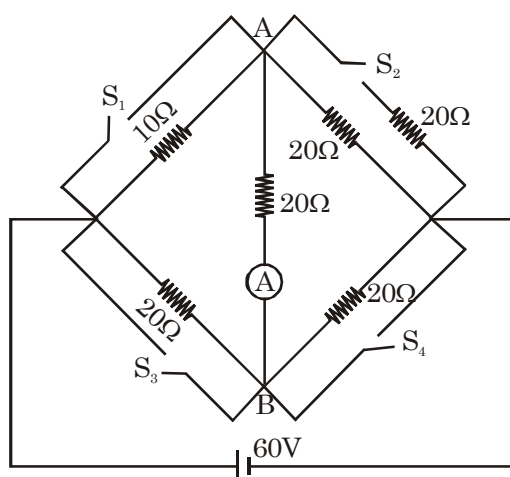7. Consider the circuit shown. Resistance connected between terminal 'A' and 'B' is 20Ω and ammeter is ideal. Then select the **CORRECT** statement :-




- (A) When switch ' S_1 ' and ' S_4 ' are closed, current reading of ammeter is 3 amp.
 (B) When switch ' S_3 ' and ' S_2 ' are closed, current reading of ammeter is $\frac{6}{5}$ amp.
 (C) When only ' S_2 ' is closed, reading of ammeter is zero.
 (D) When all the switch are close, reading of ammeter is 0 amp.


8. In given figure AB and CD are diameter of rings such that $AB = 10\text{ cm}$, $CD = 20\text{ cm}$ and $OA = 10\text{ cm}$. The resistance per unit length of straight segment is $1\Omega/\text{cm}$ and that of rings is $\frac{4}{\pi}\Omega/\text{cm}$. A battery of emf 60 V is

connected across AB. Select correct alternatives :

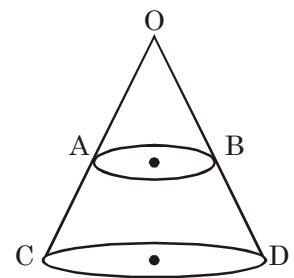- (A) Current through AO is 4 A
 (B) Current through BD is 1.5 A
 (C) Potential difference across CD is 30 V
 (D) Potential difference across AD is 40 V



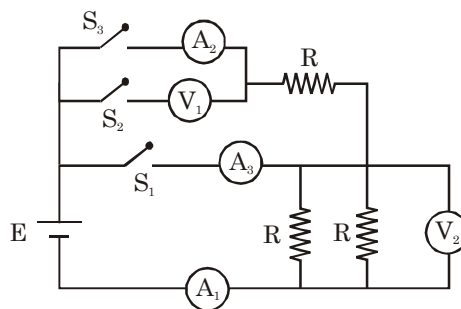9. All ammeter/voltmeter are ideal. Which of the statements are **CORRECT**.




- (A) when all switch are closed, reading of A_1 and A_3 are same.
 (B) When only S_2 is closed then reading of V_2 is E .
 (C) When only S_2, S_3 closed then a reading of A_1 is $\frac{2E}{3R}$
 (D) Reading of A_1 is independent of the function of switch S_2 .





Linked Comprehension Type (1 Para $\times$ 3 Q.) [4 M (-1)]
(Multiple Correct Answer Type)

Paragraph for Questions no. 10 to 12

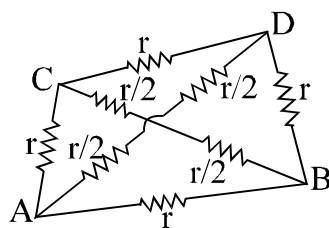The figure shows a tetrahedron, each side of which has a resistance r



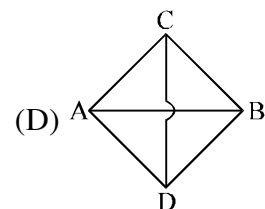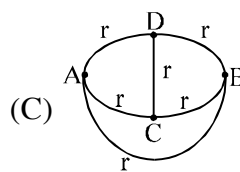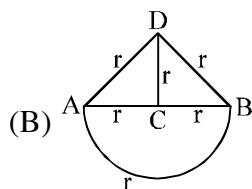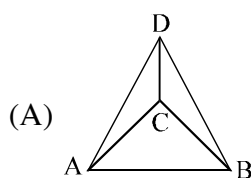10. Choose the correct statement(s) related to the resistance between any two points.
 (A) $R_{AB} = R_{BD} = R_{BC} = R_{CD} = R_{CA} = R_{AD}$
 (B) $R_{AB} = R_{AC} = R_{AD} = R_{BD} = R_{BC} \neq R_{CD}$
 (C) R_{CD} is the least
 (D) $R_{AB} = R_{AC} = R_{BC}$ and $R_{CD} = R_{AD} = R_{BD}$
11. Choose the correct diagram(s), which show two-dimensional equivalent of the tetrahedron.



12. If a battery is connected between any two points of the tetrahedron, then identify the correct statement(s).
 (A) The potentials of the other two points are always equal.
 (B) There always exists a branch through which no current flows.
 (C) The current coming out of the battery in each case is same.
 (D) None of these


Matching List Type (4 × 4)

2 Q. [3 M (-1)]


13. List-I shows electric circuits and List-II shows equivalent resistance between A and B.

List-I


List-II

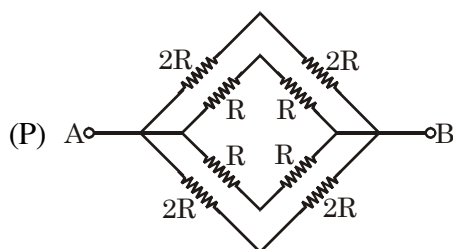


(1) $R/2$

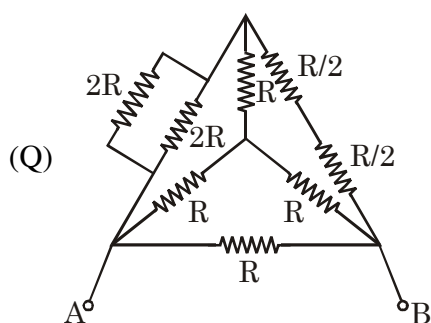

(2) $R/3$

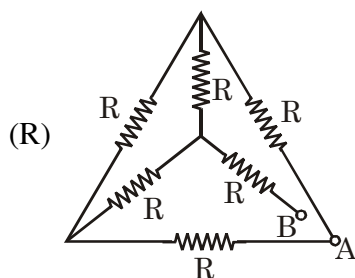

(3) $2R/3$

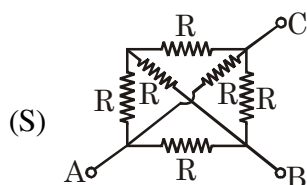

(4) $2R$


Code

	P	Q	R	S
(A)	3	1	4	2
(B)	2	1	4	2
(C)	3	1	4	1
(D)	2	1	4	3

14. Match the list-I with list-II.


List-I

List-II

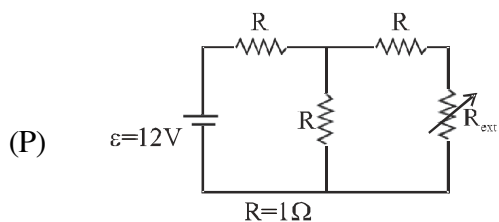

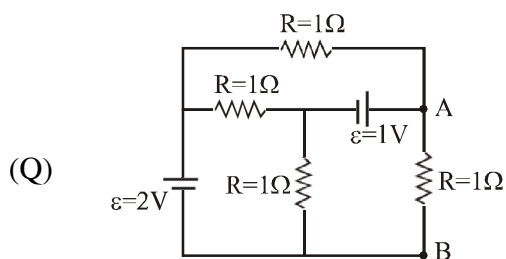
(1) $\frac{1}{2}$

Numerical value of maximum power (in watt) delivered to R_{ext} is



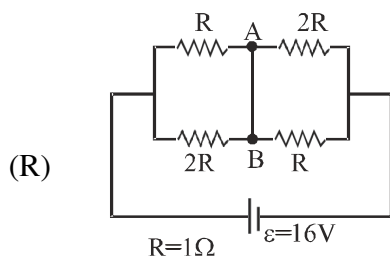
(2) $\frac{3}{2}$

Numerical value of potential difference (in volt) between points A & B is



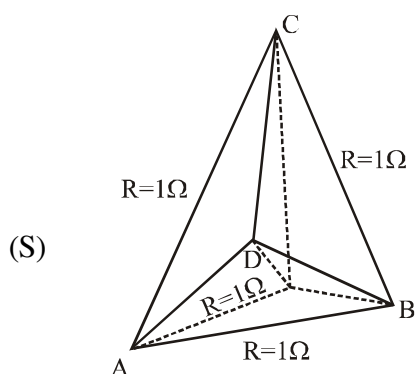(3) 6

Wire AB has negligible resistance.
Numerical value of current (in ampere) through AB is



(4) 4

Resistances are arranged in tetrahedron configuration. All resistance are equal.
Numerical value of equivalent resistance (in Ω) between A & B is

Code


	P	Q	R	S
(A)	4	3	2	1
(B)	3	2	4	1
(C)	1	2	3	4
(D)	2	3	1	4

SECTION-III


Numerical Grid Type (Ranging from 0 to 9)

5 Q. [4 M (0)]

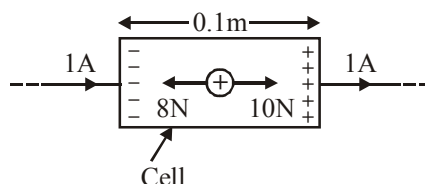
1. Figure shows a cell in which unit positive charge experiences a constant non electric force of 10N and a constant electric force of 8N in directions shown in the figure. The internal resistance of the cell is $r\ \Omega$. Fill $10r$ in OMR sheet.



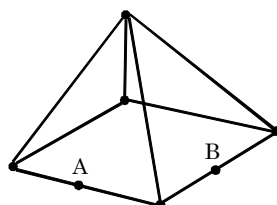
2. A regular pyramid of square is made of eight identical wires each resistance $12\ \Omega$ shown in the figure. The terminals A and B are the mid-points of the corresponding sides. Find equivalent resistance between the terminals A and B in ohms.



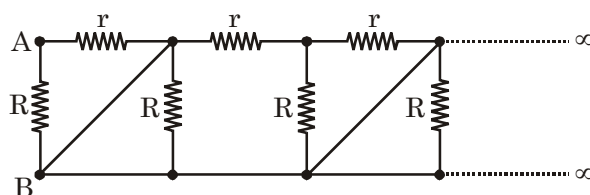
3. Find the equivalent resistance between the terminals A and B as shown on the diagram below. Put $R = 12\ \Omega$, $r = 6\ \Omega$ and neglect the resistance of leads.



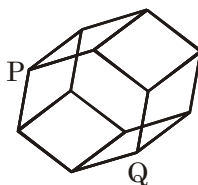4. All the wires on the front and the back hexagonal face (of the Skelton hexagonal prism) have resistance R . All the wires along the lines joining the vertices of two hexagons have resistance R . Take $R = \frac{20}{3}\ \Omega$. The equivalent resistance between P and Q as shown in the figure is ... Ω .



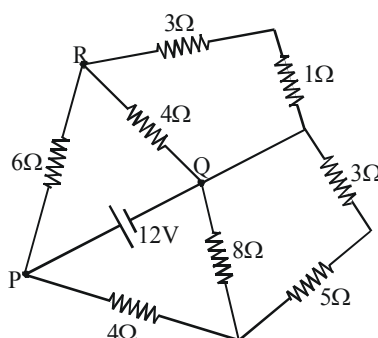5. Find n if the total power dissipated by the circuit is $6n$ watts.



SECTION-I

Single Correct Answer Type**5 Q. [3 M (–1)]**

1. Ans. (C)

2. Ans. (C)

3. Ans. (D)

4. Ans. (C)

5. Ans. (B)

Multiple Correct Answer Type**4 Q. [4 M (–1)]**

6. Ans. (A, C)

7. Ans. (A,B,C,D)

8. Ans. (B,C)

9. Ans. (A,C,D)

Linked Comprehension Type**(1 Para × 3 Q.) [4 M (–1)]****(Multiple Correct Answer Type)**

10. Ans. (A,D)

11. Ans. (A,B,C,D)

12. Ans. (A,B,C)

Matching List Type (4 × 4)**2 Q. [3 M (–1)]**

13. Ans. (C)

14. Ans. (B)

SECTION-III

Numerical Grid Type (Ranging from 0 to 9)**5 Q. [4 M (0)]**

1. Ans. 2

2. Ans. 8

3. Ans. 4

4. Ans. 7

5. Ans. 6